

Dr. Waheed Ahmad Younis

Do not submit this homework. There will be a quiz from this homework on Wednesday, 17 Nov 2021.

Topics covered in this week:

- Voltages and currents on transmission line:

$$V_s(z) = V_0^+ [e^{-\gamma z} + \Gamma e^{\gamma z}]$$

$$I_s(z) = \frac{V_0^+}{Z_0} [e^{-\gamma z} - \Gamma e^{\gamma z}]$$

- Max and min voltage and current on the line:

$$V_{max} = V_0^+ [1 + |\Gamma|] \quad V_{min} = V_0^+ [1 - |\Gamma|]$$

$$I_{max} = \frac{V_0^+}{Z_0} [1 + |\Gamma|] \quad I_{min} = \frac{V_0^+}{Z_0} [1 - |\Gamma|]$$

- Impedance on transmission line:

$$Z(l) = \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} Z_0 \quad \text{if loss-less} \quad Z(l) = \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} Z_0$$

- Max and min impedance on the line:

$$Z_{max} = \frac{V_{max}}{I_{min}} = Z_0 \frac{1+|\Gamma|}{1-|\Gamma|} = Z_0 (SWR) \quad Z_{min} = \frac{V_{min}}{I_{max}} = Z_0 \frac{1-|\Gamma|}{1+|\Gamma|} = \frac{Z_0}{SWR}$$

- Characteristic impedance of loss less line:

$$Z_0 = \sqrt{Z_{short} Z_{open}}$$

- Smith chart:

- Marking normalized impedance on the Smith chart
- Finding reflection co-efficient
- Finding standing wave ratio (SWR)

Q1. A transmission line with characteristic impedance $Z_0 = 100 \Omega$ has a load of $Z_L = 50 \Omega$. Load voltage is 50 volt. Calculate

- Maximum and minimum voltage on the line
- Location of voltage maxima and minima on the line
- The maximum and minimum impedance on the line. Where do these occur?
- Power transmitted to the load.

Solution:

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{50 - 100}{50 + 100} = \frac{-50}{150} = -\frac{1}{3} = 0.3333 \angle 180^\circ \quad SWR = \frac{1+|\Gamma|}{1-|\Gamma|} = \frac{1+0.333}{1-0.333} = 2$$

$$a. \quad V_s(z) = V_0^+ (e^{-\gamma z} + \Gamma e^{\gamma z}) \Rightarrow V_s(0) = V_0^+ (1 + \Gamma) = V_L = 50 \Rightarrow V_0^+ = \frac{50}{1+\Gamma} = \frac{50}{1-\frac{1}{3}} = 75$$

$$V_{max} = V_0^+ (1 + |\Gamma|) = 75 \left(1 + \frac{1}{3}\right) = 100 \text{ volt}$$

$$V_{min} = V_0^+ (1 - |\Gamma|) = 75 \left(1 - \frac{1}{3}\right) = 50 \text{ volt}$$

- Location of voltage maxima:

$$z_{max} = -\frac{\phi}{2\beta} - n\frac{\pi}{\beta} = -\frac{\phi+2n\pi}{2\beta} = -\frac{\pi+2n\pi}{2(2\pi)} \lambda = -\frac{1+2n}{4} \lambda = -\frac{\lambda}{4}, -\frac{3\lambda}{4}, -\frac{5\lambda}{4}, \dots$$

Location of voltage minima:

$$z_{min} = z_{max} + \frac{\lambda}{4} = 0, -\frac{\lambda}{2}, -\lambda, \dots$$

$$c. \quad Z_{max} = Z_0(SWR) = 100(2) = 200 \, \Omega \quad Z_{min} = \frac{Z_0}{SWR} = \frac{100}{2} = 50 \, \Omega$$

$$d. \quad P_L = \frac{|V_0^+|^2}{2Z_0} [1 - |\Gamma_L|^2] = \frac{75^2}{2(100)} \left[1 - \left| \frac{1}{3} \right|^2 \right] = 25 \, W$$

Q2. A transmission line with characteristic impedance $Z_0 = 50 \, \Omega$ has a load of $Z_L = 100 \, \Omega$. Load voltage is 50 volt. Calculate

- Maximum and minimum voltage on the line
- Location of voltage maxima and minima on the line
- The maximum and minimum impedance on the line. Where do these occur?
- Power transmitted to the load.

Solution:

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 - 50}{100 + 50} = \frac{50}{150} = \frac{1}{3} = 0.3333 \angle 0^\circ \quad SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.333}{1 - 0.333} = 2$$

$$a. \quad V_s(z) = V_0^+(e^{-\gamma z} + \Gamma e^{\gamma z}) \Rightarrow V_s(0) = V_0^+(1 + \Gamma) = 50 \Rightarrow V_0^+ = \frac{50}{1 + \Gamma} = \frac{50}{1 + \frac{1}{3}} = 37.5 \, \text{volt}$$

$$V_{max} = V_0^+(1 + |\Gamma|) = 37.5 \left(1 + \frac{1}{3} \right) = 50 \, \text{volt}$$

$$V_{min} = V_0^+(1 - |\Gamma|) = 37.5 \left(1 - \frac{1}{3} \right) = 25 \, \text{volt}$$

b. Location of voltage maxima:

$$z_{max} = -\frac{\phi}{2\beta} - n\frac{\pi}{\beta} = -\frac{\phi + 2n\pi}{2\beta} = -\frac{0 + 2n\pi}{2(2\pi)}\lambda = -\frac{n}{2}\lambda = 0, -\frac{\lambda}{2}, -\lambda, -\frac{3\lambda}{2}, \dots$$

Location of voltage minima:

$$z_{min} = z_{max} + \frac{\lambda}{4} = -\frac{\lambda}{4}, -\frac{3\lambda}{4}, -\frac{5\lambda}{4}, \dots$$

$$c. \quad Z_{max} = Z_0(SWR) = 50(2) = 100 \, \Omega \quad Z_{min} = \frac{Z_0}{SWR} = \frac{50}{2} = 25 \, \Omega$$

$$d. \quad P_L = \frac{|V_0^+|^2}{2Z_0} [1 - |\Gamma_L|^2] = \frac{37.5^2}{2(50)} \left[1 - \left| \frac{1}{3} \right|^2 \right] = 12.5 \, W$$

Q3. A lossless line has $Z_0 = 300 \, \Omega$, $l = 2 \, m$, and $v_p = 2.5 \times 10^8 \, m/s$. Let $Z_L = 300 \, \Omega$. Source voltage is $60 \angle 0^\circ$ volt at 100 MHz and source impedance is $300 \, \Omega$.

- Find voltage, current and power at the input of the line and at the load.
- If load impedance becomes $150 \, \Omega$, find the new values of part (a).
- Find voltage maxima, minima and their locations on the line.

Solution:

a. Since the line is matched ($Z_0 = Z_L$), reflection co-efficient is zero; standing wave ratio is unity (no standing waves; only travelling waves).

$$\text{Wavelength on the line} = \lambda = \frac{2.5 \times 10^8}{100 \times 10^6} = 2.5 \, m \text{ and } \beta = \frac{2\pi}{\lambda} = \frac{2\pi}{2.5} = 0.8\pi \, \text{rad/m}.$$

Attenuation constant is zero, electrical length of line is $\beta l = 1.6\pi \, \text{rad} = 288^\circ$, or 0.8λ .

Impedance at the input of the line $Z_{in} = Z_0 = 300 \, \Omega$

Using voltage divider rule, voltage at the input of the line $V_{in} = 30\angle 0^\circ$ volt

Voltage at the load $V_L = 30\angle -288^\circ$.

Current at the input of the line $I_{in} = \frac{30}{300}\angle 0^\circ = 0.1\angle 0^\circ$ Amp and at the load $I_L = 0.1\angle -288^\circ$ Amp.

Power delivered at the input of the line must all be delivered to the load

$$P_{in} = P_L = \frac{1}{2} V_{in} I_{in} \cos \theta = \frac{1}{2} (30)(0.1) = 1.5 \text{ Watt.}$$

- b. Load impedance $Z_L = 150 \Omega$. Reflection co-efficient $\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{150 - 300}{150 + 300} = -\frac{1}{3}$. Standing wave ratio $SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + \frac{1}{3}}{1 - \frac{1}{3}} = 2$.

$$\text{Impedance at the input of the line } Z_{in} = Z(2m) = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} = 300 \frac{150 + j300 \tan 288}{300 + j150 \tan 288} = 300 \frac{1 + j2 \tan 288}{2 + j \tan 288} = 300 \frac{1 - j6.1554}{2 - j3.0777} = 300 \frac{6.2361\angle -80.77^\circ}{3.6705\angle -56.98^\circ} = 509.69\angle -23.79^\circ = (466.38 - j205.6) \Omega$$

Current at the input of the line

$$I_{in} = \frac{60\angle 0^\circ}{300 + (466.38 - j205.6)} = \frac{60\angle 0^\circ}{766.38 - j205.6} = \frac{60\angle 0^\circ}{793.48\angle -15.02^\circ} = 0.0756\angle 15.02^\circ \text{ Amp.}$$

Voltage at the input of the line $V_{in} = (0.0756\angle 15.02^\circ)(509.69\angle -23.79^\circ) = 38.53\angle -8.77^\circ$ volt

Voltage at the load is a bit complicated:

$$\text{Recall } V_s(z) = V_0^+ [e^{-j\beta z} + \Gamma e^{j\beta z}].$$

$$\text{Hence } V_0^+ = \frac{V_s(z)}{e^{-j\beta z} + \Gamma e^{j\beta z}} = \frac{V_{in}}{e^{-j(-2)\beta} + \Gamma e^{j(-2)\beta}} = \frac{38.53\angle -8.77^\circ}{e^{j1.6\pi} - \frac{1}{3}e^{-j1.6\pi}} = \frac{38.53\angle -8.77^\circ}{(0.309 - j0.951) - (0.103 + j0.317)} = \frac{38.53\angle -8.77^\circ}{1.2846\angle 80.77^\circ} = 30\angle 72^\circ \text{ volt}$$

$$\text{Now } V_L = V_s(0) = V_0^+ [e^{-j\beta(0)} + \Gamma e^{j\beta(0)}] = 30\angle 72^\circ \left[1 - \frac{1}{3}\right] = 20\angle 72^\circ \text{ volt}$$

$$I_L = \frac{20}{150}\angle 72^\circ = 0.133\angle 72^\circ \text{ Amp}$$

$$P_{in} = P_L = \frac{1}{2} V_{in} I_{in} \cos \theta = \frac{1}{2} (38.53)(0.0756) \cos(15.02^\circ + 8.77^\circ) = 1.33 \text{ Watt.}$$

$$\text{c. } V_{s,max} = |V_0^+| [1 + |\Gamma|] = 30 \left[1 + \frac{1}{3}\right] = 40 \text{ volt}$$

$$V_{s,min} = |V_0^+| [1 - |\Gamma|] = 30 \left[1 - \frac{1}{3}\right] = 20 \text{ volt}$$

$$z_{max} = -\frac{\phi}{2\beta} - n \frac{\pi}{\beta} = -\frac{\pi}{2(0.8\pi)} - n \frac{\pi}{0.8\pi} = -0.625 - 1.25n = -0.625 \text{ m}, -1.875 \text{ m}$$

$$z_{min} = \frac{\lambda}{4} + z_{max} = 0.625 - 0.625, 0.625 - 1.875 = 0 \text{ m}, -1.25 \text{ m}$$

Q4. Mark the following load impedances (given in Ohms) on the Smith chart ($Z_0 = 50 \Omega$):

$$Z_L = 30 + j40, 25 - j45, j15, -j25, 400 + j800, 50, SC, OC$$

Solution:

Z_L	Inductive 30+j40	Capacitive 25-j45	Pure inductive j15	Pure capacitive -j25	Large 400+j800	Matched 50+j0	Short circuit 0+j0	Open circuit $\infty \pm j\infty$
$z_L = Z_L/Z_0$	0.6+j0.8	0.5-j0.9	0+j0.3	0-j0.5	8+j16	1+j0	0+j0	$\infty \pm j\infty$
	P0	P1	P2	P3	P4	P5	P6	P7

