

Dr. Waheed Ahmad Younis

Do not submit this homework. There will be a quiz from this homework on Wednesday, 03 Nov 2021.

Topics covered in this week:

- Transmission line theory – distributed parameters (Recall that circuit theory – lumped parameters).

$$\frac{dV_s}{dz} = -(R + j\omega L)I_s$$

$$\frac{dI_s}{dz} = -(G + j\omega C)V_s$$

$$\text{Propagation constant} = \gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\text{Characteristic impedance} = Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

$$\frac{d^2V_s}{dz^2} = -(R + j\omega L)\frac{dI_s}{dz} = (R + j\omega L)(G + j\omega C)V_s = \gamma^2 V_s$$

$$V_s(z) = V_0 e^{-\gamma z} \quad V(z, t) = V_0 e^{-\alpha z} \cos(\omega t - \beta z)$$

$$I_s(z) = \frac{V_0}{Z_0} e^{-\gamma z} \quad I(z, t) = \frac{V_0}{Z_0} e^{-\alpha z} \cos(\omega t - \beta z)$$

$$\lambda = \frac{2\pi}{\beta}, \quad v = \frac{\omega}{\beta}$$

Q1. At a frequency of 100 MHz, the following are the values of a transmission line:

$R = 0.15 \, \Omega/m$, $L = 0.25 \, \mu H/m$, $C = 80 \, pF/m$, $G = 8 \, \mu S/m$. Calculate the values of (a) attenuation constant, (b) phase constant, (c) wavelength, (d) phase velocity, and (e) characteristic impedance.

Solution:

$$\begin{aligned} \text{a. } \gamma &= \sqrt{(R + j\omega L)(G + j\omega C)} \\ &= \sqrt{(0.15 + j2\pi 10^8(0.25 \times 10^{-6}))(8 \times 10^{-6} + j2\pi 10^8(80 \times 10^{-12}))} \\ &= \sqrt{(0.15 + j157.08)(0.000008 + j0.0503)} = \sqrt{-7.8957 + j0.0088} \\ &= 0.0016 + j2.8099 \end{aligned}$$

$$\text{Attenuation constant} = \alpha = 0.0016 \, m^{-1}$$

$$\text{b. Phase constant} = \beta = 2.8099 \, rad/m.$$

$$\text{c. Wavelength} = \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{2.8099} = 2.24 \, m.$$

$$\text{d. Phase velocity} = v_p = \frac{\omega}{\beta} = \frac{2\pi 10^8}{2.8099} = 2.24 \times 10^8 \, m/s.$$

$$\begin{aligned} \text{e. Characteristic impedance} = Z_0 &= \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{0.15 + j157.08}{0.000008 + j0.0503}} = \sqrt{3125 - j2.4868} \\ &= 55.9 - j0.0222 = (55.9 \angle -0.0227^\circ) \, \Omega \end{aligned}$$

Q2. A transmission line operating at 500 Mrad/sec has $R = 25 \, \Omega/m$, $L = 0.5 \, \mu H/m$, $C = 32 \, pF/m$, $G = 100 \, \mu S/m$. Calculate (a) γ , α , β , v_p , λ , and Z_0 , (b) What distance down the line

can a voltage wave travel before it is reduced to 10% of its original amplitude, and (c) what distance must it travel to undergo a 90° phase shift.

Solution:

$$\begin{aligned}
 \text{a. } \gamma &= \sqrt{(R + j\omega L)(G + j\omega C)} \\
 &= \sqrt{[25 + j(5 \times 10^8)(0.5 \times 10^{-6})][100 \times 10^{-6} + j(5 \times 10^8)(32 \times 10^{-12})]} \\
 &= \sqrt{(2.5 + j250)(0.0001 + j0.016)} = \sqrt{-3.9975 + j0.425} \\
 &= 0.1061 + j2.0022 \\
 \alpha &= 0.1061 \text{ m}^{-1} \\
 \beta &= 2.0022 \text{ rad/m} \\
 v_p &= \frac{\omega}{\beta} = \frac{5 \times 10^8}{2.0022} = 2.497 \times 10^8 \text{ m/s} \\
 \lambda &= \frac{2\pi}{\beta} = \frac{2\pi}{2.0022} = 3.138 \text{ m} \\
 Z_0 &= \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{2.5 + j250}{0.0001 + j0.016}} = \sqrt{15634 - j1464.8} = 125.17 - j5.851 \\
 &= (125.3 \angle -2.68^\circ) \Omega \\
 \text{b. } V(z) &= V_0 e^{-\alpha z} \Rightarrow z = -\frac{\ln[V(z)/V_0]}{\alpha} = -\frac{\ln[10/100]}{0.1061} = 21.7 \text{ m} \\
 \text{c. } \beta z &= \frac{\pi}{2} \Rightarrow z = \frac{\pi}{2\beta} = \frac{\pi}{2(2.0022)} = 0.785 \text{ m}
 \end{aligned}$$

Q3. At a frequency of 80 MHz, a lossless transmission line has a characteristic impedance of 300Ω and a wavelength of 2.5 m. Find (a) L, (b) C.

Solution:

$$\begin{aligned}
 \text{For lossless transmission line: } Z_0 &= \sqrt{\frac{L}{C}} = 300 \Omega \\
 \text{and } \lambda &= \frac{2\pi}{\omega\sqrt{LC}} \Rightarrow \sqrt{LC} = \frac{2\pi}{\omega\lambda} = \frac{2\pi}{2\pi f\lambda} = \frac{1}{\lambda f} = \frac{1}{2.5(80 \times 10^6)} = 5 \times 10^{-9} \\
 \text{a. } L &= \sqrt{LC} \sqrt{\frac{L}{C}} = (5 \times 10^{-9})(300) = 1.5 \times 10^{-6} = 1.5 \mu\text{H/m} \\
 \text{b. } C &= \sqrt{LC} \div \sqrt{\frac{L}{C}} = \frac{5 \times 10^{-9}}{300} = 16.67 \times 10^{-12} = 16.67 \text{ pF/m}
 \end{aligned}$$

Q4. A 75-ohm coaxial line has a current $I(z, t) = 1.8 \cos(3.77 \times 10^9 t - 18.13z) \text{ mA}$. Determine (a) the frequency, (b) the phase velocity, (c) the wavelength, (d) the phasor form of the current, and (e) the time domain voltage on the line.

Solution:

$$\begin{aligned}
 \text{a. } f &= \frac{\omega}{2\pi} = \frac{3.77 \times 10^9}{2\pi} = 600 \times 10^6 \text{ Hz} = 600 \text{ MHz} \\
 \text{b. Phase velocity} &= v_p = \frac{\omega}{\beta} = \frac{3.77 \times 10^9}{18.13} = 2.08 \times 10^8 \text{ m/s} \\
 \text{c. } \lambda &= \frac{2\pi}{\beta} = \frac{2\pi}{18.13} = 0.3466 \text{ m} \\
 \text{d. } I_s(z) &= 1.8e^{-j18.13z} \\
 \text{e. } V(z, t) &= (75)0.0018 \cos(3.77 \times 10^9 t - 18.13z) = 0.135 \cos(3.77 \times 10^9 t - 18.13z) \text{ volt}
 \end{aligned}$$

Q5. An antenna cable has a characteristic impedance of 300-ohm and phase velocity “c”. Find the phase constant when receiving (a) VHF channel 3 (63 MHz), and (b) UHF channel 69 (803 MHz).

Solution:

$$\text{a. } \beta = \frac{\omega}{v_p} = \frac{\omega}{c} = \frac{2\pi(63 \times 10^6)}{3 \times 10^8} = 1.32 \text{ rad/m}$$

$$\text{b. } \beta = \frac{\omega}{v_p} = \frac{\omega}{c} = \frac{2\pi(803 \times 10^6)}{3 \times 10^8} = 16.82 \text{ rad/m}$$

Q6. A low loss antenna cable has an attenuation of 1 dB/km. The phase velocity is 1.353×10^8 m/s. The frequency of the signal is 80 MHz (approximately middle frequency of VHF channel 5).

- Find the propagation constant.
- This cable is used to connect a cable TV distribution center to a TV, 20 km away. If the TV requires a signal of at least 100 mV, what must be the signal amplitude at the generator.

Solution:

$$\text{a. } V(z) = V_0 e^{-\alpha z} \Rightarrow V(1 \text{ km}) = V_0 e^{-\alpha(1000 \text{ m})} \Rightarrow \frac{V_0}{V(1 \text{ km})} = e^{1000\alpha}$$

$$\Rightarrow 20 \log \frac{V_0}{V(1 \text{ km})} = 20 \log e^{1000\alpha}$$

The quantity on the left is given as 1 dB. Hence

$$20 \log e^{1000\alpha} = 1 \Rightarrow e^{1000\alpha} = 10^{0.05} \Rightarrow \alpha = \frac{\ln 10^{0.05}}{1000} = 1.151 \times 10^{-4} \text{ Np/m}$$

$$\beta = \frac{\omega}{v_p} = \frac{2\pi(80 \times 10^6)}{1.353 \times 10^8} = 3.715 \text{ rad/m}$$

$$\gamma = \alpha + j\beta = (1.151 \times 10^{-4} + j3.715) \text{ m}^{-1}$$

$$\text{b. } V(z) = V_0 e^{-\alpha z}$$

$$\Rightarrow V_0 = V(z) e^{\alpha z} = V(20,000 \text{ m}) e^{\alpha(20,000)} = 0.1 e^{(1.151 \times 10^{-4})(20,000)} = 0.9994 \text{ volt}$$

Q7. A TV cable has an attenuation of 10 dB/km. What is the required voltage amplitude at the generator to produce a signal of 10 mV at the TV 10 km away?

Solution:

Attenuation in 10 km = (10 dB/km) x (10 km) = 100 dB.

$$\text{Hence, } 20 \log \frac{V_0}{V(10 \text{ km})} = 100 \text{ dB} \Rightarrow \log \frac{V_0}{V(10 \text{ km})} = \frac{100}{20} = 5 \Rightarrow \frac{V_0}{V(10 \text{ km})} = 10^5$$

$$\Rightarrow V_0 = V(10 \text{ km}) 10^5 = (0.01) 10^5 = 1,000 \text{ volt}$$