

ELEC3100- Fundamentals of Electromagnetic Fields and Waves

Module 1: Learning Material

Week 2: Wave Propagation on Transmission Line

Course Learning Outcomes

1. Calculate the transmission lines characteristic parameters.
2. Analyze the wave propagation and standing waves on a transmission line.


Lecturer Name: Dr. Hilal Fadhil

Academic Year: 2021-2022

Course Coordinator Name: Dr. Hilal A. Fadhil

Wave propagation on a transmission line

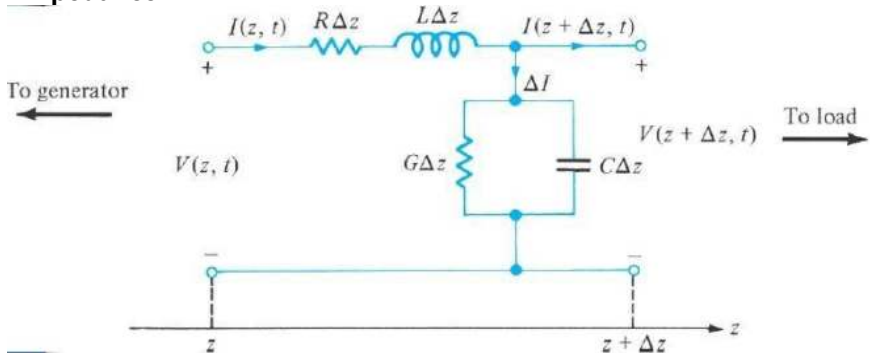- The generalized lumped-element model of a transmission line can be used to derive the wave propagation along the line. In addition, it can be used to calculate its characteristic parameters.
- These parameters are: characteristic impedance, propagation constant (phase and attenuation), phase velocity, and input impedance .



Wave propagation on a transmission line

General Solutions of Transmission-Line Equations

The voltage $v(z,t)$ and current $i(z,t)$ along the transmission line are functions of position and time.

For uniform transmission line with time-harmonic variation $e^{j\omega t}$, the transmission-line equations (Voltage and Current) are given by:

$$\frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) = 0 \quad \longrightarrow \quad \text{Voltage}$$

$$\frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) = 0 \quad \longrightarrow \quad \text{Current}$$

Where γ is the **propagation constant** and can be determined by the following equation

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$


α = attenuation constant [neper/m]

$$\gamma = \alpha + j\beta$$

β = phase constant [radians/m]

Solutions of Transmission-Line Equations

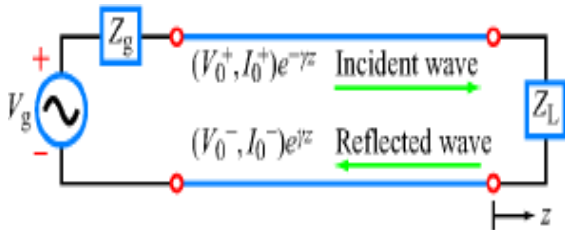Steady state wave propagation along a transmission line (TL), voltage $V(z)$ and current $I(z)$ is usually determined by employing phasor analysis (phasor domain). The figure below shows the wave propagation along a TL.



The general solution of the TL wave equations is given as below:

$$V(z) = V_o^+ e^{-\gamma z} + V_o^- e^{+\gamma z}$$

$$I(z) = I_o^+ e^{-\gamma z} - I_o^- e^{+\gamma z}$$


$$I_o^+ = \frac{V_o^+}{Z_o}$$

$$I_o^- = \frac{V_o^-}{Z_o}$$

Forward Travelling Wave

Backward Travelling Wave

Solutions of Transmission-Line Equations

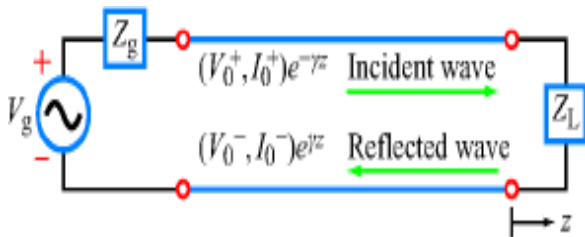

Where V_0^+ , V_0^- , I_0^+ , I_0^- are the initial amplitude of the voltages and currents. Z_0 is the **characteristic impedance** of the line and γ is the propagation constant.

In general, transmission line support two waves (**forward wave** and **backward wave**) traveling in opposite directions with their relative phase changes along the line.

Solutions of Transmission- Instantaneous Expression

The instantaneous expression of the voltage $v(z,t)$ across the transmission line can be determined from the phasor of voltage as follow:

$$v(z,t) = \text{Rel}[V(z)e^{j\omega t}]$$

$$v(z,t) = \text{Rel}[V_o^+ e^{-\gamma z} e^{j\omega t} + V_o^- e^{\gamma z} e^{j\omega t}]$$

$$v(z,t) = \text{Rel}[V_o^+ e^{-\alpha z} e^{-j\beta z} e^{j\omega t} + V_o^- e^{\alpha z} e^{j\beta z} e^{j\omega t}]$$

$$v(z,t) = \text{Rel}[V_o^+ e^{-\alpha z} e^{j(\omega t - \beta z)} + V_o^- e^{\alpha z} e^{j(\omega t + \beta z)}]$$

Using the trigonometric identity $e^{j\theta} = \cos\theta + j\sin\theta$, the instantaneous voltage is given by


$$v(z,t) = V_o^+ e^{-\alpha z} \cos(\omega t - \beta z) + V_o^- e^{\alpha z} \cos(\omega t + \beta z)$$

Attenuation Constant α

The attenuation factor α decreases the amplitude of the voltage and current wave along the TL.


- For +ve traveling wave:

$$|V_o^+| \cos(\omega t - \beta z + \phi_+) e^{-\alpha z}$$

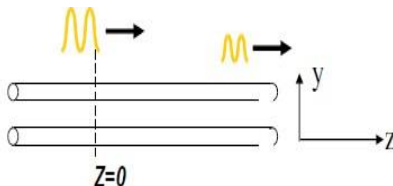

- For -ve traveling wave:

$$|V_o^-| \cos(\omega t + \beta z + \phi_-) e^{\alpha z}$$

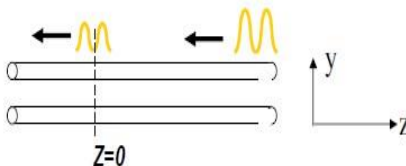


Attenuation Constant α

- Losses are due to:
 - **Conductor loss** (which usually increases with frequency)
 - **Insulation (dielectric) loss.**

Let V_o^+ is the input to the TL

Then, $|V(z)| = |V_o^+|e^{-\alpha z}$ and $|I(z)| = |I_o^+|e^{-\alpha z}$

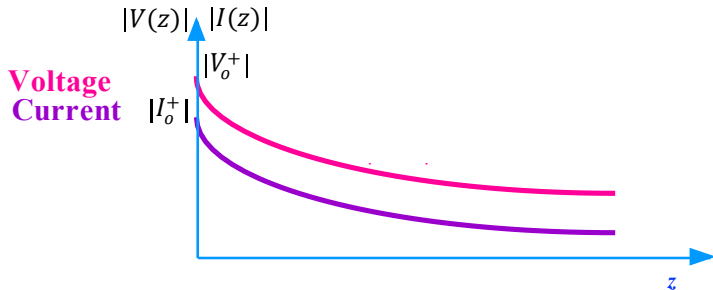

Phase Constant β


- The **phase shift** along the transmission line is due to the **time delay** caused by the distance z .
- $e^{-j\beta z}$ represents this phase shift.
- The phase constant (phase velocity) β can be determined by the following equation

$$\beta = \frac{2\pi}{\lambda} = \frac{\omega}{u_p} \text{ rad/m}$$

λ : wavelength (m)

ω : $2\pi f$, f is frequency

u_p : is the velocity of the wave

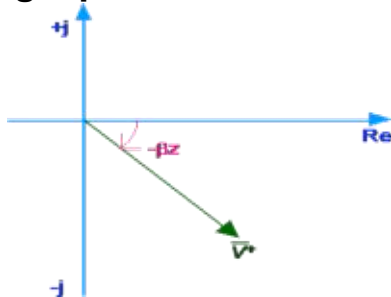

Characteristic Impedance Z_o

- ❖ The characteristic impedance of the line is the ratio of positively traveling voltage wave to current wave at any point on the line.
- ❖ Characteristic impedance (Z_o) is the most important parameter for any transmission line.

$$Z_o = \frac{V_o^+}{I_o^+}$$

$$Z_o = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

Z_o is frequency
dependent and complex

The characteristic admittance $Y_o = 1/Z_o$

Variation of Z_o vs. Frequency

At $\omega = 0$:

$$Z_o = \sqrt{\frac{R'}{G'}} \rightarrow \infty \quad \text{since } G' \text{ is very small.}$$

At high frequencies:

$$\omega L' \gg R' \quad \text{and}$$

$$\omega C' \gg G'$$

$$\therefore \lim_{\omega \rightarrow \infty} Z_o = \sqrt{\frac{L'}{C'}} \quad \text{which is also real.}$$

Characteristics of RG58-C/U

Parameters for RG58-C/U coaxial cable

- $R' = 1 \Omega / \text{m}$
- $L' = 252 \text{ nH} / \text{m}$
- $G' = 0.0004 \text{ S} / \text{m}$
- $C' = 101 \text{ pF} / \text{m}$



RG 4 A/U
40003

RG 11 A/U
40001

RG 58 C/U
40003

RG 59 B/U
40004

RG 62 A/U
40005

RG 71 B/U
40006

Line Impedance

We can define a **line impedance** as the ratio of the line voltage and line current at a distance ***d*** from the load:

$$Z_{in} = \frac{V_{in}}{I_{in}}$$



For **lossy line**, the line impedance (**Z**) can be determined by the following equation:

$$Z = Z_O \left[\frac{Z_R + Z_O \tanh \gamma d}{Z_O + Z_R \tanh \gamma d} \right]$$

For **lossless line**, the line impedance (**Z**) can be determined by the following equation:

$$Z = Z_O \left[\frac{Z_R + jZ_O \tan \beta d}{Z_O + jZ_R \tan \beta d} \right]$$

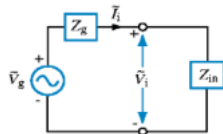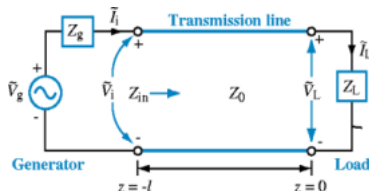* **Z** varies along the line with distance *d* and frequency



Line Impedance vs. Z_R

Consider $Z_R = 0 \Omega$ (i.e. a short circuit termination):

$$Z = jZ_o \tan \beta d$$

For $Z_R = \infty \Omega$ (i.e. an open circuit termination):

$$Z = -jZ_o \cot \beta d$$

Impedance is
purely reactive

For $Z_R = Z_o$ (i.e. a matched termination):

$$Z = Z_o$$

for the matched line, Z is constant and equal to Z_o .