



EE 201 Electric Circuits 1

Final Exam


19 April 2021

Name: _____

ID Number: _____

Problem # 1:

Given the circuit below:

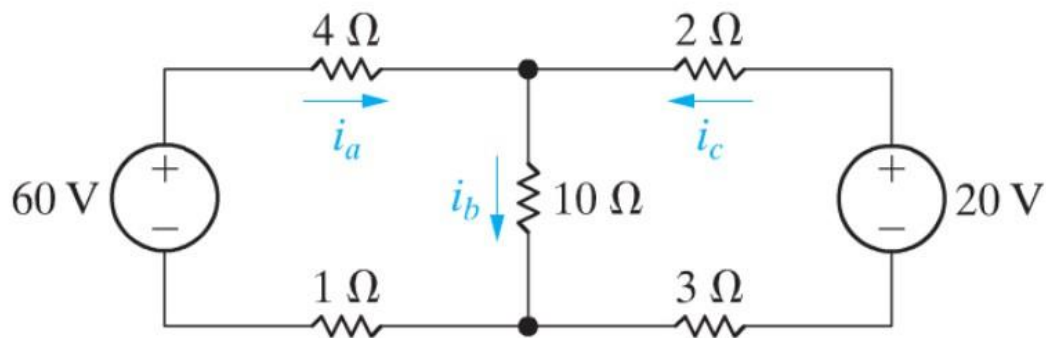

- What is the value of i_a .
- What is the value of i_b .
- What is the value of i_c .
- Find the value of the power delivered/dissipated by the independent voltage source 60 V ?