



EE 201 Electric Circuits 1

Final Exam


19 April 2021

Name: _____

ID Number: _____

Problem # 5:

Given the circuit bellow,

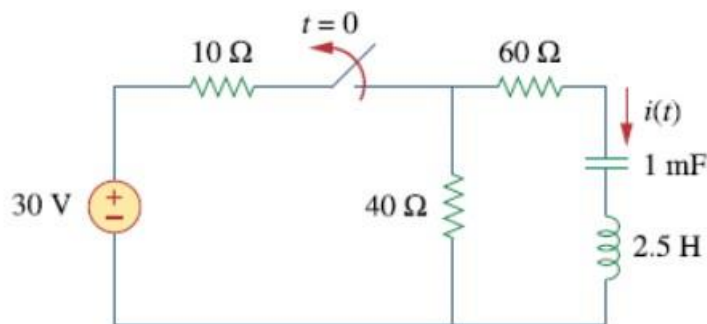

- What is the initial current across the inductor ?
- What is the initial voltage across the capacitor ?
- Find the $i(t)$ for $t > 0$ in the circuit?

<p>1- Overdamped $\alpha \geq \omega_0$</p> $s_1 = -\alpha + \sqrt{(\alpha)^2 - (\omega_0)^2}$ $s_2 = -\alpha - \sqrt{(\alpha)^2 - (\omega_0)^2}$ $i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ $i(0^+) = A_1 + A_2$ $\frac{di(0^+)}{dt} = S_1 A_1 + S_2 A_2$	<p>2- Under damped $\alpha < \omega_0$</p> $s_1 = -\alpha + j\omega_d$ $s_2 = -\alpha - j\omega_d$ $\omega_d = \sqrt{(\omega_0)^2 - (\alpha)^2}$ $i(t) = (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t}$ $i(0^+) = B_1$ $\frac{di(0^+)}{dt} = -\alpha B_1 + \omega_d B_2$	<p>3- Critically damped</p> $s_1 = -\alpha + \sqrt{(\alpha)^2 - (\omega_0)^2}$ $s_2 = -\alpha - \sqrt{(\alpha)^2 - (\omega_0)^2}$ $i(t) = (D_1 t + D_2) e^{-\alpha t}$ $i(0^+) = D_2$ $\frac{di(0^+)}{dt} = D_1 - \alpha D_2$
--	---	--

Table: Natural Responses of RLC Circuits (SERIES).