

Chapter 1

Single phase systems and power measurements

1. Value and representation of a sinusoidal signal

1.1. Periodic, alternating and sinusoidal signal

A voltage u is periodic, if its instantaneous value $u(t)$ is such that:

$$u(t) = u(t+T); \begin{cases} T : \text{period} \\ \frac{1}{T} : \text{frequency } f \end{cases}$$

- The signal u is called alternative (AC), if it is continually changing from zero up to the positive peak, through zero to the negative peak and back to zero again (sometimes positive and sometimes negative). If $u(t)$ vanishes only twice in each period, the positive alternance is the part of the period in which u is positive, the negative alternance is that in which u is negative.
- The expression of the sinusoidal voltage u is given by:

$$u(t) = U_{\max} \cos(\omega t + \varphi), \text{ avec } \begin{cases} U_{\max} = \sqrt{2}U : \text{peak value} \\ U = U_{RMS} : \text{effective value} \\ \omega = 2\pi f = \frac{2\pi}{T} : \text{angular velocity (rad/s)} \\ \omega t + \varphi : \text{instantaneous phase (rad)} \\ \varphi : \text{initial phase (rad)} \end{cases}$$

1.2. Average value

The mean value of the periodic voltage $u(t)$ with period T is defined by :

$$U_{mean} = \frac{1}{T} \int_0^T u(t) dt$$

Example :

Let's $u(t) = U_{\max} \cos(\omega t + \varphi)$ a sinusoidal signal defined by

$$\begin{aligned} U_{mean} &= \frac{1}{T} \int_0^T U_{\max} \cos(\omega t + \varphi) dt \\ &= \frac{U_{\max}}{T} \int_0^T \cos(\omega t + \varphi) dt \\ &= \frac{U_{\max}}{T} \times \frac{1}{\omega} [\sin(\omega t + \varphi)]_0^T \end{aligned}$$

$$\Rightarrow U_{mean} = \frac{U_{max}}{2\pi} [\sin(2\pi + \varphi) - \sin(\varphi)] = 0$$

1.3. Effective Value: the Root mean Square Value (RMS)

If we are dealing with a periodic voltage signal u such that $u(t) = u(t + T)$, its effective value U_{eff} is defined by:

$$U_{eff} = \sqrt{\frac{1}{T} \int_0^T u^2(t) dt}$$

1.4. Representations of sinusoidal magnitudes

1.4.1 Vector Representation

We consider a disc with center O rotating with the angular velocity ω . Let's M_1 and M_2 two points of disc showing the points of the vectors, respectively current and voltage (Fig 1.1).

- $OM_1 = I'$ makes an angle θ_1 with the origin (vector rotating at angular velocity ω),
 $\theta_1 = \omega t + \varphi_1$.
- $OM_2 = U$ makes an angle θ_2 with the origin (vector rotating at angular velocity ω),
 $\theta_2 = \omega t + \varphi_2$.
- Instantaneous values of current $i(t)$ and voltage $u(t)$ are the projection of rotating vectors \vec{I} and \vec{U} on a fixed axis.

$$\begin{cases} i(t) = I_{max} \cos(\omega t + \varphi_1) \\ u(t) = U_{max} \cos(\omega t + \varphi_2) \end{cases}$$

I_{max} and U_{max} are the maximum values of vectors modules \vec{I} and \vec{U} .

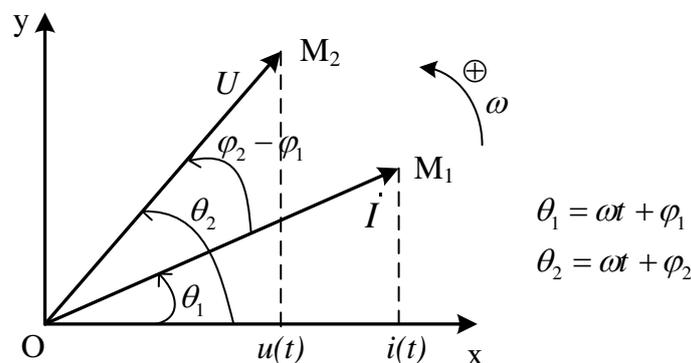


Fig 1.1

The angle deviation φ between \vec{U} and \vec{I} is called angular phase shift ($\varphi = \varphi_2 - \varphi_1 = \varphi_U - \varphi_I$).

- If ($\varphi = 0$), the voltage and the current are *in phase*.
- If ($\varphi > 0$), the voltage leads the current.
- If ($\varphi = \pi/2$), the voltage is 90° *out of phase* with the current.
- If ($\varphi < 0$), the voltage lags the current.
- If ($\varphi = -\pi/2$), the voltage is -90° *out of phase* with the current.
- If ($\varphi = \pi$), the voltage and the current are in phase opposition.

1.4.2. Complex Notation

Consider the instantaneous current i and the voltage u signals defined by:

$$\begin{cases} i(t) = I_{\max} \cos(\omega t) = \sqrt{2}I \cos(\omega t) \\ u(t) = U_{\max} \cos(\omega t + \varphi) = \sqrt{2}U \cos(\omega t + \varphi) \end{cases}$$

These quantities can be characterized by the components of their representative vectors in the complex plane.

- \vec{I} have as components I and 0 .
- \vec{U} have as components $U \cos(\varphi)$ and $U \sin(\varphi)$.

The points $M_1(I, 0)$ and $M_2(U \cos(\varphi), U \sin(\varphi))$ present in the complex plane, the following modules :

$$\begin{cases} Z_1 = I + j0 = Ie^{j0} = \vec{I} \\ Z_2 = U \cos(\varphi) + jU \sin(\varphi) = Ue^{j\varphi} = \vec{U} \end{cases}$$

In complex notation, $i(t)$ and $u(t)$ can be represented by their complex amplitudes \vec{I} and \vec{U} defined by their effective values I and U and their phases in the origin 0 and φ .

1.5. Properties of sinusoidal quantities

1.5.1 Addition - subtraction

we pose :

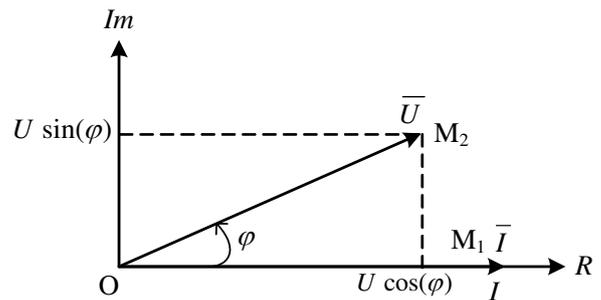


Fig 1.2

$$\begin{aligned}
 & \left. \begin{aligned} i_1(t) &= \sqrt{2}I_1 \cos(\omega t + \varphi_1) \\ i_2(t) &= \sqrt{2}I_2 \cos(\omega t + \varphi_2) \end{aligned} \right\} i(t) = i_1(t) + i_2(t) = \sqrt{2}I \cos(\omega t + \varphi) \\
 & \Rightarrow \bar{I} = \bar{I}_1 + \bar{I}_2 \\
 & \Rightarrow I(\cos \varphi + j \sin \varphi) = I_1(\cos \varphi_1 + j \sin \varphi_1) + I_2(\cos \varphi_2 + j \sin \varphi_2) \\
 & \Rightarrow \begin{cases} I \cos \varphi = I_1 \cos \varphi_1 + I_2 \cos \varphi_2 \\ I \sin \varphi = I_1 \sin \varphi_1 + I_2 \sin \varphi_2 \end{cases} \\
 & \Rightarrow \begin{cases} I = \sqrt{I^2 \cos^2 \varphi + I^2 \sin^2 \varphi} \\ \varphi = \operatorname{arctg} \left(\frac{I \sin \varphi}{I \cos \varphi} \right) \end{cases}
 \end{aligned}$$

1.1.5.2. Derivation - Integration

$$\begin{aligned}
 & i(t) = \sqrt{2}I \cos(\omega t + \varphi) \\
 & \Rightarrow \begin{cases} \frac{di(t)}{dt} = \omega \sqrt{2}I \cos(\omega t + \varphi + \frac{\pi}{2}) = -\omega \sqrt{2}I \sin(\omega t + \varphi) \\ \int i(t) dt = \frac{\sqrt{2}I}{\omega} \cos(\omega t + \varphi - \frac{\pi}{2}) = \frac{\sqrt{2}I}{\omega} \sin(\omega t + \varphi) \end{cases} \\
 & \Rightarrow \begin{cases} i(t) = \bar{I} \\ \frac{di(t)}{dt} \Rightarrow j \omega \bar{I} \\ \int id(t) dt \Rightarrow \frac{1}{j \omega} \bar{I} = -\frac{j}{\omega} \bar{I} \end{cases}
 \end{aligned}$$

2. Impedance

- The impedance Z is defined as the quotient of the effective value of voltage by that of the current : $Z = \frac{U}{I}$.

- The complex impedance \bar{Z} is defined as the quotient of the complex quantities representing voltage and current : $\bar{Z} = \frac{\bar{U}}{\bar{I}}$.







If $\bar{Z} = R + jX$, with $\begin{cases} R: \text{total resistance of a circuit} \\ X: \text{total reactance of a circuit} \end{cases}$

\bar{Z} have a module Z such that $|\bar{Z}| = Z = \sqrt{R^2 + X^2}$.

\bar{Z} have an argument φ such that $\operatorname{tg} \varphi = \frac{X}{R}$ ($\sin \varphi = \frac{X}{Z}$ and $\cos \varphi = \frac{R}{Z}$).

$\Rightarrow \bar{Z} = Z e^{j\varphi}$

- The inverse of the impedance is the admittance $\bar{Y} = \frac{1}{Z}$

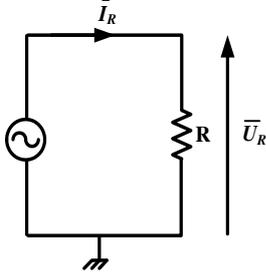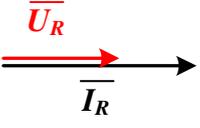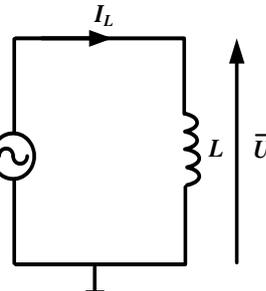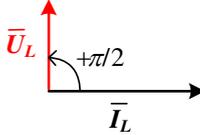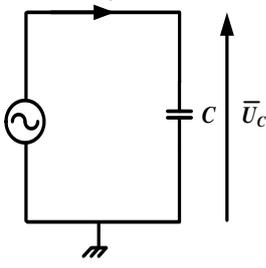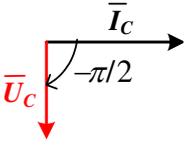Circuits	Instantaneous Expression	complex Expression	vector Diagram
<p><u>R Circuit</u></p> 	$i_R(t) = \sqrt{2}I_R \cos(\omega t)$ $u_R(t) = Ri_R(t)$ $u_R(t) = RI_R \sqrt{2} \cos(\omega t)$	$\bar{I}_R = I_R$ $\bar{U}_R = RI_R$ $= R\bar{I}_R$ $= \bar{Z}_R \bar{I}_R$ $\Rightarrow \bar{Z}_R = R = Ze^{j\varphi}$ $\Rightarrow \begin{cases} Z = R \\ \varphi = 0 \end{cases}$	
<p><u>L Circuit</u></p> 	$i_L(t) = \sqrt{2}I_L \cos(\omega t)$ $u_L(t) = L \frac{di_L(t)}{dt}$ $u_L(t) = L\omega I_L \sqrt{2} \cos(\omega t + \frac{\pi}{2})$ $= -L\omega I_L \sqrt{2} \sin(\omega t)$	$\bar{I}_L = I_L$ $\bar{U}_L = jL\omega \bar{I}_L$ $= \bar{Z}_L \bar{I}_L$ $\Rightarrow \bar{Z}_L = jL\omega = Ze^{j\varphi}$ $\Rightarrow \begin{cases} Z = L\omega \\ \varphi = \pi/2 \end{cases}$	
<p><u>C Circuit</u></p> 	$i_C(t) = \sqrt{2}I_C \cos(\omega t)$ $u_C(t) = \frac{1}{C} \int i_C(t) dt$ $u_C(t) = \frac{\sqrt{2}I_C}{C\omega} \cos(\omega t - \frac{\pi}{2})$ $= \frac{\sqrt{2}I_C}{C\omega} \sin(\omega t)$	$\bar{I}_C = I_C$ $\bar{U}_C = \frac{\bar{I}_C}{jC\omega} = -j \frac{\bar{I}_C}{C\omega}$ $\bar{U}_C = \bar{Z}_C \bar{I}_C$ $\Rightarrow \bar{Z}_C = \frac{1}{jC\omega}$ $= -j \frac{1}{C\omega}$ $\Rightarrow \begin{cases} Z = \frac{1}{C\omega} \\ \varphi = -\pi/2 \end{cases}$	

3. Power measurements

The instantaneous power p supplied by a voltage source u providing a current i is:

$$p = ui$$

- ◆ The active power P (or simply power), is defined as the mean value of the instantaneous power:

$$P = \frac{1}{T} \int_0^T p \cdot dt = \frac{1}{T} \int_0^T ui \cdot dt, \quad T: \text{period}$$

In the sinusoidal regime:

$$\begin{cases} u(t) = \sqrt{2}U \cos(\omega t + \varphi) \\ i(t) = \sqrt{2}I \cos(\omega t) \end{cases},$$

We can write:

$$P = \frac{1}{T} \int_0^T p \cdot dt = UI \cos \varphi \text{ (Watt : W)}$$

- ◆ The reactive power Q is defined by the following expression :

$$Q = UI \sin \varphi \text{ (VAr : Volt-Ampere reactive)}$$

- ◆ The Volt-Amperes (S), a scalar quantity, is the product of the magnitudes the voltage and the current:

$$S = UI \text{ (en VA : Volt-Ampere)}$$

- ◆ We define the complexe power \bar{S} by :



$$\bar{S} = \bar{U} \cdot \bar{I}^*, \quad \bar{I}^* : \text{conjugate of } \bar{I} ;$$


$$\Rightarrow \bar{S} = P + jQ$$

- ◆ We call power factor, the quotient of P by S :

$$F = \frac{P}{S} = \cos \varphi$$

The following table shows the active, reactive and apparent powers of the circuits R,L and C :

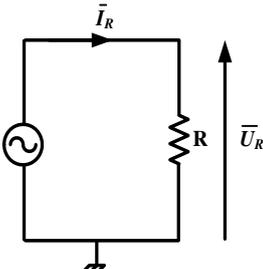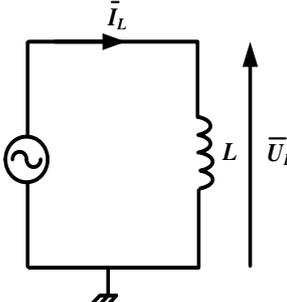Circuits	Power : $\bar{S} / S / P / Q$
<p><u>R Circuit</u></p> 	$\bar{S}_R = \bar{U}_R \cdot \bar{I}_R^* = R \bar{I}_R \cdot \bar{I}_R^* = R I_R^2$ <p>Or, $\bar{S}_R = P_R + jQ_R$</p> $\Rightarrow \begin{cases} P_R = R I_R^2 = \frac{U_R^2}{R} \\ Q_R = 0 \end{cases}$
<p><u>L Circuit</u></p> 	$\bar{S}_L = \bar{U}_L \cdot \bar{I}_L^* = jL\omega \bar{I}_L \cdot \bar{I}_L^* = jL\omega I_L^2$ <p>Or, $\bar{S}_L = P_L + jQ_L$</p> $\Rightarrow \begin{cases} P_L = 0 \\ Q_L = L\omega I_L^2 = \frac{U_L^2}{L\omega} \end{cases}$

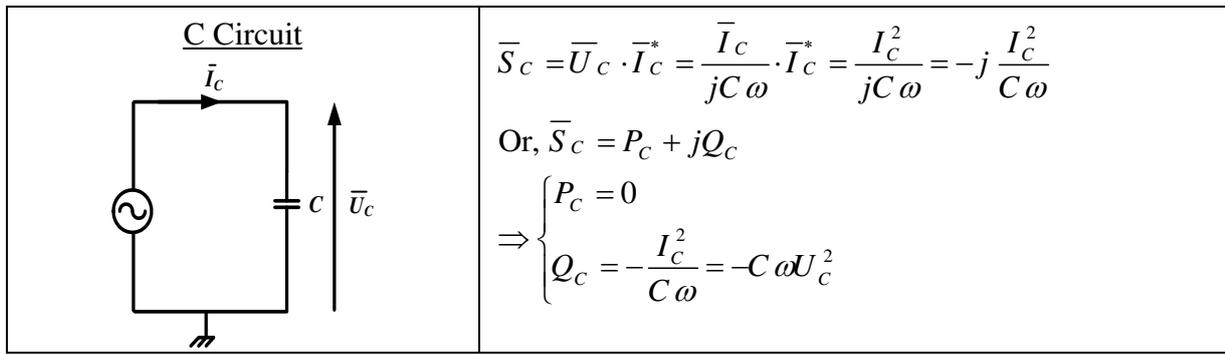

3. Improvement of power factor

We consider a load \bar{Z} that consume an active power P and a reactive power Q with a power factor $\cos \varphi$. We want to improve $\cos \varphi$ ($\cos \varphi \rightarrow 1$) by adding a capacitance in parallel with the load \bar{Z} (Fig 1.3).

The circuit consumes then a reactive power Q' under a new power factor $\cos \varphi'$.

Before adding C :

We have :

$$\begin{cases} P \\ Q = P \cdot \operatorname{tg} \varphi \end{cases}$$

After adding C :

The added capacitor produces only reactive power Q_c , so we obtain :

$$\begin{cases} P' = P \\ Q' = Q + Q_c = P \cdot \operatorname{tg} \varphi + Q_c = P' \cdot \operatorname{tg} \varphi' = P \cdot \operatorname{tg} \varphi' \\ \Rightarrow Q_c = P(\operatorname{tg} \varphi' - \operatorname{tg} \varphi) \end{cases} \Rightarrow C = \frac{-P(\operatorname{tg} \varphi' - \operatorname{tg} \varphi)}{\omega U_c^2}$$

we have also: $Q_c = -\frac{I_c^2}{C\omega} = -C\omega U_c^2$

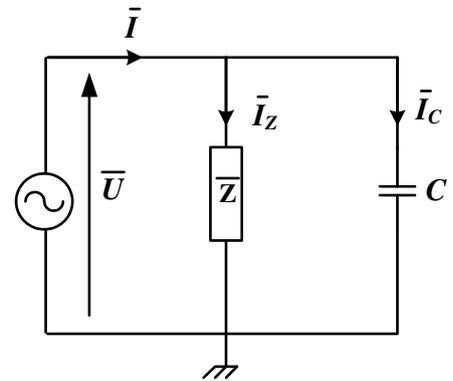


Fig 1.3