



ELEE 250/ Electric Circuits II

Final Exam/ Summer 2020

120 Minutes Date: 19/07/2020


Student's Name:

Student's ID:

Problem #1: A balanced three-phase Δ -connection generator with positive sequence has impedance $0.6 + j1.5 \Omega$ feeds a balanced three-phase Δ -connected load with an impedance $117 + j84 \Omega$ through connected lines that have impedances of $0.8 + j1.5 \Omega$. The internal voltage is $120\sqrt{3}\angle 30^\circ$ V.

- Construct a single-phase equivalent circuit of the three-phase system.
- Obtain the phase currents I_{AB} , I_{BC} and I_{CA}
- Calculate the line currents I_{aA} , I_{bB} and I_{cC} .
- Find the phase voltages at load terminals (V_{AB} , V_{BC} and V_{CA}).
- Determine the line voltages.
- Determine phase voltages at the terminals of generator (V'_{ab} , V'_{bc} and V'_{ca}).
- Find the average power delivered to load.
- Calculate the total average power at load.
- Find the total power lost at line.
- Find the total power lost at generator.
- Determine the total reactive power (Q) absorbed by load.
- Calculate the total complex power (S) delivered by source.

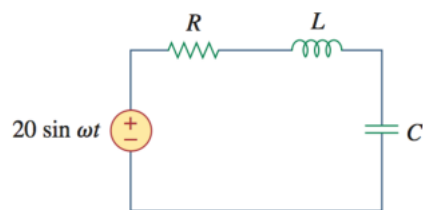Problem #2: For the following circuit, $R = 10 \Omega$, $L = 5 \text{ mH}$, and $C = 2 \mu\text{F}$.




- Find the resonant frequency and the half-power frequencies.
- Calculate the quality factor and bandwidth.
- Determine the amplitude of the current at ω_0 , ω_1 , and ω_2 .

Instructor: M Alsharari




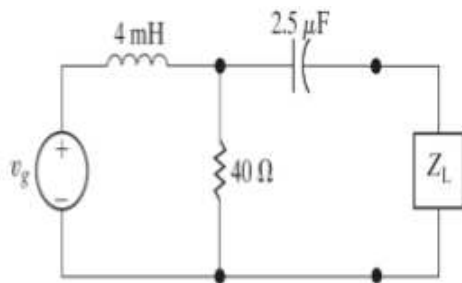Problem #3: For the entire circuit,


- If $\omega = 10 \text{ krad/sec}$, obtain the load impedance.
- By assuming the $v_g(t) = 120 \sin(10,000t + 90^\circ) \text{ V}$, find the maximum average power delivered to the load.



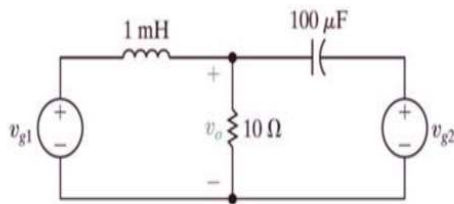Problem #4: Find the steady state expression for $v_o(t)$ in the circuit shown below by using nodal analysis if $v_{g1} = 20 \sin(2000t + 53.14^\circ) \text{ V}$ and $v_{g2} = 50 \cos(2000t - 106.26^\circ) \text{ V}$.



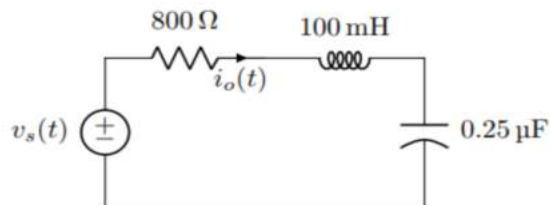Problem #5: Find the steady state expression for $i_o(t)$ in the circuit. If $v_s = 500 \sin(4000t) \text{ mV}$.



Instructor: M Alsharari

Good Luck