

**UNIT 8**

**FIELD-EFFECT TRANSISTORS (FETs)**

1875

## 8-1 ■ THE JUNCTION FIELD-EFFECT TRANSISTOR (JFET)


The junction field-effect transistor (JFET) is a type of FET that operates with a reverse-biased junction to control current in a channel. Depending on their structure, JFETs fall into either of two categories, *n* channel or *p* channel.

After completing this section, you should be able to

- Explain the operation of JFETs
  - Identify the three terminals of a JFET
  - Explain what a channel is
  - Describe the structural difference between an *n*-channel JFET and a *p*-channel JFET
  - Discuss how voltage controls the current in a JFET.
  - Identify the symbols for *n*-channel and *p*-channel JFETs

Figure 8-1(a) shows the basic structure of an *n*-channel junction field-effect transistor (JFET). Wire leads are connected to each end of the *n*-channel; the drain is at the upper end, and the source is at the lower end. Two *p*-type regions are diffused in the *n*-type material to form a channel, and both *p*-type regions are connected to the gate lead. For simplicity, the gate lead is shown connected to only one of the *p* regions. A *p*-channel JFET is shown in Figure 8-1(b).

FIGURE 8-1  
A representation of the basic structure of the two types of JFET.

 



## Basic Operation

To illustrate the operation of a JFET, Figure 8-2 shows bias voltages applied to an *n*-channel device.  $V_{DD}$  provides a drain-to-source voltage and supplies current from drain to source.  $V_{GG}$  sets the reverse-bias voltage between the gate and the source, as shown.


The JFET is always operated with the gate-source *pn* junction reverse-biased. Reverse-biasing of the gate-source junction with a negative gate voltage produces a depletion region along the *pn* junction, which extends into the *n* channel and thus increases its resistance by restricting the channel width.

The channel width can be controlled by varying the gate voltage, whereby the amount of drain current,  $I_D$ , can also be controlled. Figure 8-3 illustrates this concept. The white areas represent the depletion region created by the reverse bias. It is wider


FIGURE 8-2  
A biased n-channel JFET.

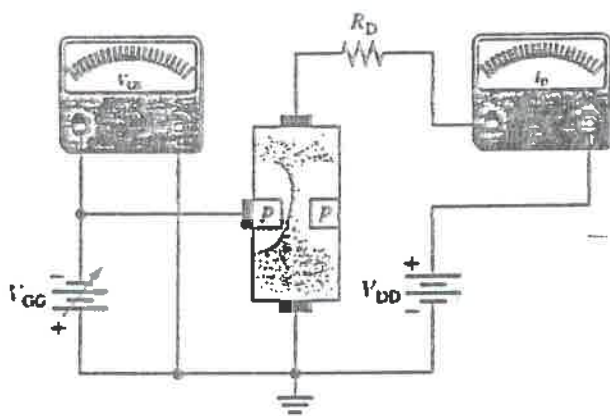 

(a) JFET biased for conduction

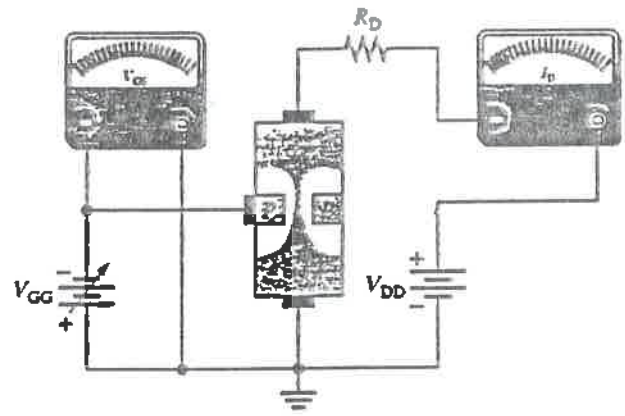

 (b) Greater  $V_{GS}$  narrows the channel and decreases  $I_D$ .



(c) Less  $V_{GS}$  widens the channel and increases  $I_D$ .


FIGURE 8-3  
Effects of  $V_{GS}$  on channel width and on drain current ( $V_{GS} = V_{GG}$ ).

toward the drain end of the channel because the reverse-bias voltage between the gate and the drain is greater than that between the gate and the source. We will discuss JFET characteristic curves and some important parameters in Section 8-2.

### JFET Symbols

The schematic symbols for both  $n$ -channel and  $p$ -channel JFETs are shown in Figure 8-4. Notice that the arrow on the gate points "in" for  $n$  channel and "out" for  $p$  channel.

FIGURE 8-4  
JFET schematic symbols.

 

### SECTION 8-1 REVIEW

1. Name the three terminals of a JFET.
2. Does an  $n$ -channel JFET require a positive or negative value for  $V_{GS}$ ?
3. How is the drain current controlled in a JFET?

### 8-2 ■ JFET CHARACTERISTICS AND PARAMETERS

*In this section, you will see how the JFET operates as a voltage-controlled, constant-current device. You will also learn about cutoff and pinch-off as well as JFET transfer characteristics.*

*After completing this section, you should be able to*

- Define, discuss, and apply important JFET parameters
  - Explain ohmic region, constant-current region, and breakdown
  - Define *pinch-off voltage*
  - Describe how gate-to-source voltage controls the drain current
  - Define *cutoff voltage*
  - Compare pinch-off and cutoff
  - Analyze a JFET transfer characteristic curve
  - Use the equation for the transfer characteristic to calculate  $I_D$
  - Use a JFET data sheet
  - Define *transconductance*
  - Explain and determine input resistance and capacitance
  - Determine drain-to-source resistance

First, let's consider the case where the gate-to-source voltage is zero ( $V_{GS} = 0$  V). This is produced by shorting the gate to the source, as in Figure 8-5(a) where both are grounded. As  $V_{DD}$  (and thus  $V_{DS}$ ) is increased from zero,  $I_D$  will increase proportionally through the  $n$ -type material, as shown in the graph of Figure 8-5(b) between points  $A$  and  $B$ . In this region, the channel resistance is essentially constant because the depletion region is not large enough to have significant effect. This is called the *ohmic region* because  $V_{DS}$  and  $I_D$  are related by Ohm's law.

 


FIGURE 8-5  
The drain characteristic curve of a JFET for  $V_{GS} = 0$  showing pinch-off.

At point  $B$  in Figure 8-5(b), the curve levels off and  $I_D$  becomes essentially constant. As  $V_{DS}$  increases from point  $B$  to point  $C$ , the reverse-bias voltage from gate to drain ( $V_{GD}$ ) produces a depletion region large enough to offset the increase in  $V_{DS}$ , thus keeping  $I_D$  relatively constant.

### Pinch-Off Voltage

For  $V_{GS} = 0$  V, the value of  $V_{DS}$  at which  $I_D$  becomes essentially constant (point  $B$  on the curve in Figure 8-5(b)) is the pinch-off voltage,  $V_p$ . For a given JFET,  $V_p$  has a fixed value. As you can see, a continued increase in  $V_{DS}$  above the pinch-off voltage produces an almost constant drain current. This value of drain current is  $I_{DSS}$  (Drain to Source current with gate Shorted) and is always specified on JFET data sheets.  $I_{DSS}$  is the *maximum* drain current that a specific JFET can produce regardless of the external circuit, and it is always specified for the condition,  $V_{GS} = 0$  V.

As shown in the graph in Figure 8-5(b), *breakdown* occurs at point  $C$  when  $I_D$  begins to increase very rapidly with any further increase in  $V_{DS}$ . Breakdown can result in irreversible damage to the device, so JFETs are always operated below breakdown and

 


FIGURE 8-6  
JFET action that produces the characteristic curve for  $V_{GS} = 0$  V.

within the *constant-current region* (between points B and C on the graph). The JFET action that produces the drain characteristic curve to the point of breakdown for  $V_{GS} = 0$  V is illustrated in Figure 8-6.

### $V_{GS}$ Controls $I_D$

Now, let's connect a bias voltage,  $V_{GG}$ , from gate to source as shown in Figure 8-7(a). As  $V_{GS}$  is set to increasingly more negative values by adjusting  $V_{GG}$ , a family of drain characteristic curves is produced, as shown in Figure 8-7(b). Notice that  $I_D$  decreases as the magnitude of  $V_{GS}$  is increased to larger negative values because of the narrowing of the channel. Also notice that, for each increase in  $V_{GS}$ , the JFET reaches pinch-off (where constant current begins) at values of  $V_{DS}$  less than  $V_P$ . So, the amount of drain current is controlled by  $V_{GS}$ , as illustrated in Figure 8-8.

 


FIGURE 8-7  
Pinch-off occurs at a lower  $V_{DS}$  as  $V_{GS}$  is increased to more negative values.

 


FIGURE 8-8  
 $V_{GS}$  controls  $I_D$ .

### Cutoff Voltage

The value of  $V_{GS}$  that makes  $I_D$  approximately zero is the cutoff voltage,  $V_{GS(off)}$ . The JFET must be operated between  $V_{GS} = 0$  V and  $V_{GS(off)}$ . For this range of gate-to-source voltages,  $I_D$  will vary from a maximum of  $I_{DSS}$  to a minimum of almost zero.

As you have seen, for an  $n$ -channel JFET, the more negative  $V_{GS}$  is, the smaller  $I_D$  becomes in the constant-current region. When  $V_{GS}$  has a sufficiently large negative value,  $I_D$  is reduced to zero. This cutoff effect is caused by the widening of the depletion region to a point where it completely closes the channel as shown in Figure 8-9.

The basic operation of a  $p$ -channel JFET is the same as for an  $n$ -channel device except that a  $p$ -channel JFET requires a negative  $V_{DD}$  and a positive  $V_{GS}$ , as illustrated in Figure 8-10.

 


FIGURE 8-9  
JFET at cutoff.

 


FIGURE 8-10  
A biased  $p$ -channel JFET.

### Comparison of Pinch-Off and Cutoff


As you have seen, there is definitely a difference between pinch-off and cutoff. There is also a connection.  $V_P$  is the value of  $V_{DS}$  at which the drain current becomes constant and is always measured at  $V_{GS} = 0$  V. However, pinch-off occurs for  $V_{DS}$  values less than  $V_P$  when  $V_{GS}$  is nonzero. So, although  $V_P$  is a constant, the minimum value of  $V_{DS}$  at which  $I_D$  becomes constant varies with  $V_{GS}$ .

$V_{GS(off)}$  and  $V_P$  are always equal in magnitude but opposite in sign. A data sheet usually will give either  $V_{GS(off)}$  or  $V_P$ , but not both. However, when you know one, you have the other. For example, if  $V_{GS(off)} = -5$  V, then  $V_P = +5$  V.

#### EXAMPLE 8-1

For the JFET in Figure 8-11,  $V_{GS(off)} = -4$  V and  $I_{DSS} = 12$  mA. Determine the *minimum* value of  $V_{DD}$  required to put the device in the constant-current region of operation.

FIGURE 8-11

 

**Solution** Since  $V_{GS(\text{off})} = -4 \text{ V}$ ,  $V_P = 4 \text{ V}$ . The minimum value of  $V_{DS}$  for the JFET to be in its constant-current region is

$$V_{DS} = V_P = 4 \text{ V}$$

In the constant-current region with  $V_{GS} = 0 \text{ V}$ ,

$$I_D = I_{DSS} = 12 \text{ mA}$$

The drop across the drain resistor is

$$V_{RD} = I_D R_D = (12 \text{ mA})(560 \Omega) = 6.72 \text{ V}$$

Apply Kirchhoff's law around the drain circuit.

$$V_{DD} = V_{DS} + V_{RD} = 4 \text{ V} + 6.72 \text{ V} = 10.7 \text{ V}$$

This is the value of  $V_{DD}$  to make  $V_{DS} = V_P$  and put the device in the constant-current region.

**Related Exercise** If  $V_{DD}$  is increased to 15 V, what is the drain current?

**EXAMPLE 8-2**

A particular  $p$ -channel JFET has a  $V_{GS(\text{off})} = +4 \text{ V}$ . What is  $I_D$  when  $V_{GS} = +6 \text{ V}$ ?

**Solution** The  $p$ -channel JFET requires a positive gate-to-source voltage. The more positive the voltage, the less the drain current. When  $V_{GS} = 4 \text{ V}$ ,  $I_D$  is 0. Any further increase in  $V_{GS}$  keeps the JFET cut off, so  $I_D$  remains 0.

**Related Exercise** What is  $V_P$  for the JFET described in this example?


**JFET Transfer Characteristic**

You have learned that a range of  $V_{GS}$  values from zero to  $V_{GS(\text{off})}$  controls the amount of drain current. For an  $n$ -channel JFET,  $V_{GS(\text{off})}$  is negative, and for a  $p$ -channel JFET,  $V_{GS(\text{off})}$  is positive. Because  $V_{GS}$  does control  $I_D$ , the relationship between these two quantities is very important. Figure 8-12 is a typical transfer characteristic curve that illustrates graphically the relationship between  $V_{GS}$  and  $I_D$ .

Notice that the bottom end of the curve is at a point on the  $V_{GS}$  axis equal to  $V_{GS(\text{off})}$ , and the top end of the curve is at a point on the  $I_D$  axis equal to  $I_{DSS}$ . This curve, of course, shows that the operating limits of a JFET are

$$I_D = 0 \quad \text{when} \quad V_{GS} = V_{GS(\text{off})}$$

FIGURE 8-12  
JFET transfer characteristic curve  
(n-channel).

 

and

$$I_D = I_{DSS} \text{ when } V_{GS} = 0$$

The transfer characteristic curve can be developed from the drain characteristic curves by plotting values of  $I_D$  for the values of  $V_{GS}$  taken from the family of drain curves in the pinch-off region, as illustrated in Figure 8-13 for a specific set of curves. Each point on the transfer characteristic curve corresponds to specific values of  $V_{GS}$  and  $I_D$  on the drain curves. For example, when  $V_{GS} = -2$  V,  $I_D = 4.32$  mA. Also, for this specific JFET,  $V_{GS(off)} = -5$  V and  $I_{DSS} = 12$  mA.

A JFET transfer characteristic curve is nearly parabolic in shape and can therefore be expressed approximately as

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 \tag{8-1}$$


 


FIGURE 8-13  
Example of the development of an n-channel JFET transfer characteristic curve (left) from the JFET drain characteristic curves (right).

With Equation (8-1),  $I_D$  can be determined for any  $V_{GS}$  if  $V_{GS(off)}$  and  $I_{DSS}$  are known. These quantities are usually available from the data sheet for a given JFET. Notice the squared term in the equation. Because of its form, a parabolic relationship is known as a *square law*, and therefore, JFETs and MOSFETs are often referred to as *square-law devices*.

The data sheet for a typical JFET series is shown in Figure 8-14.

FIGURE 8-14  
JFET data sheet.

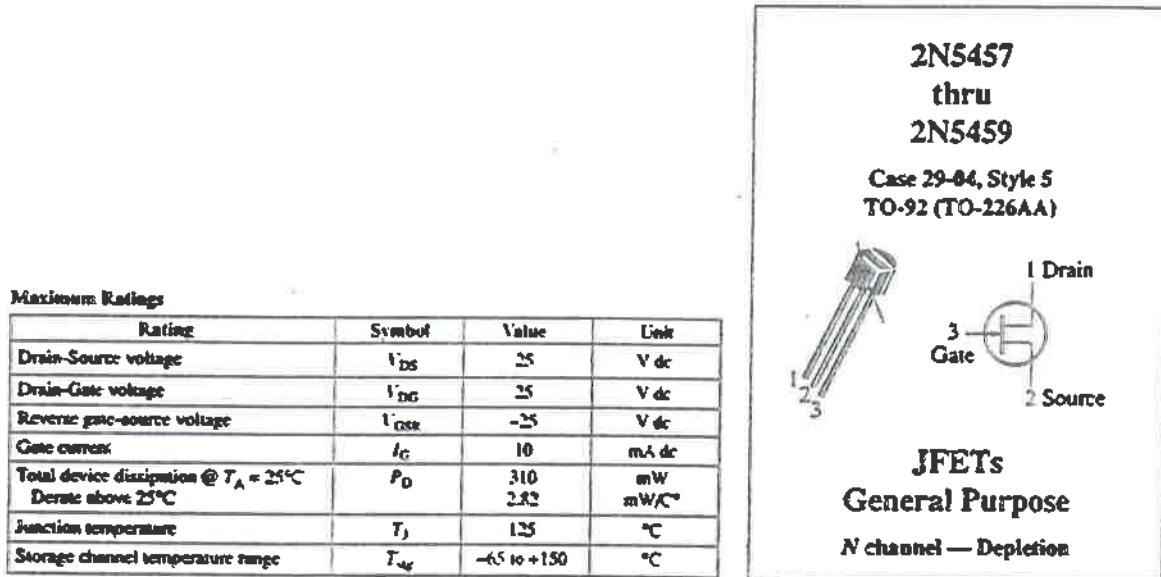

Electrical Characteristics ( $T_A = 25^\circ\text{C}$  unless otherwise noted.)

Characteristic	Symbol	Min	Typ	Max	Unit
----------------	--------	-----	-----	-----	------

OFF Characteristics

Gate-Source breakdown voltage ( $I_G = -10 \mu\text{A}$ dc, $V_{DS} = 0$ )	$V_{(BR)GS}$	-25	-	-	V dc
Gate reverse current ( $V_{GS} = -15$ V dc, $V_{DS} = 0$ ) ( $V_{GS} = -15$ V dc, $V_{DS} = 0$ , $T_A = 100^\circ\text{C}$ )	$I_{GSR}$	-	-	-1.0 -200	nA dc
Gate-Source cutoff voltage ( $V_{DS} = 15$ V dc, $I_D = 10$ nA dc)	$V_{GS(off)}$	-0.5 -1.0 -2.0	-	-6.0 -7.0 -8.0	V dc
Gate-Source voltage ( $V_{DS} = 15$ V dc, $I_D = 100 \mu\text{A}$ dc) ( $V_{DS} = 15$ V dc, $I_D = 200 \mu\text{A}$ dc) ( $V_{DS} = 15$ V dc, $I_D = 400 \mu\text{A}$ dc)	$V_{GS}$	-	-2.5 -3.5 -4.5	-	V dc

ON Characteristics

Zero-Gate-Voltage drain current ( $V_{DS} = 15$ V dc, $V_{GS} = 0$ )	$I_{DSS}$	1.0 2.0 4.0	3.0 6.0 9.0	5.0 9.0 16	mA dc
---	-----------	-------------------	-------------------	------------------	-------

Small-signal Characteristics

Forward transfer admittance common source ( $V_{DS} = 15$ V dc, $V_{GS} = 0$ , $f = 1.0$ kHz)	$ y_{fs} $	1000 1500 2000	-	5000 5500 6000	$\mu\text{mhos}$ or $\mu\text{S}$
Output admittance common source ( $V_{DS} = 15$ V dc, $V_{GS} = 0$ , $f = 1.0$ kHz)	$ y_{os} $	-	10	50	$\mu\text{mhos}$ or $\mu\text{S}$
Input capacitance ( $V_{DS} = 15$ V dc, $V_{GS} = 0$ , $f = 1.0$ MHz)	$C_{iss}$	-	4.5	7.0	pF
Reverse transfer capacitance ( $V_{DS} = 15$ V dc, $V_{GS} = 0$ , $f = 1.0$ MHz)	$C_{rss}$	-	1.5	3.0	pF

**EXAMPLE 8-3**

The data sheet in Figure 8-14 for a 2N5459 JFET indicates that typically  $I_{DSS} = 9 \text{ mA}$  and  $V_{GS(off)} = -8 \text{ V}$  (maximum). Determine the drain current for  $V_{GS} = 0 \text{ V}$ ,  $-1 \text{ V}$ , and  $-4 \text{ V}$ .

**Solution** For  $V_{GS} = 0 \text{ V}$ ,  $I_D = I_{DSS} = 9 \text{ mA}$ . For  $V_{GS} = -1 \text{ V}$ , use Equation (8-1).

$$\begin{aligned} I_D &= I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = (9 \text{ mA}) \left( 1 - \frac{-1 \text{ V}}{-8 \text{ V}} \right)^2 \\ &= (9 \text{ mA})(1 - 0.125)^2 = (9 \text{ mA})(0.766) = 6.89 \text{ mA} \end{aligned}$$

For  $V_{GS} = -4 \text{ V}$ :

$$I_D = (9 \text{ mA}) \left( 1 - \frac{-4 \text{ V}}{-8 \text{ V}} \right)^2 = (9 \text{ mA})(1 - 0.5)^2 = (9 \text{ mA})(0.25) = 2.25 \text{ mA}$$

**Related Exercise** Determine  $I_D$  for  $V_{GS} = -3 \text{ V}$  for the 2N5459 JFET.

**JFET Forward Transconductance**

The forward transfer conductance (transconductance),  $g_m$ , is the change in drain current ( $\Delta I_D$ ) for a given change in gate-to-source voltage ( $\Delta V_{GS}$ ) with the drain-to-source voltage constant. It is expressed as a ratio and has the unit of siemens (S).

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

Other common designations for this parameter are  $g_{fs}$  and  $y_{fs}$  (forward transfer admittance). As you will see in Chapter 9,  $g_m$  is important in FET amplifiers as a major factor in determining the voltage gain.

Because the transfer characteristic curve for a JFET is nonlinear,  $g_m$  varies in value depending on the location on the curve as set by  $V_{GS}$ . The value for  $g_m$  is greater near the top of the curve (near  $V_{GS} = 0$ ) than it is near the bottom (near  $V_{GS(off)}$ ), as illustrated in Figure 8-15. A data sheet normally gives the value of  $g_m$  measured at  $V_{GS} = 0 \text{ V}$  ( $g_{m0}$ ). For example, the data sheet for the 2N5457 JFET specifies a minimum  $g_{m0}$  ( $y_{fs}$ ) of  $1000 \mu\text{S}$  with  $V_{DS} = 15 \text{ V}$ .

Given  $g_{m0}$ , you can calculate an approximate value for  $g_m$  at any point on the transfer characteristic curve using the following formula:

$$g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right) \quad (8-2)$$

When a value of  $g_{m0}$  is not available, you can calculate it using values of  $I_{DSS}$  and  $V_{GS(off)}$ . The vertical lines indicate an absolute value (no sign).

$$g_{m0} = \frac{2I_{DSS}}{|V_{GS(off)}|} \quad (8-3)$$

 


FIGURE 8-15  
 $g_m$  varies depending on the bias point ( $V_{GS}$ ).

#### EXAMPLE 8-4

The following information is included on the data sheet in Figure 8-14 for a 2N5457 JFET: typically,  $I_{DSS} = 3.0 \text{ mA}$ ,  $V_{GS(off)} = -6 \text{ V}$  maximum, and  $y_{fs(max)} = 5000 \text{ } \mu\text{S}$ . Determine the forward transconductance for  $V_{GS} = -4 \text{ V}$ , and find  $I_D$  at this point.

**Solution**  $g_{m0} = y_{fs} = 5000 \text{ } \mu\text{S}$ . Use Equation (8-2) to calculate  $g_m$ .

$$g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right) = (5000 \text{ } \mu\text{S}) \left( 1 - \frac{-4 \text{ V}}{-6 \text{ V}} \right) = 1667 \text{ } \mu\text{S}$$

Next, use Equation (8-1) to calculate  $I_D$  at  $V_{GS} = -4 \text{ V}$ .

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = (3.0 \text{ mA}) \left( 1 - \frac{-4 \text{ V}}{-6 \text{ V}} \right)^2 = 333 \text{ } \mu\text{A}$$

**Related Exercise** A given JFET has the following characteristics:  $I_{DSS} = 12 \text{ mA}$ ,  $V_{GS(off)} = -5 \text{ V}$ , and  $g_{m0} = 3000 \text{ } \mu\text{S}$ . Find  $g_m$  and  $I_D$  when  $V_{GS} = -2 \text{ V}$ .

#### Input Resistance and Capacitance

A JFET operates with its gate-source junction reverse-biased. Therefore, the input resistance at the gate is very high. This high input resistance is one advantage of the JFET over the bipolar transistor. (Recall that a bipolar transistor operates with a forward-biased base-emitter junction.) JFET data sheets often specify the input resistance by giving a

value for the gate reverse current  $I_{GSS}$  at a certain gate-to-source voltage. The input resistance can then be determined using the following equation:

$$R_{IN} = \left| \frac{V_{GS}}{I_{GSS}} \right| \quad (8-4)$$

For example, the 2N5457 data sheet in Figure 8-14 lists a maximum  $I_{GSS}$  of 1 nA for  $V_{GS} = -15$  V at 25°C.  $I_{GSS}$  increases with temperature, so the input resistance decreases.

The input capacitance,  $C_{iss}$ , is a result of the JFET operating with a reverse-biased *pn* junction. Recall that a reverse-biased *pn* junction acts as a capacitor whose capacitance depends on the amount of reverse voltage. For example, the 2N5457 has a maximum  $C_{iss}$  of 7 pF for  $V_{GS} = 0$ .

**EXAMPLE 8-5**

A certain JFET has an  $I_{GSS}$  of 2 nA for  $V_{GS} = -20$  V. Determine the input resistance.

*Solution*

$$R_{IN} = \left| \frac{V_{GS}}{I_{GSS}} \right| = \frac{20 \text{ V}}{2 \text{ nA}} = 10,000 \text{ M}\Omega$$

*Related Exercise* Determine the minimum input resistance for the 2N5458 from the data sheet in Figure 8-14.

**Drain-to-Source Resistance**

You learned from the drain characteristic curve that, above pinch-off, the drain current is relatively constant over a range of drain-to-source voltages. Therefore, a large change in  $V_{DS}$  produces only a very small change in  $I_D$ . The ratio of these changes is the drain-to-source resistance of the device,  $r'_{ds}$ .

$$r'_{ds} = \frac{\Delta V_{DS}}{\Delta I_D}$$

Data sheets often specify this parameter as output conductance,  $g_{os}$ , or output admittance,  $y_{os}$ .

**SECTION 8-2  
REVIEW**

1. The drain-to-source voltage at the pinch-off point of a particular JFET is 7 V. If the gate-to-source voltage is zero, what is  $V_P$ ?
2. The  $V_{GS}$  of a certain *n*-channel JFET is increased negatively. Does the drain current increase or decrease?
3. What value must  $V_{GS}$  have to produce cutoff in a *p*-channel JFET with a  $V_P = -3$  V?

## 8-3 ■ JFET BIASING

Using some of the FET parameters discussed in the previous sections, we will now see how to dc-bias JFETs. The purpose of biasing is to select the proper dc gate-to-source voltage to establish a desired value of drain current and, thus, a proper Q-point. You will learn about two major types of bias circuits, self-bias and voltage-divider bias.

After completing this section, you should be able to

- Discuss and analyze JFET bias circuits
  - Describe self-bias
  - Analyze a self-biased JFET circuit
  - Set the self-biased Q-point
  - Analyze a voltage-divider-biased JFET circuit
  - Use transfer characteristic curves to analyze JFET bias circuits
  - Discuss Q-point stability

## Self-Bias

Recall that a JFET must be operated such that the gate-source junction is always reverse-biased. This condition requires a negative  $V_{GS}$  for an  $n$ -channel JFET and a positive  $V_{GS}$  for a  $p$ -channel JFET. This can be achieved using the self-bias arrangements shown in Figure 8-16. The gate resistor,  $R_G$ , does not affect the bias because it has essentially no voltage drop across it; and therefore the gate remains at 0 V.  $R_G$  is necessary only to isolate an ac signal from ground in amplifier applications, as you will see later.


For the  $n$ -channel JFET in Figure 8-16(a),  $I_S$  produces a voltage drop across  $R_S$  and makes the source positive with respect to ground. Since  $I_S = I_D$  and  $V_G = 0$ , then  $V_S = I_D R_S$ . The gate-to-source voltage is

$$V_{GS} = V_G - V_S = 0 - I_D R_S$$

so

$$V_{GS} = -I_D R_S \quad (8-5)$$

FIGURE 8-16  
Self-biased JFETs ( $I_S = I_D$  in all FETs).

 

For the  $p$ -channel JFET shown in Figure 8-16(b), the current through  $R_S$  produces a negative voltage at the source and therefore

$$V_{GS} = +I_D R_S \quad (8-6)$$

In the following analysis, the  $n$ -channel JFET in Figure 8-16(a) is used for illustration. Keep in mind that analysis of the  $p$ -channel JFET is the same except for opposite-polarity voltages. The drain voltage with respect to ground is determined as follows:

$$V_D = V_{DD} - I_D R_D$$


Since  $V_S = I_D R_S$ , the drain-to-source voltage is

$$V_{DS} = V_D - V_S = V_{DD} - I_D (R_D + R_S)$$

**EXAMPLE 8-6**

Find  $V_{DS}$  and  $V_{GS}$  in Figure 8-17, given that  $I_D = 5$  mA.

FIGURE 8-17

 **Solution**

$$V_S = I_D R_S = (5 \text{ mA})(470 \Omega) = 2.35 \text{ V}$$

$$V_D = V_{DD} - I_D R_D = 15 \text{ V} - (5 \text{ mA})(1 \text{ k}\Omega) = 15 \text{ V} - 5 \text{ V} = 10 \text{ V}$$

Therefore,

$$V_{DS} = V_D - V_S = 10 \text{ V} - 2.35 \text{ V} = 7.65 \text{ V}$$

Since  $V_G = 0$  V,

$$V_{GS} = V_G - V_S = 0 \text{ V} - 2.35 \text{ V} = -2.35 \text{ V}$$

**Related Exercise** Determine  $V_{DS}$  and  $V_{GS}$  in Figure 8-17 when  $I_D = 8$  mA. Assume that  $R_D = 860 \Omega$ ,  $R_S = 390 \Omega$ , and  $V_{DD} = 12$  V.

### Setting the Q-Point of a Self-Biased JFET

The basic approach to establishing a JFET bias point is to determine  $I_D$  for a desired value of  $V_{GS}$  or vice versa. Then calculate the required value of  $R_S$  using the relationship derived from Equation (8-5) and stated in Equation (8-7). The vertical lines indicate an absolute value.


$$R_S = \left| \frac{V_{GS}}{I_D} \right| \quad (8-7)$$

For a desired value of  $V_{GS}$ ,  $I_D$  can be determined in either of two ways: from the transfer characteristic curve for the particular JFET, or more practically, from Equation (8-1) using  $I_{DSS}$  and  $V_{GS(off)}$  from the JFET data sheet. The next two examples illustrate these procedures.

#### EXAMPLE 8-7

Determine the value of  $R_S$  required to self-bias an  $n$ -channel JFET having the transfer characteristic curve shown in Figure 8-18 at  $V_{GS} = -5$  V.

FIGURE 8-18

 

**Solution** From the graph,  $I_D = 6.25$  mA when  $V_{GS} = -5$  V. Calculate  $R_S$ :

$$R_S = \left| \frac{V_{GS}}{I_D} \right| = \frac{5 \text{ V}}{6.25 \text{ mA}} = 800 \Omega$$

**Related Exercise** Find  $R_S$  for  $V_{GS} = -3$  V.

**EXAMPLE 8-8**

Determine the value of  $R_S$  required to self-bias a  $p$ -channel JFET with  $I_{DSS} = 25$  mA and  $V_{GS(off)} = 15$  V.  $V_{GS}$  is to be 5 V.

**Solution** Use Equation (8-1) to calculate  $I_D$ .

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = (25 \text{ mA}) \left( 1 - \frac{5 \text{ V}}{15 \text{ V}} \right)^2 = (25 \text{ mA})(1 - 0.333)^2 = 11.1 \text{ mA}$$

Now, determine  $R_S$ .

$$R_S = \left| \frac{V_{GS}}{I_D} \right| = \frac{5 \text{ V}}{11.1 \text{ mA}} = 450 \Omega$$

Since 450  $\Omega$  is not a standard value, use a 470  $\Omega$  resistor.

**Related Exercise** Find the value of  $R_S$  required to self-bias a  $p$ -channel JFET with  $I_{DSS} = 18$  mA and  $V_{GS(off)} = 8$  V.  $V_{GS} = 4$  V.

**Midpoint Bias** It is often desirable to bias a JFET near the midpoint of its transfer characteristic curve where  $I_D = I_{DSS}/2$ . Under signal conditions, midpoint bias allows a maximum amount of drain current swing between  $I_{DSS}$  and 0. Using Equation (8-1), it is shown in Appendix B that  $I_D$  is approximately one-half of  $I_{DSS}$  when  $V_{GS} = V_{GS(off)}/3.4$ .

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2 = I_{DSS} \left( 1 - \frac{V_{GS(off)}/3.4}{V_{GS(off)}} \right)^2 = 0.5 I_{DSS}$$


So, by selecting  $V_{GS} = V_{GS(off)}/3.4$ , you get a midpoint bias in terms of  $I_D$ .

To set the drain voltage at midpoint ( $V_D = V_{DD}/2$ ), select a value of  $R_D$  to produce the desired voltage drop. Choose  $R_G$  arbitrarily large to prevent loading on the driving stage in a cascaded amplifier arrangement. Example 8-9 illustrates these concepts.

**EXAMPLE 8-9**

Select resistor values in Figure 8-19 to set up an approximate midpoint bias. The JFET parameters are  $I_{DSS} = 15$  mA and  $V_{GS(off)} = -8$  V.  $V_D$  should be 6 V (one-half of  $V_{DD}$ ).

FIGURE 8-19

 

**Solution** For midpoint bias,

$$I_D \cong \frac{I_{DSS}}{2} = 7.5 \text{ mA}$$

and

$$V_{GS} \cong \frac{V_{GS(off)}}{3.4} = \frac{-8 \text{ V}}{3.4} = -2.35 \text{ V}$$

Then

$$R_S = \left| \frac{V_{GS}}{I_D} \right| = \frac{2.35 \text{ V}}{7.5 \text{ mA}} = 313 \Omega$$

$$V_D = V_{DD} - I_D R_D$$

$$I_D R_D = V_{DD} - V_D$$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{12 \text{ V} - 6 \text{ V}}{7.5 \text{ mA}} = 800 \Omega$$

Use the nearest standard values of 330  $\Omega$  and 820  $\Omega$ .

**Related Exercise** Select resistor values in Figure 8-19 to set up an approximate midpoint bias. The JFET parameters are  $I_{DSS} = 10 \text{ mA}$  and  $V_{GS(off)} = -10 \text{ V}$ .  $V_{DD} = 15 \text{ V}$ .

### Graphical Analysis of a Self-Biased JFET

You can use the transfer characteristic curve of a JFET and certain parameters to determine the Q-point ( $I_D$  and  $V_{GS}$ ) of a self-biased circuit. A circuit is shown in Figure 8-20(a), and a transfer characteristic curve is shown in Figure 8-20(b). If a curve is not available from the data sheet, you can plot it from Equation (8-1) using data sheet values for  $I_{DSS}$  and  $V_{GS(off)}$ .

To determine the Q-point of the circuit in Figure 8-20(a), a self-bias dc load line is established as follows. First, calculate  $V_{GS}$  when  $I_D$  is zero.

$$V_{GS} = -I_D R_S = (0)(470 \Omega) = 0 \text{ V}$$

This establishes a point at the origin on the graph ( $I_D = 0$ ,  $V_{GS} = 0$ ). Next, get  $I_{DSS}$  from the data sheet and calculate  $V_{GS}$  when  $I_D = I_{DSS}$ . From the curve,  $I_{DSS} = 10 \text{ mA}$  for the JFET in Figure 8-20.

$$V_{GS} = -I_D R_S = -(10 \text{ mA})(470 \Omega) = -4.7 \text{ V}$$

This establishes a second point on the graph ( $I_D = 10 \text{ mA}$ ,  $V_{GS} = -4.7 \text{ V}$ ). Now, with two points, the load line can be drawn on the graph of the transfer characteristic curve as shown in Figure 8-21. The point where the line intersects the transfer characteristic curve is the Q-point of the circuit.


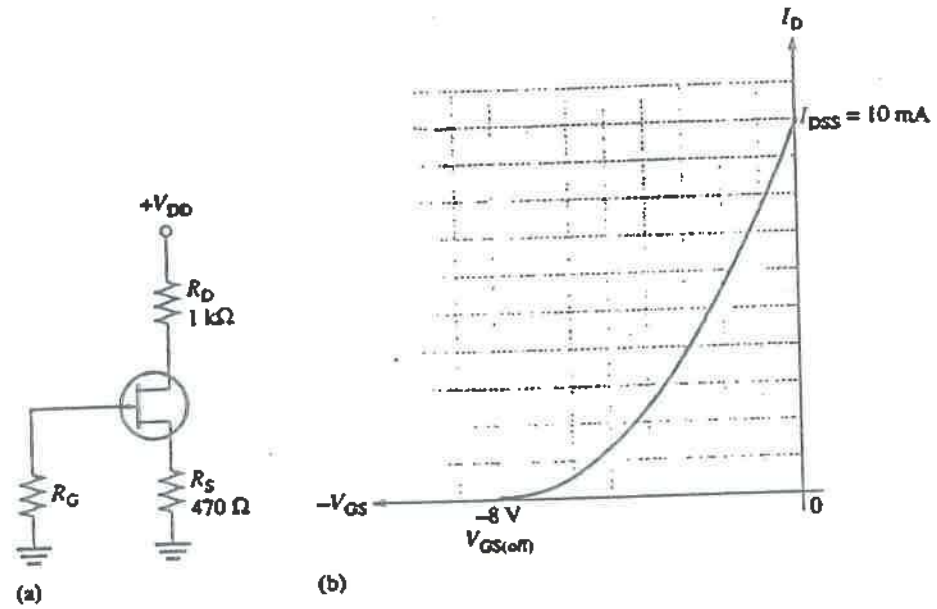


FIGURE 8-20  
A self-biased JFET and its transfer characteristic curve.

FIGURE 8-21  
The intersection of the self-bias dc load line and the transfer characteristic curve is the Q-point.

 

**EXAMPLE 8-10**

Determine the Q-point for the JFET circuit in Figure 8-22(a). The transfer characteristic curve is given in Figure 8-22(b).

**Solution** For  $I_D = 0$ ,

$$V_{GS} = -I_D R_S = (0)(680 \Omega) = 0 \text{ V}$$

This gives a point at the origin. From the curve,  $I_{DSS} = 4 \text{ mA}$ . So for  $I_D = I_{DSS} = 4 \text{ mA}$ ,

$$V_{GS} = -I_D R_S = -(4 \text{ mA})(680 \Omega) = -2.72 \text{ V}$$

This gives a second point at 4 mA and  $-2.72 \text{ V}$ . A line is now drawn between the two points, and the values of  $I_D$  and  $V_{GS}$  at the intersection of the line and the curve are taken from the graph, as illustrated in Figure 8-22(b). The Q-point values from the graph are  $I_D = 2.25 \text{ mA}$  and  $V_{GS} = -1.5 \text{ V}$ .

 



FIGURE 8-22

**Related Exercise** If  $R_S$  is increased to  $1 \text{ k}\Omega$  in Figure 8-22(a), what is the new Q-point?

### Voltage-Divider Bias

An  $n$ -channel JFET with voltage-divider bias is shown in Figure 8-23. The voltage at the source of the JFET must be more positive than the voltage at the gate in order to keep the gate-source junction reverse-biased.

FIGURE 8-23  
An  $n$ -channel JFET with voltage-divider bias ( $I_S = I_D$ ).

 

The source voltage is

$$V_S = I_D R_S$$

The gate voltage is set by resistors  $R_1$  and  $R_2$  as expressed by the following equation using the voltage-divider formula:

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} \quad (8-8)$$

The gate-to-source voltage is

$$V_{GS} = V_G - V_S$$

and the source voltage is

$$V_S = V_G - V_{GS}$$

The drain current can be expressed as

$$I_D = \frac{V_S}{R_S}$$


Substituting for  $V_S$ ,

$$I_D = \frac{V_G - V_{GS}}{R_S} \quad (8-9)$$

### EXAMPLE 8-11

Determine  $I_D$  and  $V_{GS}$  for the JFET with voltage-divider bias in Figure 8-24, given that  $V_D = 7$  V.

FIGURE 8-24

 

**Solution**

$$I_D = \frac{V_{DD} - V_D}{R_D} = \frac{12 \text{ V} - 7 \text{ V}}{3.3 \text{ k}\Omega} = \frac{5 \text{ V}}{3.3 \text{ k}\Omega} \approx 1.52 \text{ mA}$$

Calculate the gate-to-source voltage as follows:

$$V_S = I_D R_S = (1.52 \text{ mA})(1.8 \text{ k}\Omega) = 2.74 \text{ V}$$

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \left( \frac{1 \text{ M}\Omega}{7.8 \text{ M}\Omega} \right) 12 \text{ V} = 1.54 \text{ V}$$

$$V_{GS} = V_G - V_S = 1.54 \text{ V} - 2.74 \text{ V} = -1.2 \text{ V}$$

If  $V_D$  had not been given in this example, the Q-point values could not have been found without the transfer characteristic curve.

**Related Exercise** Given that  $V_D = 6 \text{ V}$  in Figure 8–24, determine the Q-point.

### Graphical Analysis of a JFET with Voltage-Divider Bias

An approach similar to the one used for self-bias can be used with voltage-divider bias to graphically determine the Q-point of a circuit on the transfer characteristic curve.

In a JFET with voltage-divider bias when  $I_D = 0$ ,  $V_{GS}$  is not zero, as in the self-biased case, because the voltage divider produces a voltage at the gate independent of the drain current. The voltage-divider dc load line is determined as follows.

For  $I_D = 0$ ,

$$V_S = I_D R_S = (0)R_S = 0 \text{ V}$$

$$V_{GS} = V_G - V_S = V_G - 0 \text{ V} = V_G$$


Therefore, one point on the line is at  $I_D = 0$  and  $V_{GS} = V_G$ .

For  $V_{GS} = 0$ ,

$$I_D = \frac{V_G - V_{GS}}{R_S} = \frac{V_G}{R_S}$$

A second point on the line is at  $I_D = V_G/R_S$  and  $V_{GS} = 0$ . The dc load line is shown in Figure 8–25.

**FIGURE 8–25**  
DC load line for a JFET with voltage-divider bias.

 

**EXAMPLE 8-12**

Determine the Q-point for the JFET with voltage-divider bias in Figure 8-26(a), given the transfer characteristic curve in Figure 8-26(b).

**Solution** First, establish the two points for the bias line.

For  $I_D = 0$ ,

$$V_{GS} = V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} = \left( \frac{2.2 \text{ M}\Omega}{4.4 \text{ M}\Omega} \right) 8 \text{ V} = 4 \text{ V}$$

The first point is at  $I_D = 0$  and  $V_{GS} = 4 \text{ V}$ .

For  $V_{GS} = 0$ ,

$$I_D = \frac{V_G - V_{GS}}{R_S} = \frac{V_G}{R_S} = \frac{4 \text{ V}}{3.3 \text{ k}\Omega} = 1.2 \text{ mA}$$

The second point is at  $I_D = 1.2 \text{ mA}$  and  $V_{GS} = 0$ .

The load line is drawn in Figure 8-26(b), and the Q-point values of  $I_D = 1.7 \text{ mA}$  and  $V_{GS} = -2 \text{ V}$  are picked off the graph, as indicated.


 


FIGURE 8-26

 

**Related Exercise** Change  $R_S$  to  $4.7 \text{ k}\Omega$  and determine the Q-point for the circuit in Figure 8-26(a).

### Q-Point Stability

Unfortunately, the transfer characteristic of a JFET can differ considerably from one device to another of the same type. If, for example, a 2N5459 JFET is replaced in a given bias circuit with another 2N5459, the transfer characteristic curve can vary greatly as illustrated in Figure 8-27(a). In this case, the maximum  $I_{DSS}$  is  $16 \text{ mA}$  and the minimum

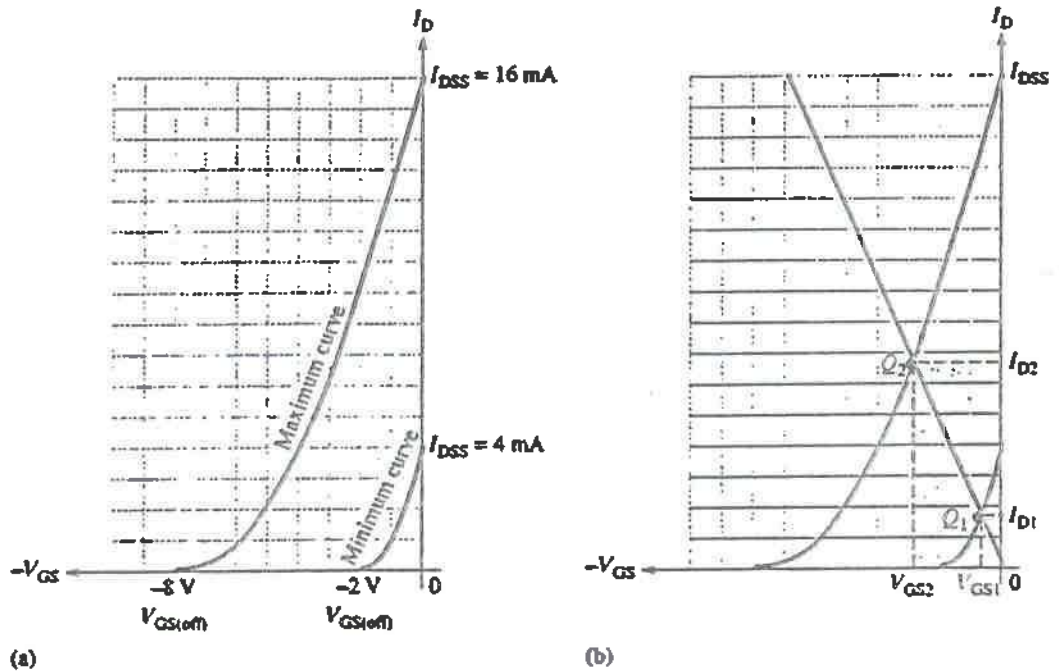


FIGURE 8-27

Variation in the transfer characteristic of 2N5459 JFETs and the effect on the Q-point.

$I_{DSS}$  is 4 mA. Likewise, the maximum  $V_{GS(off)}$  is  $-8 \text{ V}$  and the minimum  $V_{GS(off)}$  is  $-2 \text{ V}$ . This means that if you have a selection of 2N5459s and you randomly pick one out, it can have values anywhere within these ranges.

If a self-bias dc load line is drawn as illustrated in Figure 8-27(b), the same circuit using a 2N5459 can have a Q-point anywhere along the line from  $Q_1$ , the minimum bias point, to  $Q_2$ , the maximum bias point. Accordingly, the drain current can be any value between  $I_{D1}$  and  $I_{D2}$ , as shown. This means that the dc voltage at the drain can have a range of values depending on  $I_D$ . Also, the gate-to-source voltage can be any value between  $V_{GS1}$  and  $V_{GS2}$ , as indicated.

With voltage-divider bias, the dependency of  $I_D$  on the range of Q-points is reduced because the slope of the bias line is less than for self-bias. Although  $V_{GS}$  varies quite a bit for both self-bias and voltage-divider bias,  $I_D$  is much more stable with voltage-divider bias, as illustrated in Figure 8-28.

 


FIGURE 8-28

The change in  $I_D$  between the minimum and the maximum  $Q$ -points is much less for a JFET with voltage-divider bias than for a self-biased JFET.


### SECTION 8-3 REVIEW

1. Should a  $p$ -channel JFET have a positive or a negative  $V_{GS}$ ?
2. In a certain self-biased  $n$ -channel JFET circuit,  $I_D = 8 \text{ mA}$  and  $R_S = 1 \text{ k}\Omega$ . Determine  $V_{GS}$ .
3. An  $n$ -channel JFET with voltage-divider bias has a gate voltage of  $3 \text{ V}$  and a source voltage of  $5 \text{ V}$ . Calculate  $V_{GS}$ .

---

**SUMMARY OF FIELD-EFFECT TRANSISTORS**


---

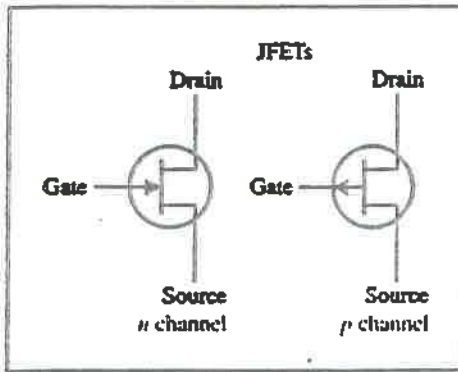**JFETs**


- Gate-source junction must be reverse-biased.
- $V_{GS}$  controls  $I_D$ .
- Value of  $V_{DS}$  at which  $I_D$  becomes constant is the pinch-off voltage.
- Value of  $V_{GS}$  at which  $I_D$  becomes zero is the cutoff voltage,  $V_{GS(off)}$ .
- $I_{DSS}$  is drain current when  $V_{GS} = 0$ .
- Transfer characteristic:

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

- Forward transconductance:

$$g_m = g_{m0} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)$$

$$g_{m0} = \frac{2I_{DSS}}{|V_{GS(off)}|}$$

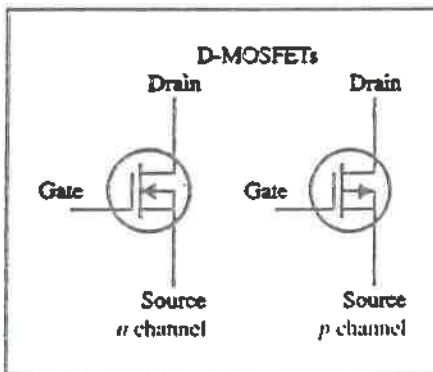**D-MOSFETs**


Except that it can be operated in enhancement mode, the D-MOSFET characteristics are the same as JFET.

- *Depletion mode:*
  - n channel:*  $V_{GS}$  negative
  - p channel:*  $V_{GS}$  positive
- *Enhancement mode:*
  - n channel:*  $V_{GS}$  positive
  - p channel:*  $V_{GS}$  negative
- $V_{GS}$  controls  $I_D$ .
- Value of  $V_{GS}$  at which  $I_D$  becomes zero is the cutoff voltage,  $V_{GS(off)}$ .
- $I_{DSS}$  is drain current when  $V_{GS} = 0$ .
- Transfer characteristic:

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

SUMMARY OF FIELD-EFFECT TRANSISTORS, *continued*

E-MOSFETs

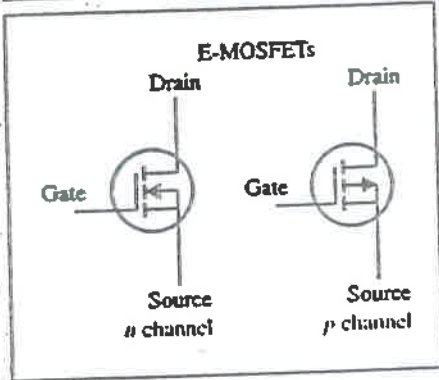

There is no depletion mode and characteristics differ from D-MOSFET.

■ *Enhancement mode:*

- n* channel:  $V_{GS}$  positive
- p* channel:  $V_{GS}$  negative

■  $V_{GS}$  controls  $I_D$ .


■ Value of  $V_{GS}$  at which  $I_D$  starts to flow is the threshold voltage,  $V_{GS(th)}$ .

■ Transfer characteristic:

$$I_D = K(V_{GS} - V_{GS(th)})^2$$

■  $K$  in formula can be calculated by substituting data sheet values  $I_{D(on)}$  for  $I_D$  and  $V_{GS}$  at which  $I_{D(on)}$  is specified for  $V_{GS}$ .

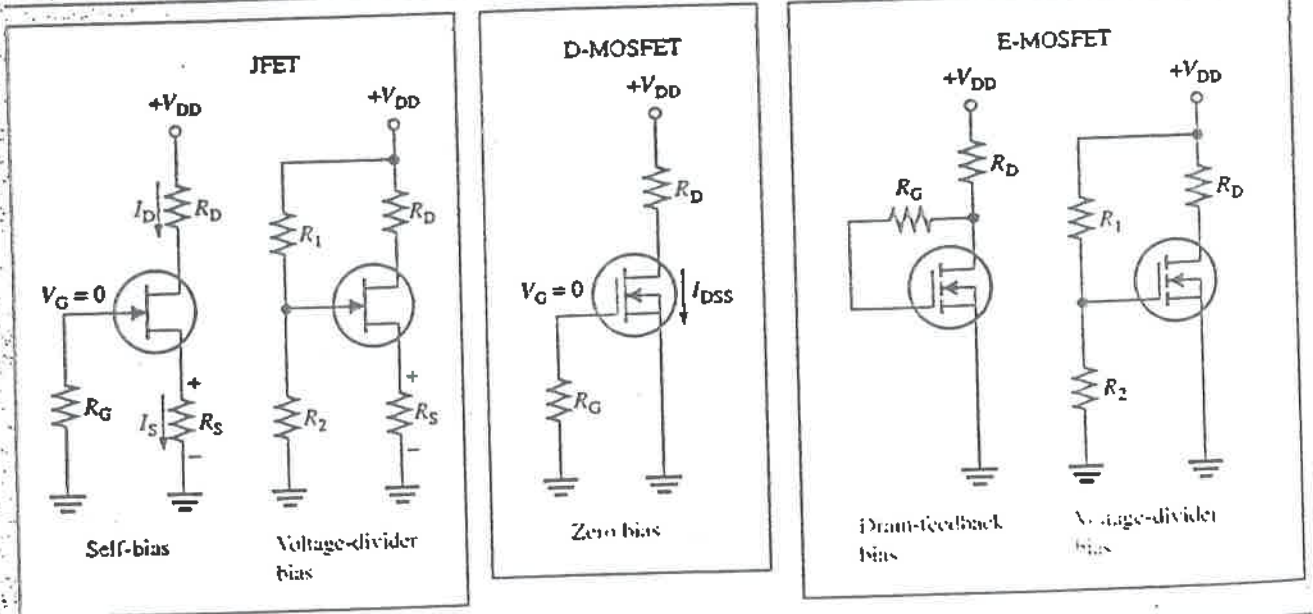FET BIASING (voltage polarities and current directions reverse for *p* channel)



## 8-4 SMALL-SIGNAL FET AMPLIFIERS

### 8-4-1 JFET Common-Source Amplifier

 


FIGURE 9-12  
JFET common-source amplifier.


 


FIGURE 9-13  
DC equivalent circuit for the amplifier in Figure 9-12.


### 8-4-2 JFET Common-Drain Amplifier

FIGURE 9-22  
JFET common-drain amplifier  
(source-follower).

 

### 8-4-3 JFET Common-Gate Amplifier

FIGURE 9-26  
JFET common-gate amplifier.

 




44155794

سجاد البكري

 1- What is the wavelength of FM radio channel with 90 MHz frequency?



$$\lambda = \frac{c}{f} = \frac{3 \times 10^8 \text{ m/s}}{90 \times 10^6 \text{ Hz}} = 3.33 \text{ Mm}$$

2- The wavelength of a Green laser light is about 500 nm, determine the frequency? (Use suitable metric Prefix)

$$f = \frac{c}{\lambda} = \frac{3 \times 10^8 \text{ m/s}}{500 \times 10^{-9} \text{ m}} = 6 \times 10^{14} \text{ Hz}$$