

Logic Gates

Lecture 08

COE211-Digital Logic Design

الفصل الدراسي الأول 1442-2020 Fall


جامعة طيبة فرع ينبع - كلية علوم وهندسة الحاسبات - شطر الطالبات




د. فاطمة الحربي

Symbols



Symbol set 1

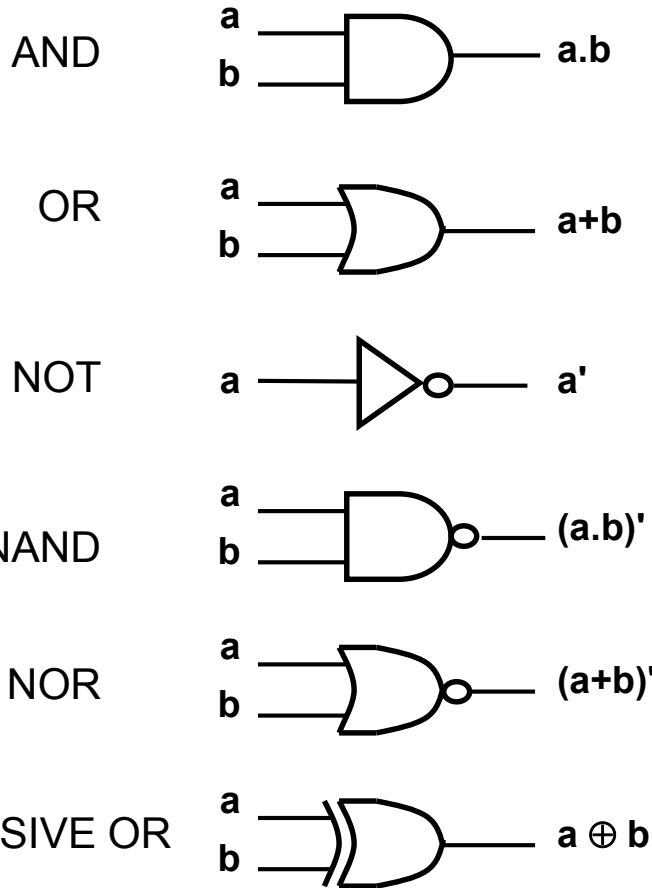

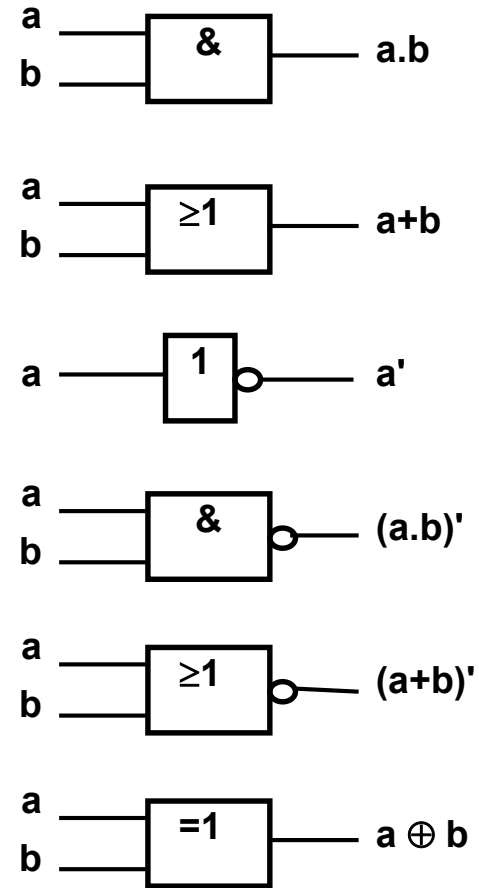Symbol set 2
(ANSI/IEEE Standard 91-1984)




Inverter Gate

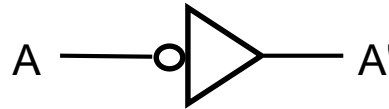
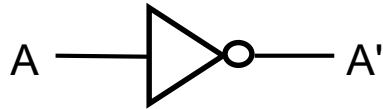


A	A'
0	1
1	0

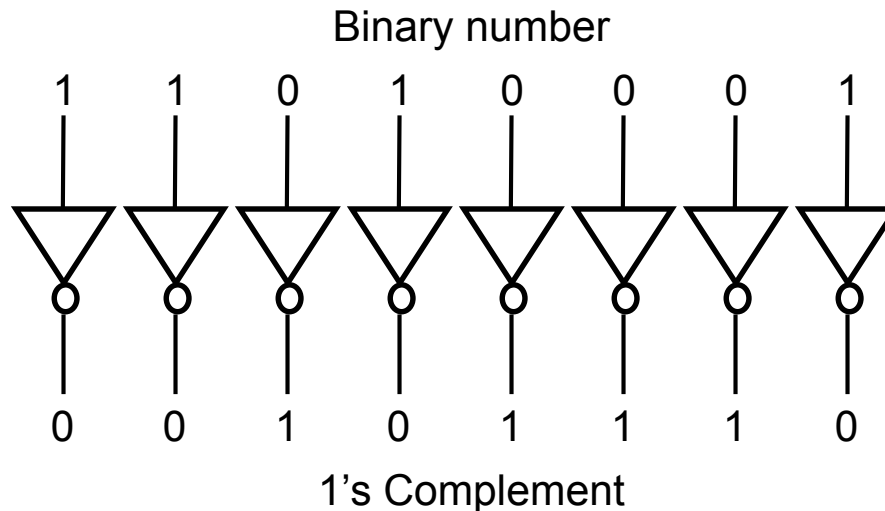- Application of the inverter: complement




AND Gate

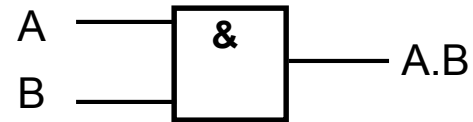
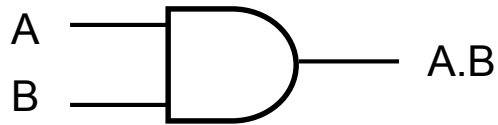


A	B	A . B
0	0	0
0	1	0
1	0	0
1	1	1

Application of AND Gate



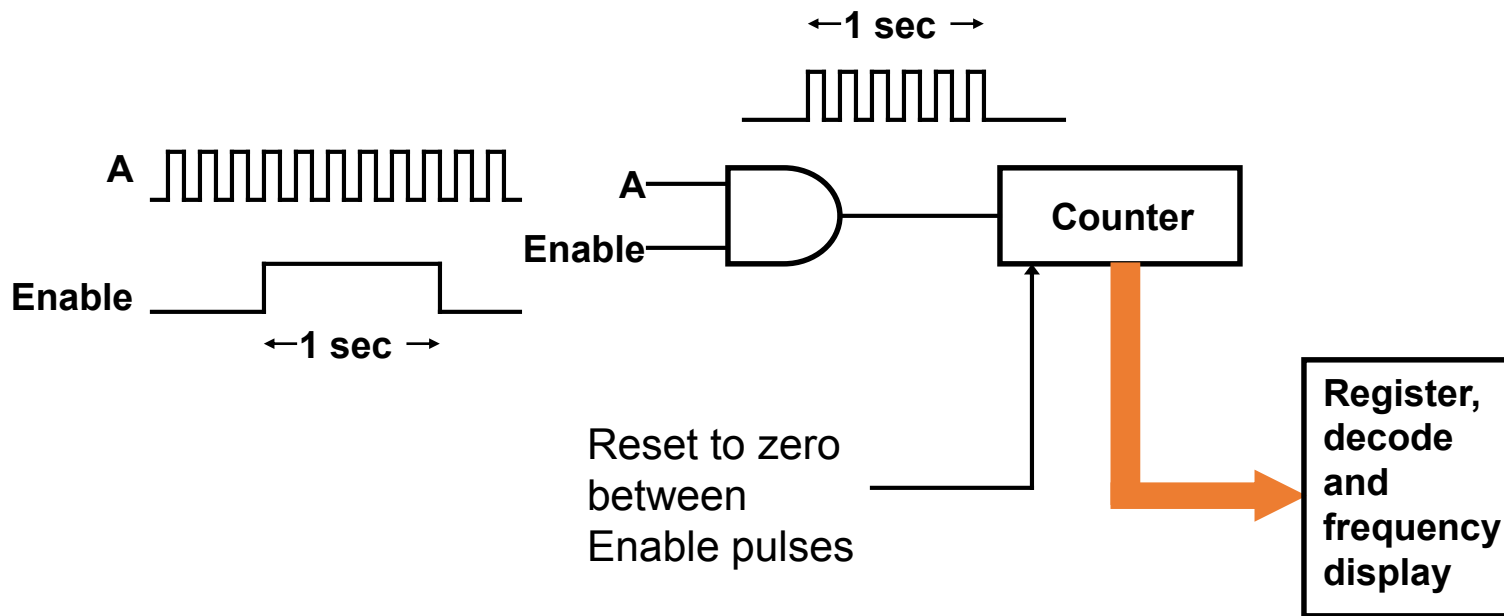


OR Gate

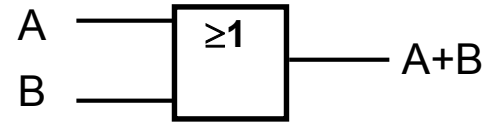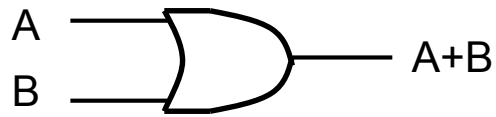


A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1

NAND Gate

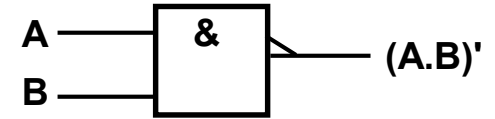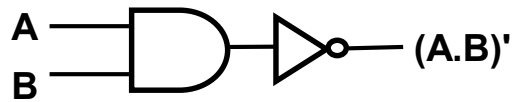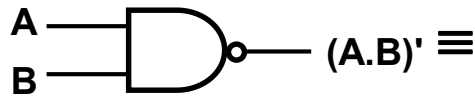


A	B	$(A.B)'$
0	0	1
0	1	1
1	0	1
1	1	0

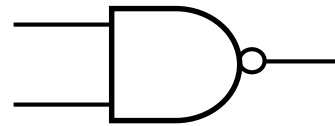


NAND

≡

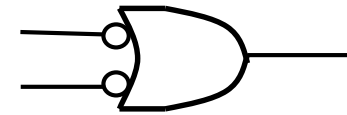


Negative-OR



NOR Gate

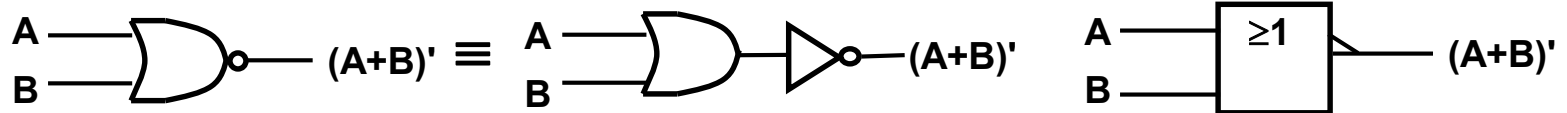

A	B	$(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0


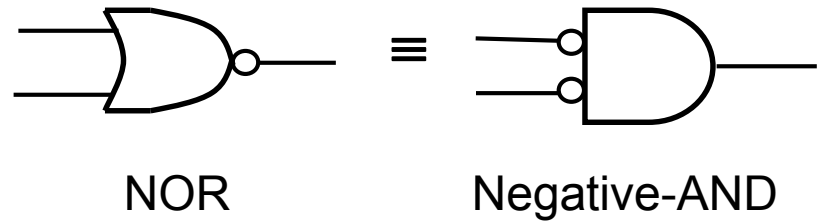


XOR Gate

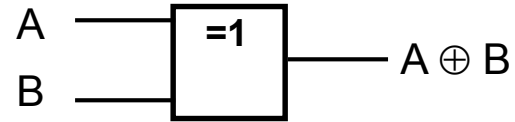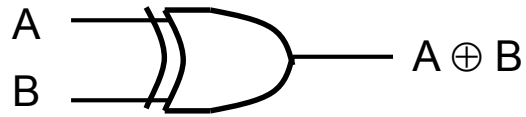

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

XNOR Gate

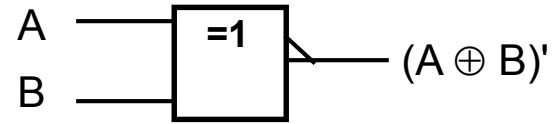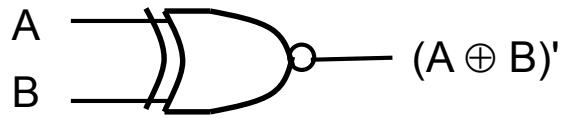


A	B	$(A \oplus B)'$
0	0	1
0	1	0
1	0	0
1	1	1

Drawing Logic Circuit

- When a Boolean expression is provided, we can easily draw the logic circuit


Example 1

- Draw the logic circuit of the following function:
 - $F1 = xyz'$ (note the use of a 3-input AND gate)

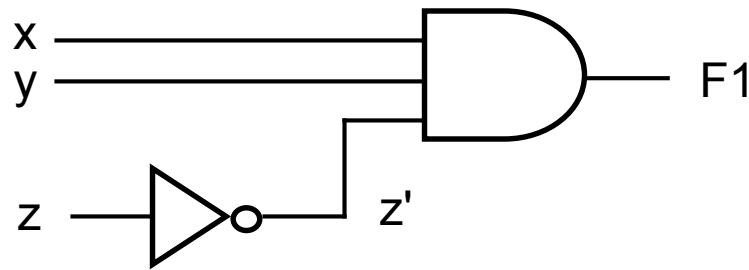


Example 2

- Draw the logic circuit of the following function:
 - $F2 = x + y'z$ (can assume that variables and their complements are available)

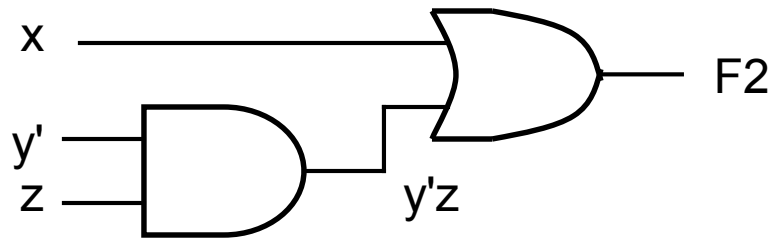

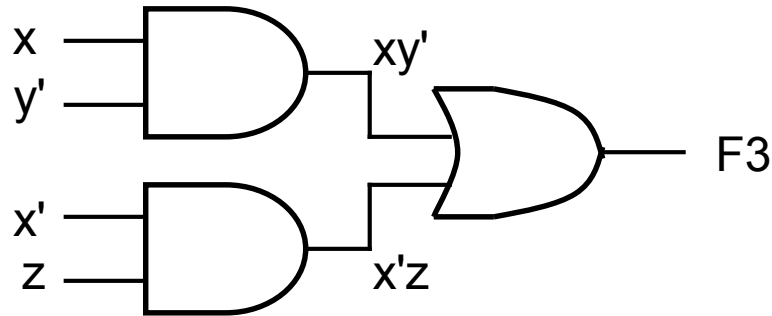
Example 3

- Draw the logic circuit of the following function:
 - $F3 = xy' + x'z$



Analyzing Logic Circuits

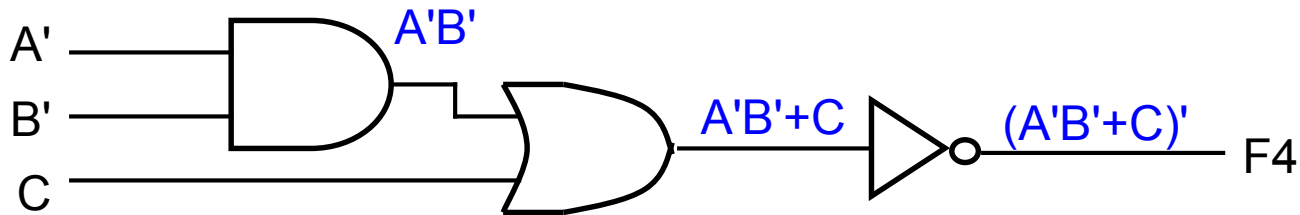- When a logic circuit is provided, we can analyse the circuit to obtain the logic expression
- Example: What is the Boolean expression of F4?



$$F4 = (A'B'+C)' = (A+B).C'$$