
Logic and Computer Design Fundamentals

Control of Register Transfers

Charles Kime

© 2008 Pearson Education, Inc.


(Hyperlinks are active in View Show mode)

Overview

- **Part 1 – Registers, Microoperations and Implementations**
- **Part 2 – Counters, Register Cells, Buses, & Serial Operations**
- **Part 3 – Control of Register Transfers**
 - **Introduction to register transfer systems**
 - **Register transfer system design procedure**
 - **A design example**
 - **Microprogrammed control**

Introduction to Register Transfer Systems

■ Datapath and Control Unit

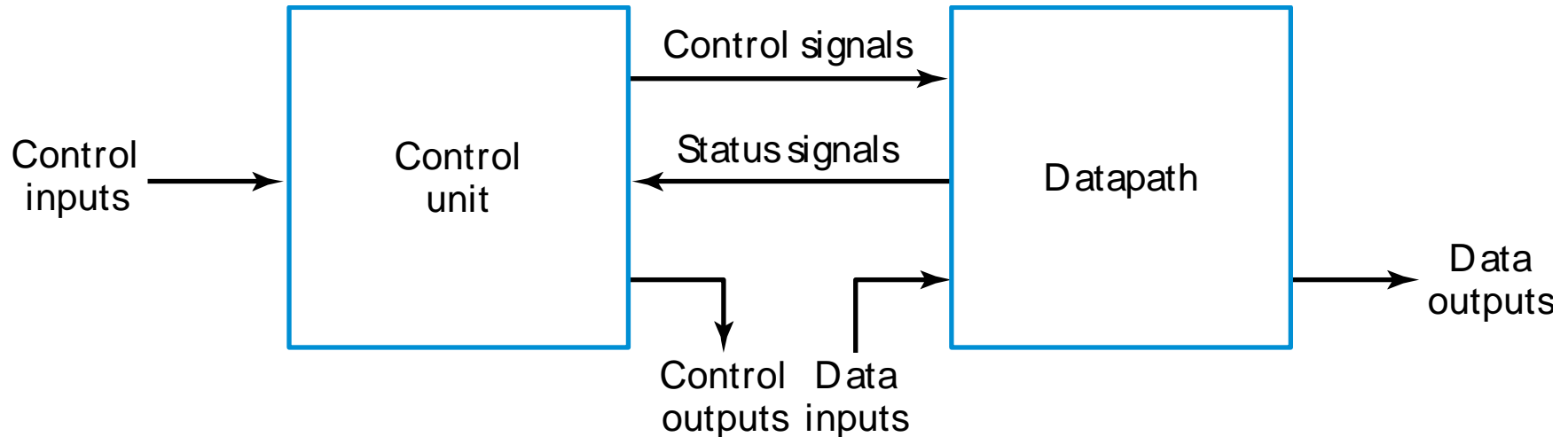

- **Set of registers, mostly in Datapath with some in Control Unit**
- **Register transfers performed on registers**
- **Control that supervises the sequencing of the register transfers**

Programmable and Non-Programmable Systems

- **Programmable System** – a portion of the input consists of a **sequence of instructions** called a *program*, typically stored in a memory and addressed by a *program counter (PC)*. The Control Unit is responsible for fetching and executing these instructions.
- **Non-programmable System** – the control unit **does not** deal with fetching and executing instructions, but contains all of the information for sequencing register transfers **based on inputs and on status bits from the datapath**.
- **Only non-programmable designs are considered here.**


Register Transfer System Design Procedure

- Write a detailed **system specification**
- Determine **all data, control and status input signals, all data, control and status output signals, and registers of the datapath and control unit.**
- Find a **state machine diagram** for the system including register transfers for the datapath and control unit as outputs.
- Determine all **internal control and status signals**. Use these signals to separate output conditions and actions, including register transfers, from the state machine diagram flow and represent them in tabular form.
- Draw a **block diagram of the datapath including all control and status inputs and outputs. Draw a block diagram of the control if it includes register transfer hardware.**
- Design **any specialized register transfer logic** as needed for the datapath and the control.
- Design **the control unit logic.**
- **Verify the correct operation** of the combined datapath and control unit. If verification fails, debug the system and verify the changed system.

Example 1

DASHWATCH

Example 1: DASHWATCH

 

Exterior View

Example 1 – DASHWATCH

Specifications

- **Very Inexpensive Stop Watch for “dash” runners**
- **Times intervals to at most 99.99 seconds**
- **Stopwatch action plus storage of best performance time per session (session ended by turning off power or pushing RESET)**
- **Inputs: START, STOP, CSS (compare and store shortest), RESET**
- **Registers: 4-digit BCD Counter (TM) and 16-bit Parallel Load Register (SD)**
- **Output: 4 digit BCD LCD with decimal point**

Example 1: DASHWATCH


Inputs, Outputs, and Registers

□ TABLE 7-15
Inputs, Outputs, and Registers of the DashWatch

Symbol	Function	Type
START	Initialize timer to 0 and start timer	Control input
STOP	Stop timer and display timer	Control input
CSS	Compare, store and display shortest dash time	Control input
RESET	Set shortest value to 10011001	Control input
B_1	Digit 1 data vector a, b, c, d, e, f, g to display	Data output vector
B_0	Digit 0 data vector a, b, c, d, e, f, g to display	Data output vector
DP	Decimal point to display (= 1)	Data output
B_{-1}	Digit -1 data vector a, b, c, d, e, f, g to display	Data output vector
B_{-2}	Digit -2 data vector a, b, c, d, e, f, g to display	Data output vector
B	The 29-bit display input vector ($B_1, B_0, DP, B_{-1}, B_{-2}$)	Data output vector
TM	4-Digit BCD counter	16-Bit register
SD	Parallel load register	16-Bit register

Example 1: DASHWATCH

SMD with Register Transfer Outputs

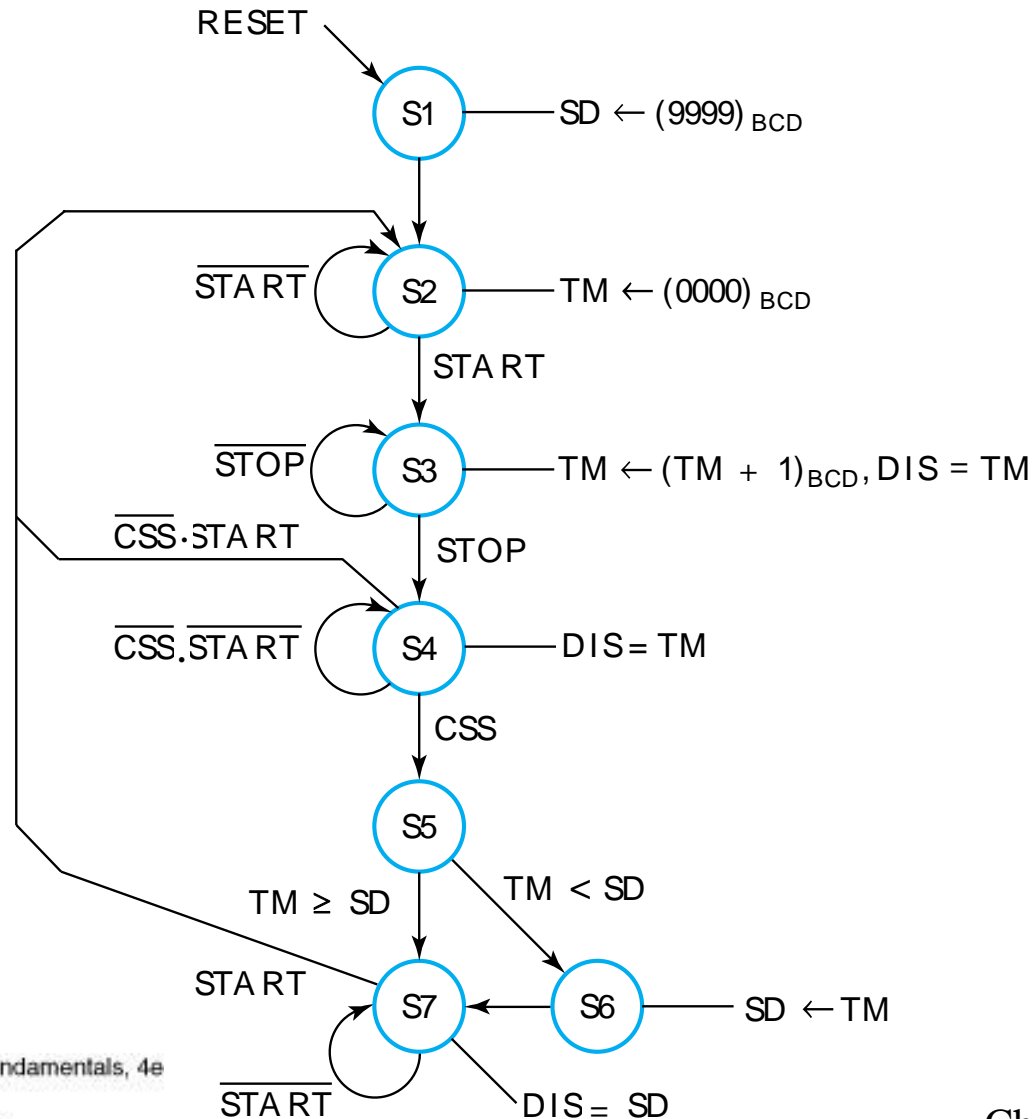

Example 1: DASHWATCH

SMD Design

- Specify only Moore outputs (no particular reason)
- **S1:** Reset state - in this state, **initialize SD to 1001100110011001 (99.99)**, the maximum possible dash time.
- **S2:** Because of Moore output spec, **S1 cannot be used for this state since SD is not to be initialized again to 99.99 after having passed through states S4 or S7. TM is initialized to (0000)_{BCD} for next dash.**
- **S3:** State during dash. Entered with START and exited with STOP. While in state, 1 (**0.01 seconds**) is added to TM for each clock pulse. (**Clock frequency is 100 Hz**), and DIS shows TM value.
- **S4:** Decision state whether to **Compare, Store, and display Shortest dash time**, or to continue to display TM. Also START begins new dash.
- **S5:** State for **comparison of TM to SD.**
- **S6:** State for **loading TM into SD if TM is smaller.**
- **S7:** State for **START to begin new dash and display of SD as shortest dash time.**

Example 1: DASHWATCH

Output Control/Status Table

□ TABLE 7-16
Datapath Output Actions and Status Generation with Control and Status Signals

Action or Status	Control or Status Signals	Meaning for Values 1 and 0
$TM \leftarrow (0000)_{BCD}$	RSTM	1: Reset TM to 0 (synchronous reset) 0: No reset of TM
$TM \leftarrow (TM + 1)_{BCD}$	ENTM	1: BCD count up TM by 1, 0: hold TM value
$SD \leftarrow (9999)_{BCD}$	UPDATE LSR	0: Select 1001100110011001 for loading SD 1: Enable load SD, 0: disable load SD
$SD \leftarrow TM$	UPDATE LSR	1: Select TM for loading SD Same as above
DIS = TM DIS = SD	DS	0: Select TM for DIS 1: Select SD for DIS
TM < SD TM ≥ SD	ALTB	1: TM less than SD 0: TM greater than or equal to SD

Example 1: DASHWATCH

Determination of Internal Control/Status Signals

■ **TM – Timer**

- Reset to 0000: **RSTM**
- Enable to Count Up: **ENTM**

■ **SD – Shortest Dash**




- Load SD: **LSR = 1**;
- Select input 9999: **UPDATE = 0**
- Select input TM: **UPDATE = 1**

■ **DIS – Display ($B_1, B_0, DP, B_{-1}, B_{-2}$)**


- Select input TM: **DS = 0**
- Select input SD: **DS = 1**

■ **Compare TM and SD (Status)**

- $TM < SD$: **ALTB = 1**
- $TM \geq SD$: **ALTB = 0**

 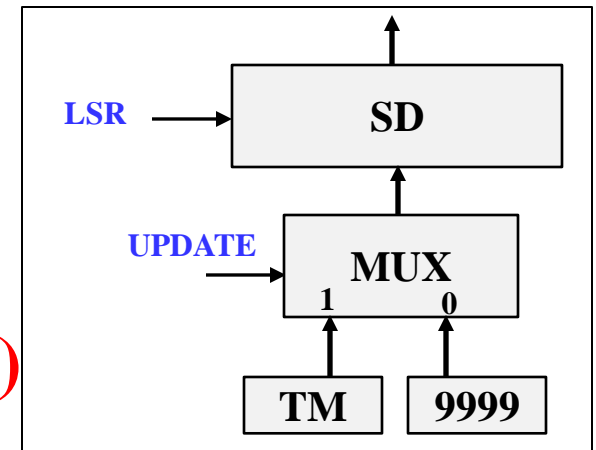 

Example 1: DASHWATCH Datapath

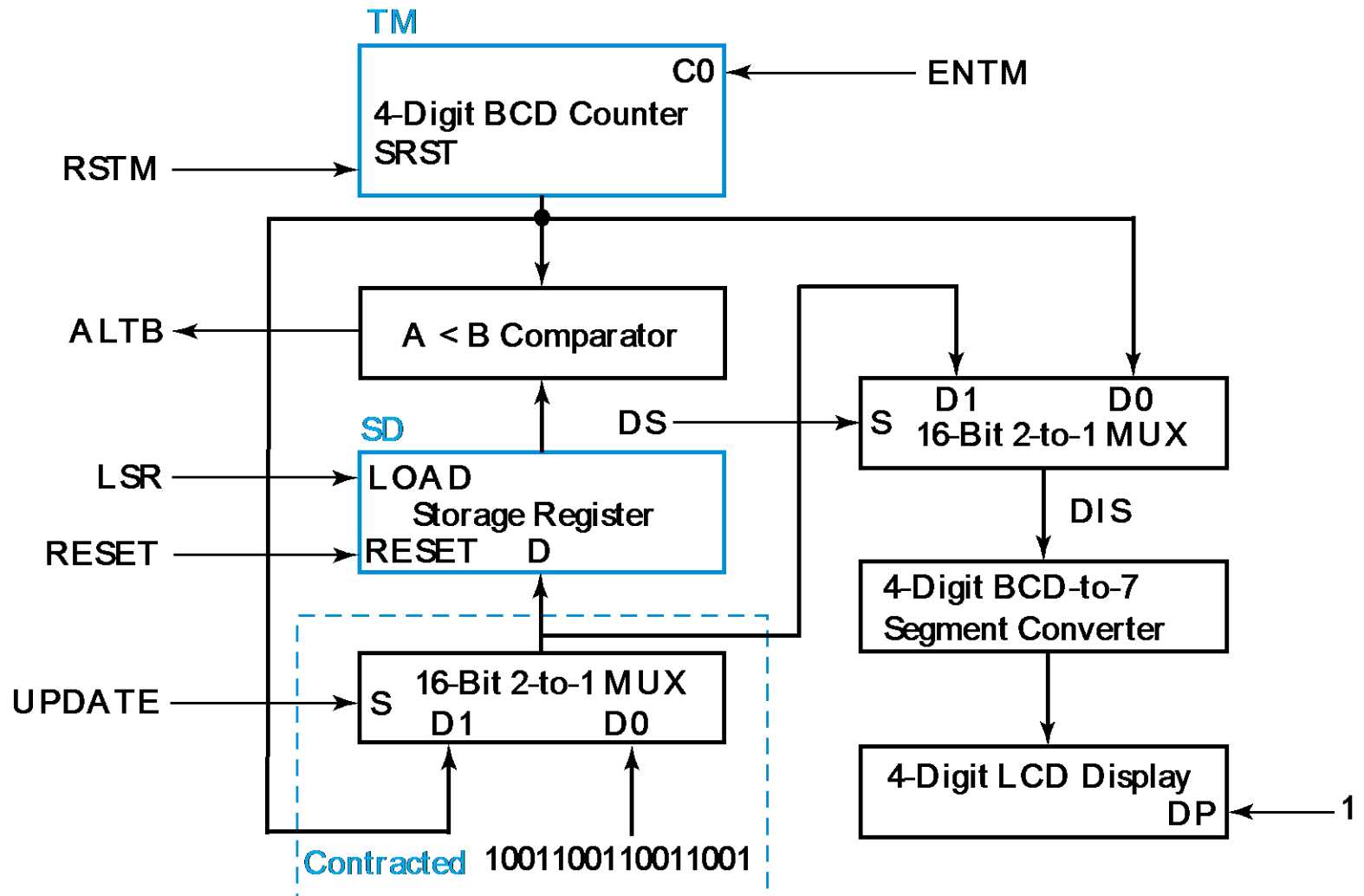

(a)

Example 1: DASHWATCH

Datapath Development

- **TM: 4-digit BCD Counter with Synchronous Reset**
 - Based on previous BCD adder digit design
 - synchronous reset SRST added
 - SRST = RSTM
 - C0 (Incoming carry) = ENTM
- **A < B Comparator**
 - Compares TM to SD
 - Designed as left-to-right iterative cell array with output C0
- **SD: Standard 16-bit parallel load register**
 - LOAD = LSR
 - Contracted standard 2-way, 16-bit multiplexer used to select between 9999_{BCD} and TM as parallel load input D
 - S = UPDATE

Example 1: DASHWATCH

Datapath Development – Display Logic




- **2-way 16-bit multiplexer**
 - Selects between TM and SD
 - $S = DS$
- **4-digit BCD-to-7 Segment Converter**
 - Uses previous design
- **4-digit 7-Segment Display with Decimal Point**
 - 2-digit fractional part
 - Decimal Point control = DP
 - $DP = 1$

Example 1: DASHWATCH

SMD with Control Signal Outputs Replacing Register Transfers

Defaults:

All Outputs = 0

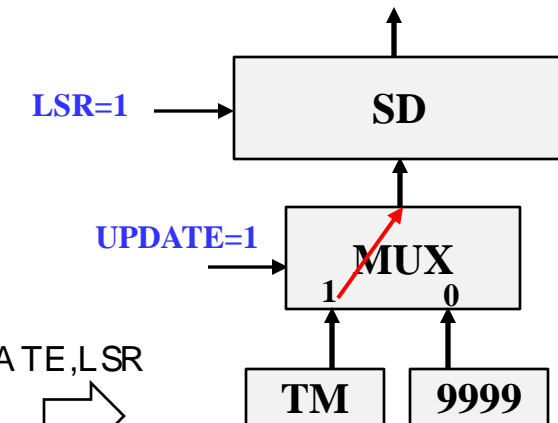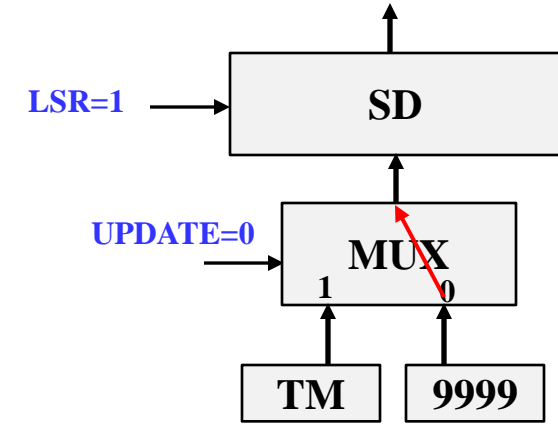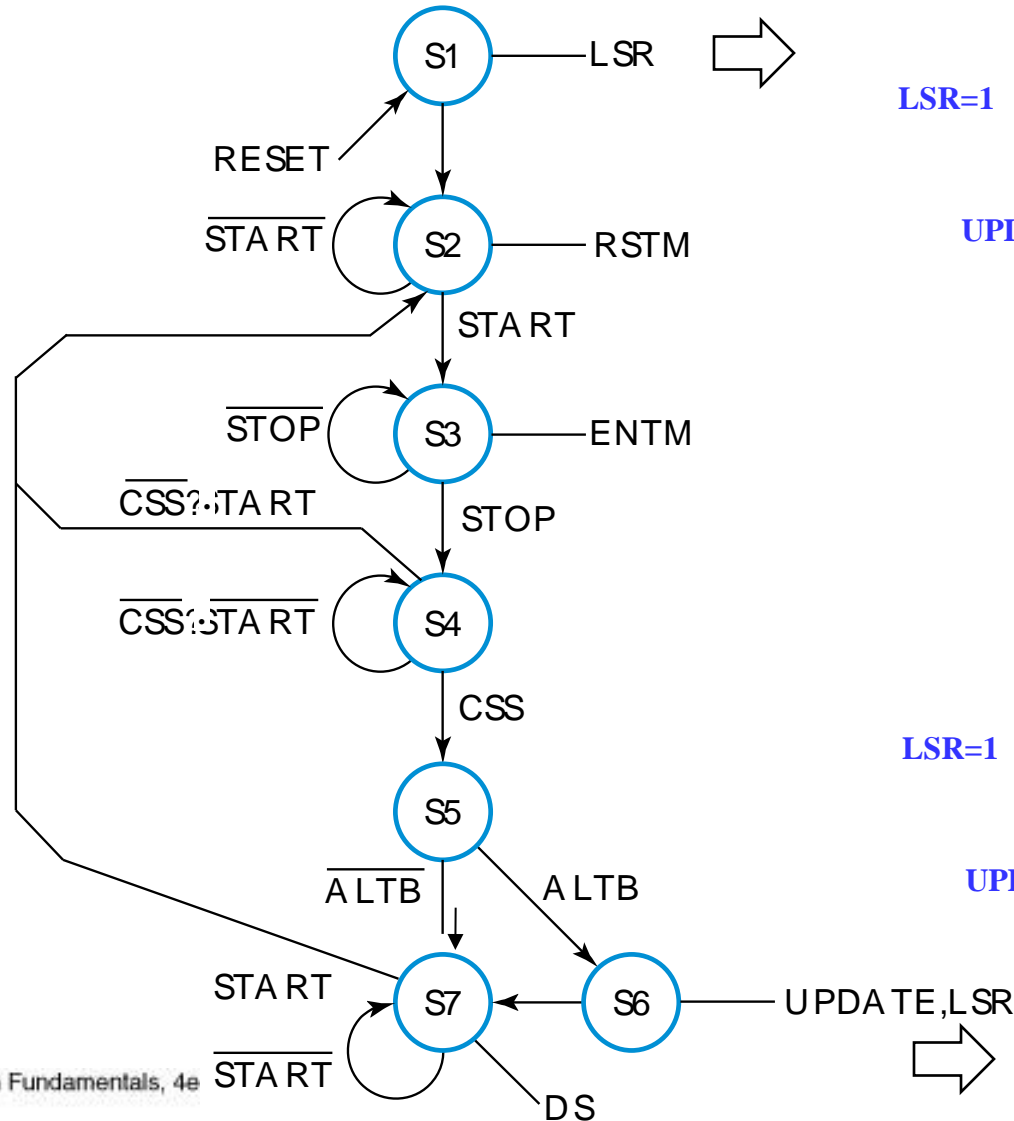

Example 1: DASHWATCH

FF Input Equations

- **One-Hot State Assignment – 7 bits**
- **State S1 entered only by using asynchronous RESET**

$$D_{S1} = S1(t+1) = 0$$

$$D_{S2} = S2(t+1) = S1 + S2 \cdot \overline{START} + S4 \cdot \overline{CSS} \cdot START + S7 \cdot START$$

$$D_{S3} = S3(t+1) = S2 \cdot START + S3 \cdot \overline{STOP}$$

$$D_{S4} = S4(t+1) = S3 \cdot STOP + S4 \cdot \overline{CSS} \cdot \overline{START}$$

$$D_{S5} = S5(t+1) = S4 \cdot CSS$$

$$D_{S6} = S5 \cdot ALTB$$

$$D_{S7} = S7(t+1) = S5 \cdot \overline{ALTB} + S6 + S7 \cdot \overline{START}$$

Example 1: DASHWATCH

Output Equations

$$LSR = S1 + S6$$

$$RSTM = S2$$

$$ENTM = S3$$


$$UPDATE = S6$$

$$DS = S7$$

Example 2

Handheld Game: PIG

Example 2: PIG

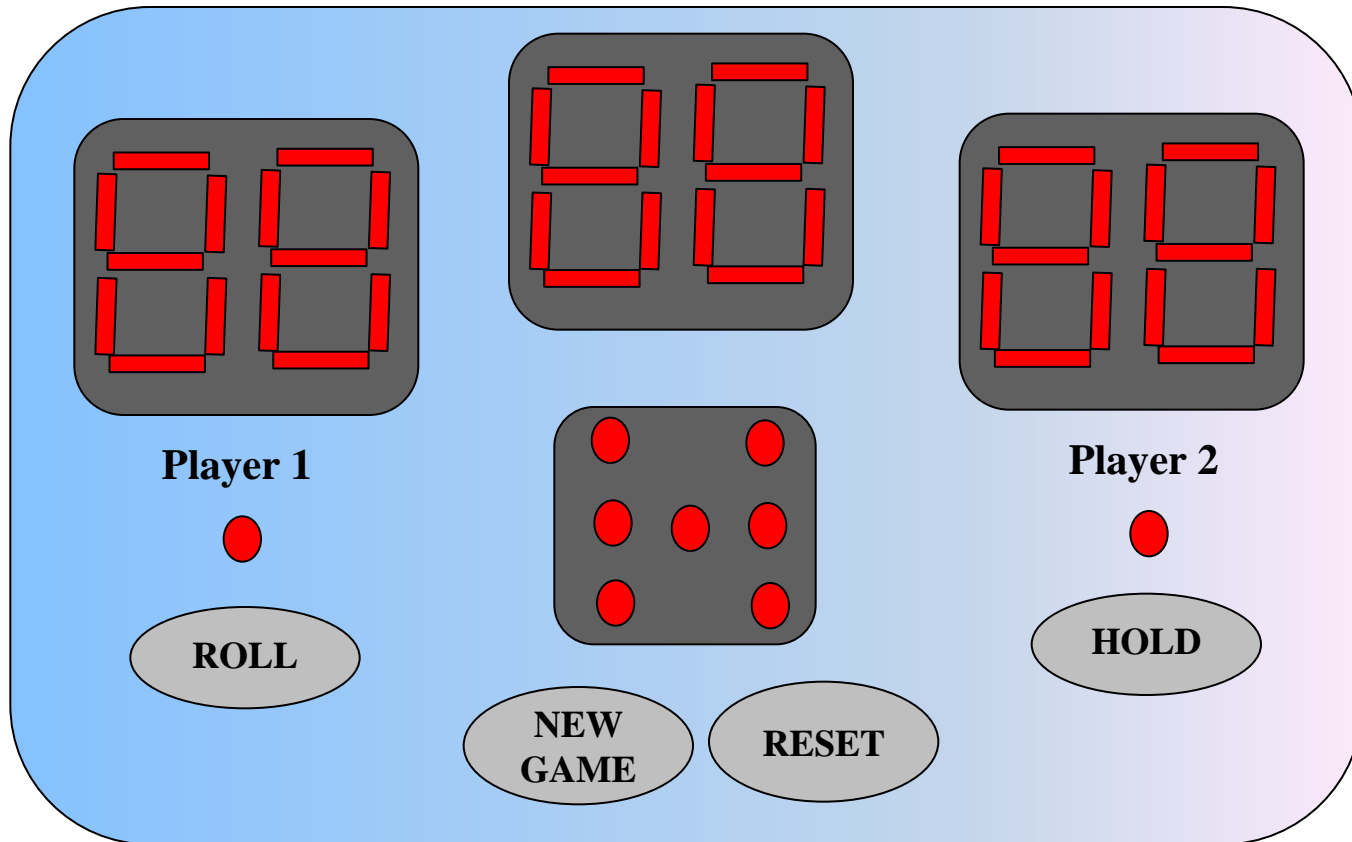

Exterior View

Example 2: PIG Registers

DIE

**3-Bit 1-to-6
Counter**

SUR

**7-Bit Parallel Load
Register**

FP

FF

FP=0 in the first game.
i.e. Player 1 starts the first game.

Then FP=1 in the second game.
i.e. Player 2 starts the second
game.

Then FP=0 in the third game,
and so on.

TR1

**7-Bit Parallel Load
Register**

TR2

**7-Bit Parallel Load
Register**

CP

FF

To specify the current player
turn within a game

Datapath Registers

Control Registers

Example 2 – PIG

Specifications

- **PIG is a dice game which is played with a single die that has 1 to 6 dots on its six faces.**
- **During each turn, the player rolls the die one or more times until either:**
 - **1 is rolled**
 - **The player chooses to HOLD.**
- **For each roll, the value rolled, except for a 1, is added to a subtotal for the current turn.**
- **If a 1 is rolled, the subtotal become 0, and the player's turn is ended.**
- **At the end of each turn, the subtotal is added to the player's overall total, and the play passes to the other player.**
- **The first player to reach or exceed 100 wins.**

Example 2 – PIG

Specifications

- **Inputs: ROLL, HOLD, NEW_GAME, RESET**
- **Outputs:**
 - **7-bit LED die display (DDIS)**
 - **7-Segment pair to display the subtotal for the current turn (SUB)**
 - **7-Segment pair to display the overall total for the player 1 (TP1)**
 - **7-Segment pair to display the overall total for the player 2 (TP2)**
 - **Player 1 LED ON/ OFF (P1)**
 - **Player 2 LED ON/ OFF (P2)**
- **Registers:**
 - **Datapath Registers:**
 - **3-bit 1-to-6 Counter (DIE)**
 - **7-bit Parallel Load Register (SUR)**
 - **7-bit Parallel Load Register (TR1)**
 - **7-bit Parallel Load Register (TR2)**
 - **Control Registers:**
 - **Flip-Flop (FP)**
 - **Flip-Flop (CP)**

Example 2: PIG

Inputs, Outputs, and Registers

Symbol	Name / Function		Type
ROLL	1: Starts die rolling	0: Stops die rolling	Control input
HOLD	1: Ends player turn	0: Continues player turn	Control input
NEW_GAME	1: Stats new game	0: Continues current game	Control input
RESET	1: Reset game to INIT state	0: No action	Control input
DDIS	7-bit LED die display array		Data output vector
SUB	14-bit 7-segment pair (a, b, c, d, e, f, g) to Turn Total display		Data output vector
TP1	14-bit 7-segment pair (a, b, c, d, e, f, g) to Player 1 display		Data output vector
TP2	14-bit 7-segment pair (a, b, c, d, e, f, g) to Player 2 display		Data output vector
P1	1: Player 1 LED on	0: Player 1 LED off	Data output
P2	1: Player 2 LED on	0: Player 2 LED off	Data output
DIE	Die value- Specialized counter to count 1, 2, 3, 4, 5, 6, 1, 2, 3, . . .		3- bit data register
SUR	Subtotal for active player: parallel load register		7- bit data register
TR1	Overall total for player 1: parallel load register		7- bit data register
TR2	Overall total for player 2: parallel load register		7- bit data register
FP	First player – flip-flop	0: Player 1, 1: Player 2	1-bit control register
CP	Current player – flip-flop	0: Player 1, 1: Player 2	1-bit control register


Example 2: PIG

SMD with Register Transfer Outputs

Defaults:

$P1 = \overline{CP}$,

$P2 = CP$

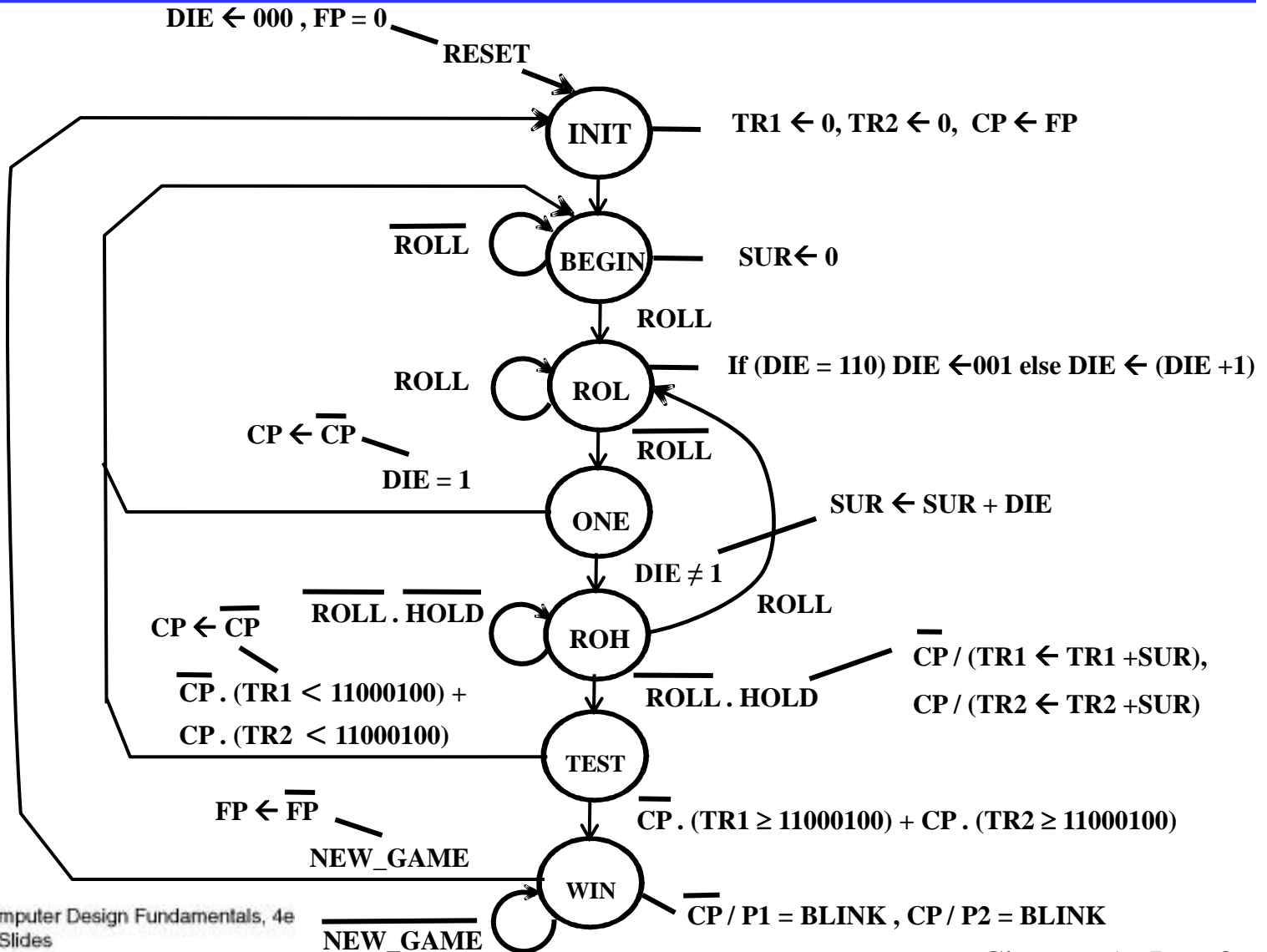







Example 2: PIG

Output Control/Status Table

Action or Status	Control or Status Signals	Meaning for values 1 and 0
TR1 \leftarrow 0 TR1 \leftarrow TR1 + SUR	RST1 LDT1	1: Reset TR1 (Synchronous reset), 1: Add SUR to TR1, 0: No action 0: No action
TR2 \leftarrow 0 TR2 \leftarrow TR2 + SUR	RST2 LDT2	1: Reset TR2 (Synchronous reset), 1: Add SUR to TR2, 0: No action 0: No action
SUR \leftarrow 0 SUR \leftarrow SUR + DIE	RSSU LDSU	1: Reset SUR (Synchronous reset), 1: Add DIE to SUR, 0: No action 0: No action
DIE \leftarrow 000 if (DIE = 110) DIE \leftarrow 001 else DIE \leftarrow (DIE + 1)	RESET ENDI	1: Reset DIE to 000 (Asynchronous reset) 1: Enable DIE to increment, 0: Hold DIE value
P1 = BLINK	BP1	1: Connect P1 to BLINK, 0: Connect P1 to 1
P2 = BLINK	BP2	1: Connect P2 to BLINK, 0: Connect P2 to 1
CP \leftarrow FP CP \leftarrow $\overline{\text{CP}}$	CPFI LDCP CPFI LDCP	1: Select FP for CP 1: Load <u>CP</u> , 0: Select CP for CP 1: Load CP, 0: No action 0: No action
FP \leftarrow $\overline{0}$ FP \leftarrow $\overline{\text{FP}}$	RESET LDFP	Asynchronous reset 1: Invert FP, 0: Hold FP
DIE = 1 DIE \neq 1	DIE1	1: DIE equal to 1 0: DIE not equal to 1
TR1 \geq 11000100	CP WN	0: Select TR1 for \geq 11000100 1: The Selected TR _i \geq 11000100 0: The Selected TR _i < 11000100
TR2 \geq 11000100	CP WN	1: Select TR2 for \geq 11000100 1: The Selected TR _i \geq 11000100 0: The Selected TR _i < 11000100


Example 2: PIG

Datapath and Control Registers

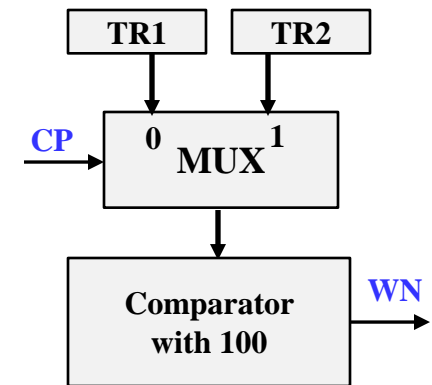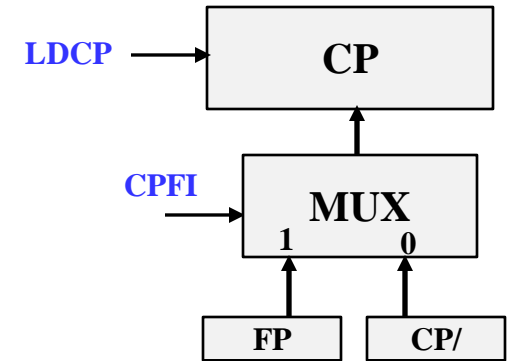 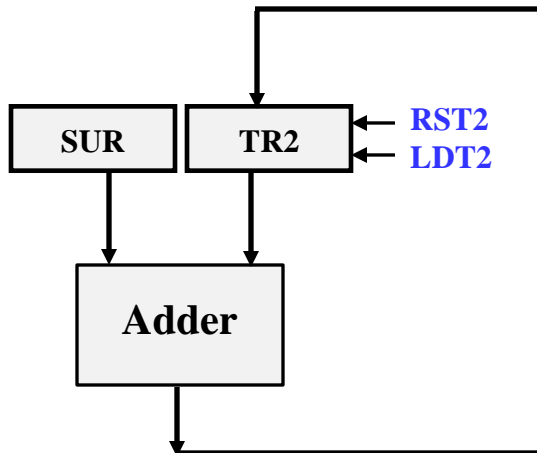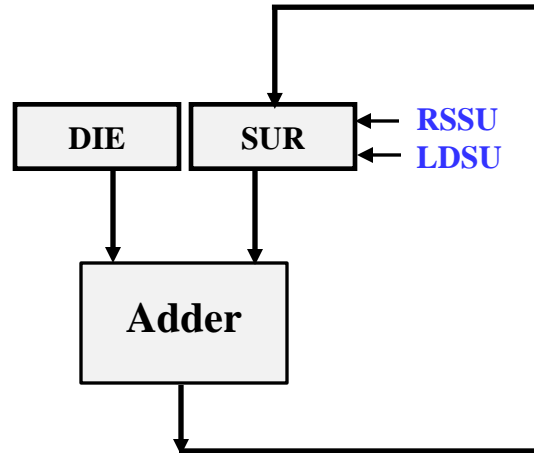 


Example 2: PIG

SMD with Control Signal Outputs Replacing Register Transfers

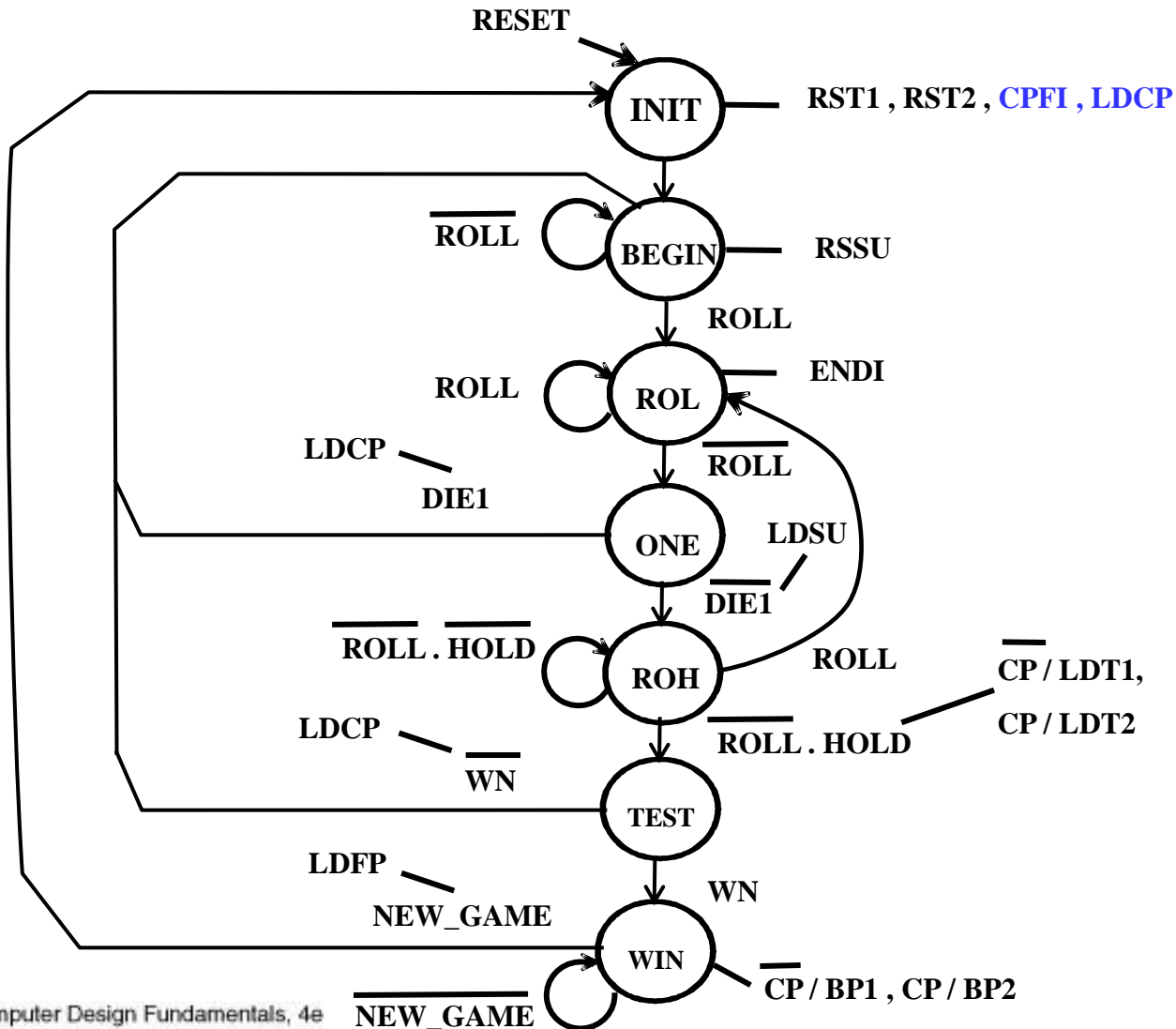

Example 2: PIG


Datapath and Control Registers

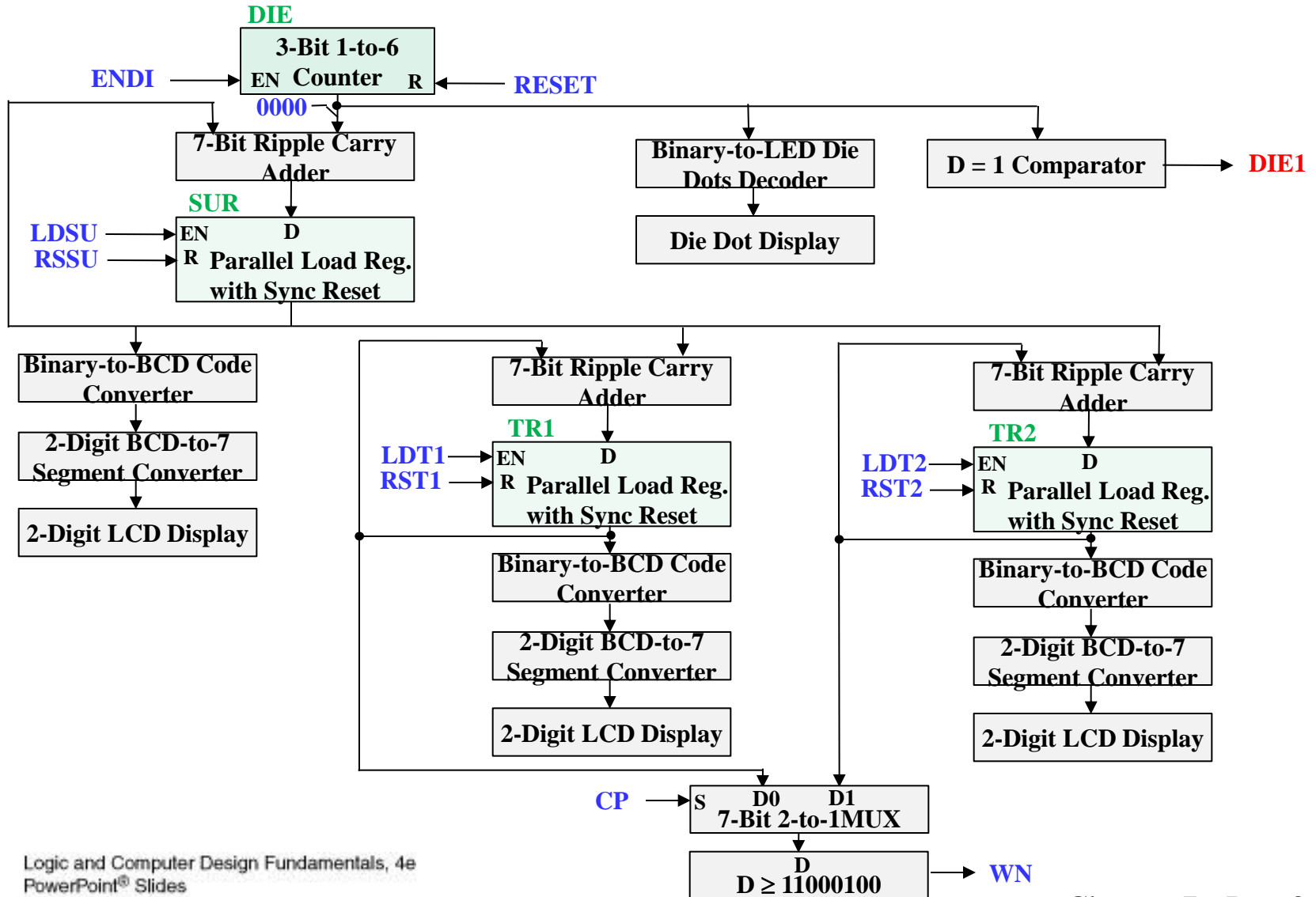

Microprogrammed Control

- ***Microprogrammed Control***— a control unit with binary control values stored as words in memory.
- ***Microinstructions***— words in the control memory.
- ***Microprogram***— a sequence of microinstructions.
- ***Control Memory***— RAM or ROM memory holding the microinstructions.
- ***Writeable Control Memory***— RAM Memory into which microinstructions may be written

Microprogrammed Control (continued)

 

Terms of Use

- **All (or portions) of this material © 2008 by Pearson Education, Inc.**
- **Permission is given to incorporate this material or adaptations thereof into classroom presentations and handouts to instructors in courses adopting the latest edition of Logic and Computer Design Fundamentals as the course textbook.**
- **These materials or adaptations thereof are not to be sold or otherwise offered for consideration.**
- **This Terms of Use slide or page is to be included within the original materials or any adaptations thereof.**