

---

# **Logic and Computer Design Fundamentals**

## **Integrated Circuits**

**Charles Kime & Thomas Kaminski**

© 2008 Pearson Education, Inc.  
(Hyperlinks are active in View Show mode)

# Overview

---

- **Part 1 – The Design Space**
  - **Integrated Circuits**
    - **Levels of Integration**
    - **Technology Parameters**
- **Part 2 – Propagation Delay and Timing**
- **Part 3 - Programmable Implementation Technologies**

# Integrated Circuits

---

- **Integrated circuit (informally, a “chip”) is a semiconductor crystal (most often silicon) containing the electronic components for the digital gates and storage elements which are interconnected on the chip.**
- **Terminology - Levels of chip integration**
  - ***SSI (small-scale integrated)* - fewer than 10 gates**
  - ***MSI (medium-scale integrated)* - 10 to 100 gates**
  - ***LSI (large-scale integrated)* - 100 to thousands of gates**
  - ***VLSI (very large-scale integrated)* - thousands to 100s of millions of gates**


# Technology Parameters

---


- **Specific gate implementation technologies are characterized by the following parameters:**
  - ***Fan-in*** – the number of inputs available on a gate
  - ***Fan-out*** – the number of standard loads driven by a gate output
  - ***Logic Levels*** – the signal value ranges for 1 and 0 on the inputs and 1 and 0 on the outputs
  - ***Noise Margin*** – the maximum external noise voltage superimposed on a normal input value that will not cause an undesirable change in the circuit output
  - ***Cost for a gate*** - a measure of the contribution by the gate to the cost of the integrated circuit
  - ***Propagation Delay*** – The time required for a change in the value of a signal to propagate from an input to an output
  - ***Power Dissipation*** – the amount of power drawn from the power supply and consumed by the gate

# Logic Levels & Noise Margin
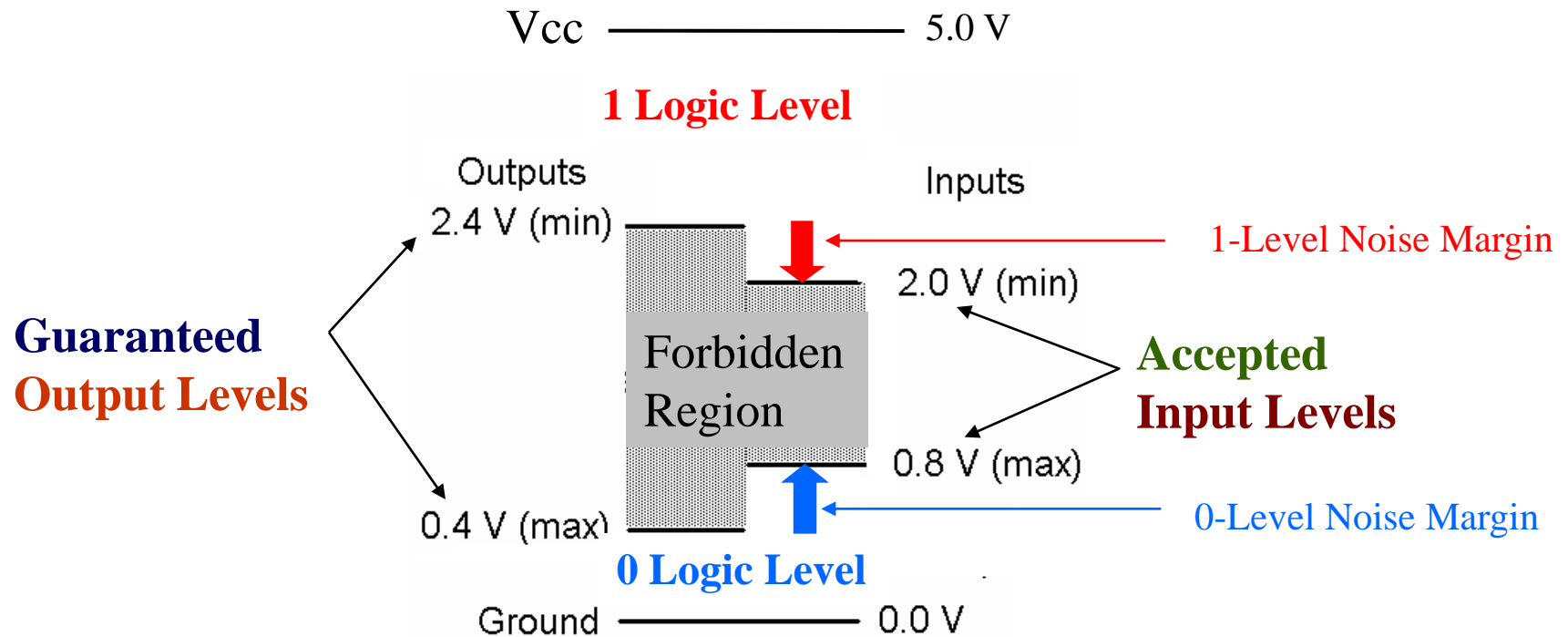
## Standard TTL Output and Inputs Voltage Levels



# Logic Levels & Noise Margin

 

High and low noise margins

$$\text{High-Level Noise Margin} = V_{OH} - V_{IH}$$


$$\text{Low-Level Noise margin} = V_{IL} - V_{OL}$$

# Fan-out

---

- **Fan-out can be defined in terms of a standard load**
  - **Example: 1 standard load equals the load contributed by the input of 1 inverter.**

# Fan-out


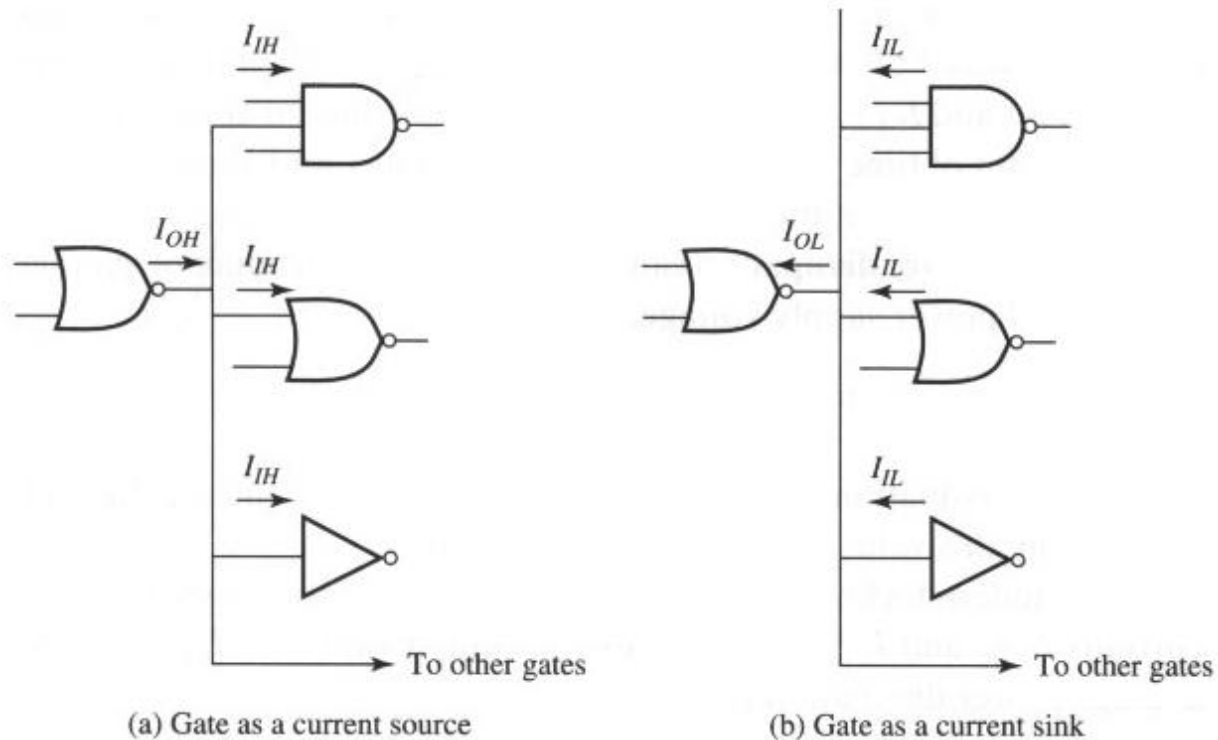


Current flow in a typical logic circuit


$$\text{Fan-out} = \min (I_{OH}/I_{IH}, I_{OL}/I_{IL})$$
  
# Fan-Out for TTL Loads

- **Fan Out =  $I_{OH}/I_{IH} = I_{OL}/I_{IL}$**
- **=  $400 \mu\text{A}/40 \mu\text{A} = 16 \text{ mA}/1.6 \text{ mA} = 10$**




# Fan-Out for TTL Loads

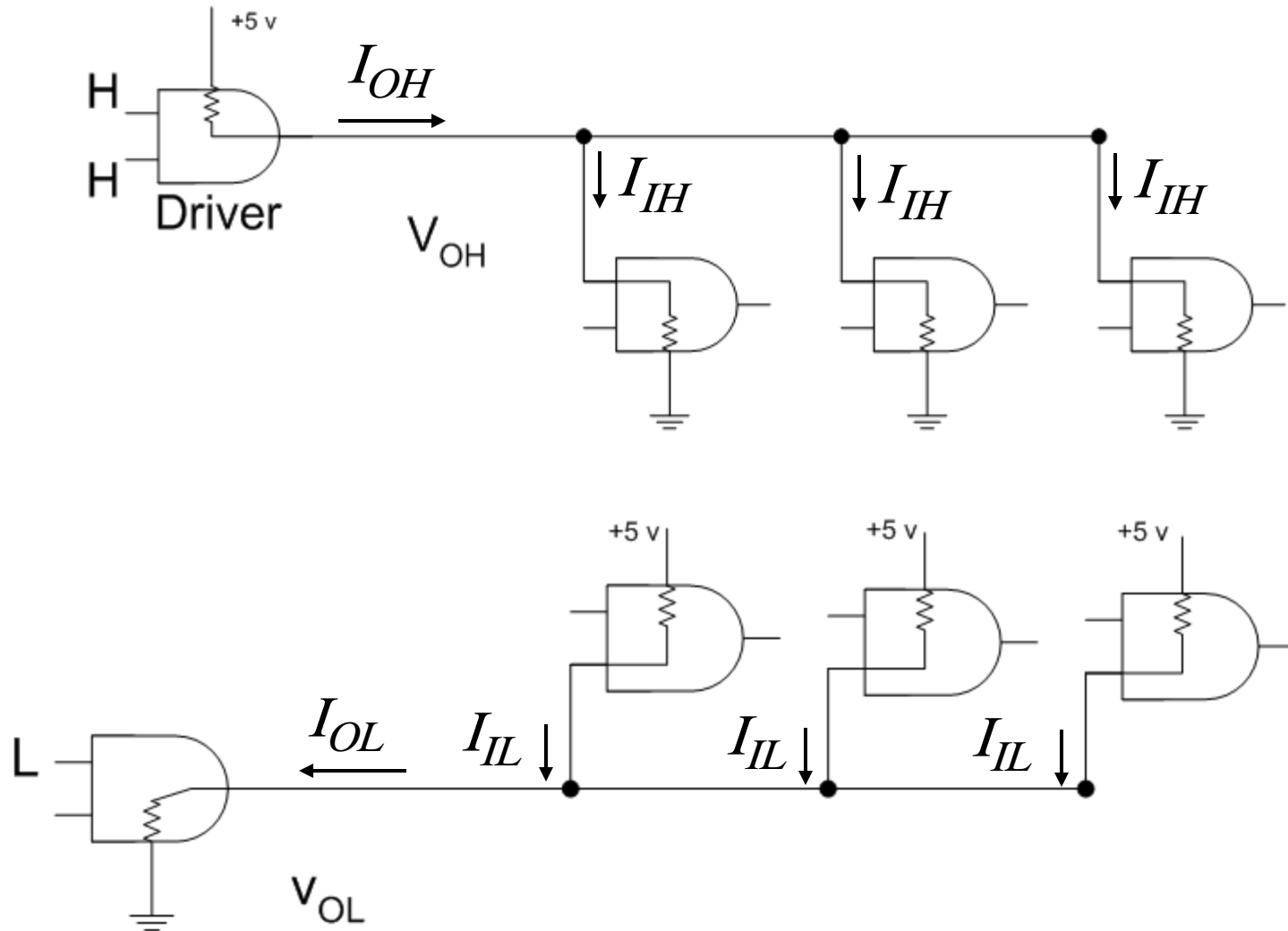
 
# Transition Time

- ***Transition time*** -the time required for a signal to change from H to L,  $t_{HL}$ , or from L to H,  $t_{LH}$



**Rise Time : a signal to switch from 10% to 90%**

**Fall Time : a signal to switch from 90% to 10%**

# Cost

---

- In an integrated circuit:
  - The cost of a gate is **proportional** to the **chip area occupied by the gate**
  - The gate area is roughly **proportional** to the **number and size of the transistors and the amount of wiring connecting them**
  - Ignoring the wiring area, the gate area is roughly **proportional** to the **gate input count**
  - **So gate input count is a rough measure of gate cost**
- If the actual chip layout area occupied by the gate is known, it is a far more accurate measure

# Power Dissipation

---

**In TTL :**

**Gate Output High      ( $I_{CCH}$ )**

**Gate Output Low      ( $I_{CCL}$ )**

**Average Power Dissipated:**

$$P_{AVG} = V_{cc} I_{cc}$$

$$P_{AVG} = V_{cc} (I_{CCH} + I_{CCL})/2$$

---

# **Part 2**

# **Propagation Delay and Timing**

# Overview

---


- **Part 1 – The Design Space**
- **Part 2 – Propagation Delay and Timing**
  - **Propagation Delay**
  - **Delay Models**
  - **Cost/Performance Tradeoffs**
  - **Flip-Flop Timing**
  - **Circuit & System Level Timing**
- **Part 3 - Programmable Implementation Technologies**

# Propagation Delay

---


- **Propagation delay** is the time for a change on an input of a gate to propagate to the output.
- Delay is usually measured at the **50%** point with respect to the H and L output voltage levels.
- **High-to-low ( $t_{PHL}$ ) and low-to-high ( $t_{PLH}$ )** output signal changes may have different propagation delays.
- High-to-low (HL) and low-to-high (LH) transitions are defined with **respect to the output, not** the input.
- An HL input transition causes:
  - an LH output transition if the gate inverts and
  - an HL output transition if the gate does not invert.

# Propagation Delay (continued)

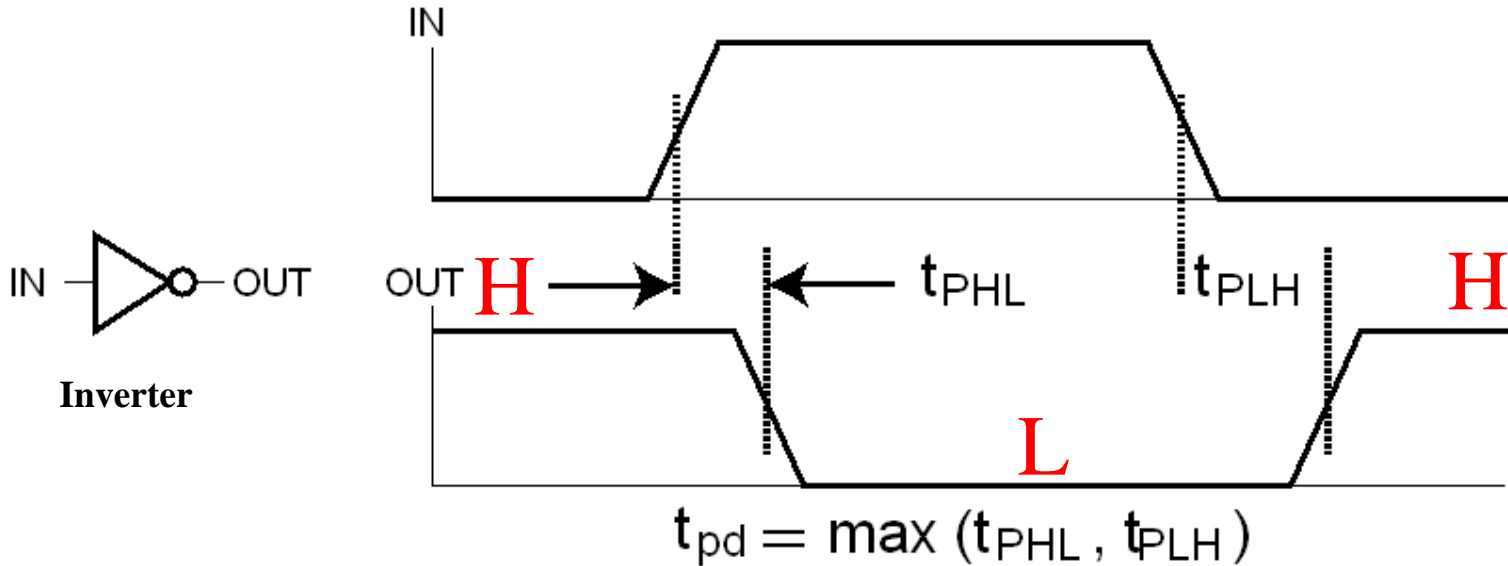

- Propagation delays measured at the midpoint between the L and H values.
- $t_{PLH}$  = The low-to-high propagation time.
- $t_{PHL}$  = The high-to-low propagation time.
- $t_{pd}$  = Propagation delay =  $\text{Max}(t_{PLH}, t_{PHL})$


# Propagation Delay

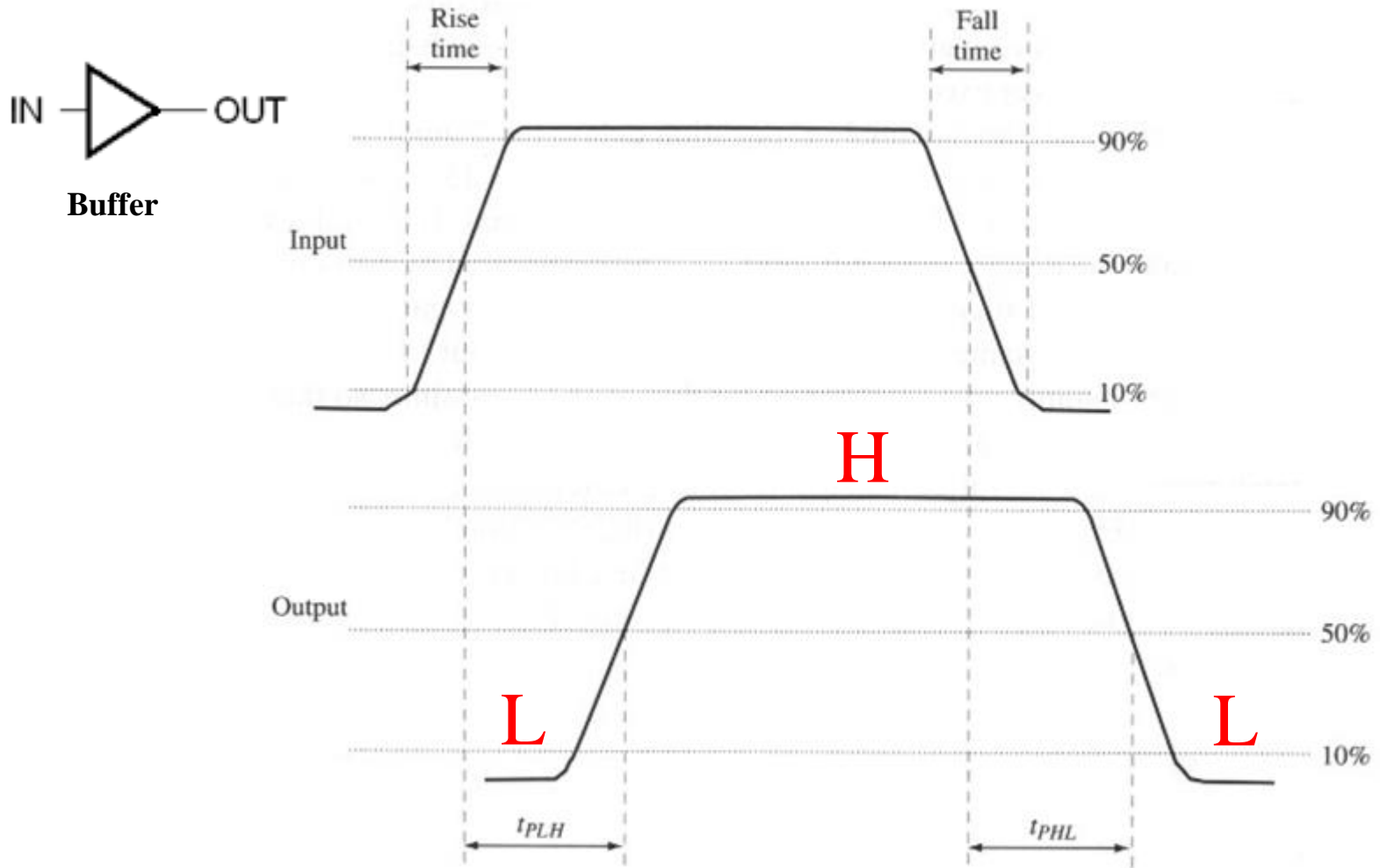

Propagation Delay:  $t_p = \max(t_{PLH}, t_{PHL})$
 
# Propagation Delay Example

- Find  $t_{PHL}$ ,  $t_{PLH}$  and  $t_{pd}$  for the signals given




# Delay Models

---

- **Transport delay** - a change in the output in response to a change on the inputs occurs after a fixed specified delay
- **Inertial delay** - similar to transport delay, except that if the input changes such that the output is to change twice in a time interval less than the *rejection time*, the output changes do not occur. Models typical electronic circuit behavior, namely, **rejects narrow “pulses” on the outputs**

# Delay Model

## Example – AND Gate

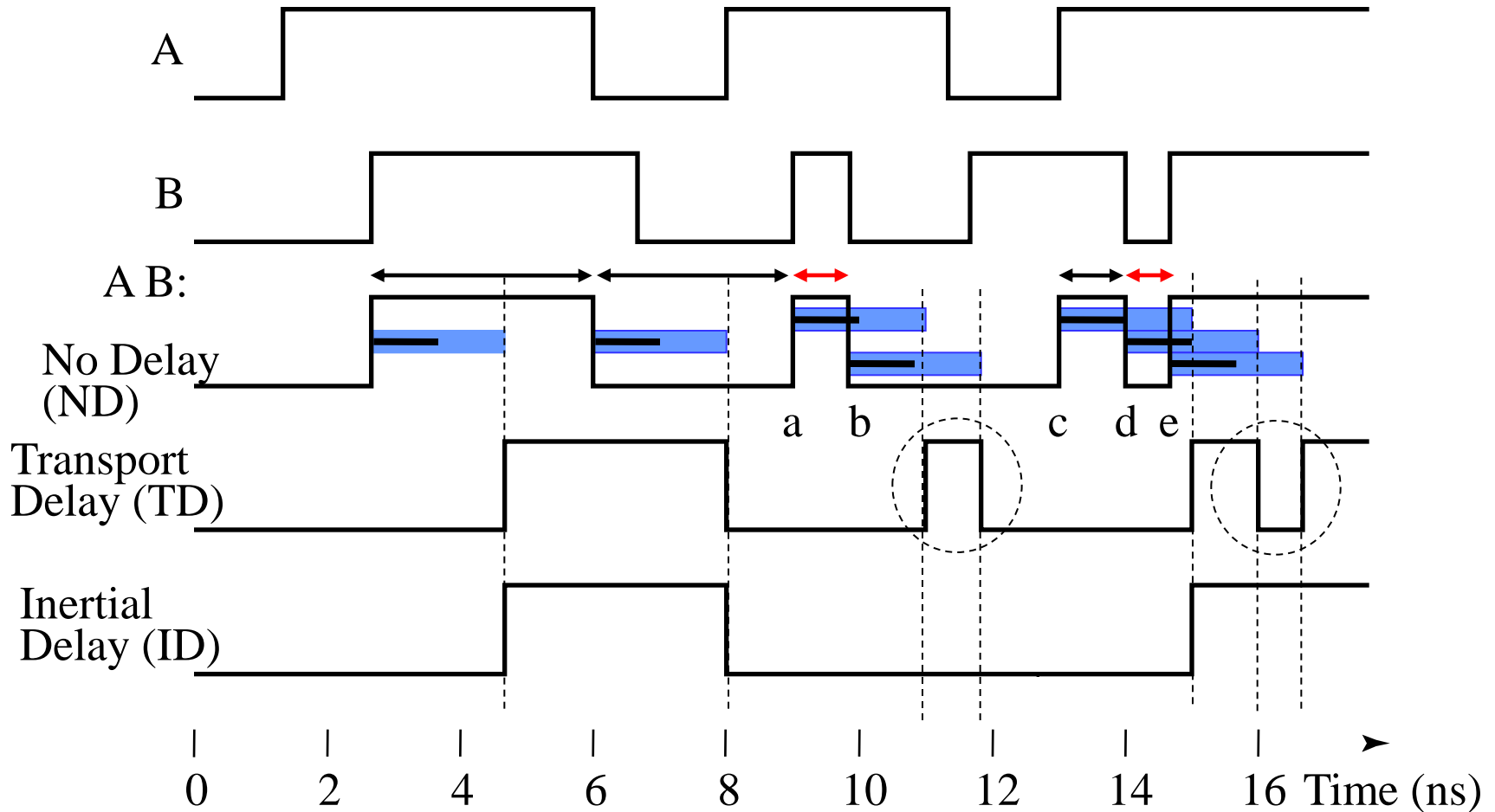

**Propagation Delay = 2.0 ns Rejection Time = 1.0 ns**

# Delay Models

---

- To determine whether an **edge** appears in the ID output, it must be determined whether the second edge occurs in the ND output before the end of the rejection time, and whether the edge will result in a change in the ID output.
- Since **edge b** occurs before the end of the rejection time for **edge a** in the ND output, **edge a** does not appear in the ID output.
- Since **edge b** does not change the state of ID, it is ignored.
- Since **edge d** occurs at the rejection time after **edge c** in the ND output, **edge c** appears.
- **Edge e** occurs within the rejection time after **edge d**, so **edge d** does not appear.
- Since **edge c** appeared and **edge d** did not appear, **edge e** does not cause a change.

# Fan-out and Delay

---

- The fan-out loading a gate's output affects the gate's propagation delay
- **Example 1:**
  - One realistic equation for  $t_{pd}$  for a NAND gate with 4 inputs is:
$$t_{pd} = 0.07 + 0.021 SL \text{ ns}$$
  - SL is the number of standard loads the gate is driving, i. e., its fan-out in standard loads
  - For  $SL = 4.5$ ,  $t_{pd} = 0.1645 \text{ ns}$
- If this effect is considered, the delay of a gate in a circuit takes on different values depending on the circuit load on its output.

# Fan-out and Delay

---

## ■ Example 2:

- One realistic equation for  $t_{pd}$  for a NAND gate with 4 inputs is:


$$t_{pd} = 0.07 + 0.021 SL \text{ ns}$$

- 4-input NAND output is attached to the inputs of the following gates with the given number of standard loads representing the inputs:
  - 4-input NOR gate – 0.80 standard load
  - 3-input NAND gate – 1.00 standard load, and
  - Inverter – 1.00 standard load.
- $t_{pd} = 0.07 + 0.021 (0.80 + 1.00 + 1.00) = 0.1288 \text{ ns}$

# Cost/Performance Tradeoffs

 
## Gate-Level Example:

- **NAND gate G** with 20 standard loads on its output has a delay of 0.45 ns and has a normalized cost of 2.0



|       |         |
|-------|---------|
| Delay | 0.45 ns |
| Cost  | 2.0     |

 - A **buffer H** has a normalized cost of 1.5. The NAND gate driving the buffer with 20 standard loads gives a total delay of 0.33 ns




|       |               |
|-------|---------------|
| Delay | 0.33 ns       |
| Cost  | 2.0+1.5 = 3.5 |

- In which of the following cases should the buffer be added?
  1. The cost of this portion of the circuit cannot be more than 2.5  
→ No Buffer
  2. The delay of this portion of the circuit cannot be more than 0.40 ns  
→ Use Buffer
  3. The delay of this portion of the circuit must be less than 0.35 ns and the cost less than 3.0  
→ Irrelevant - Buffer is needed to satisfy delay constraint, but cannot satisfy cost constraint.

 
# Flip-Flop Timing Parameters

- $t_s$  - setup time
- $t_h$  - hold time
- $t_w$  - clock pulse width
- $t_{px}$  - propagation delay



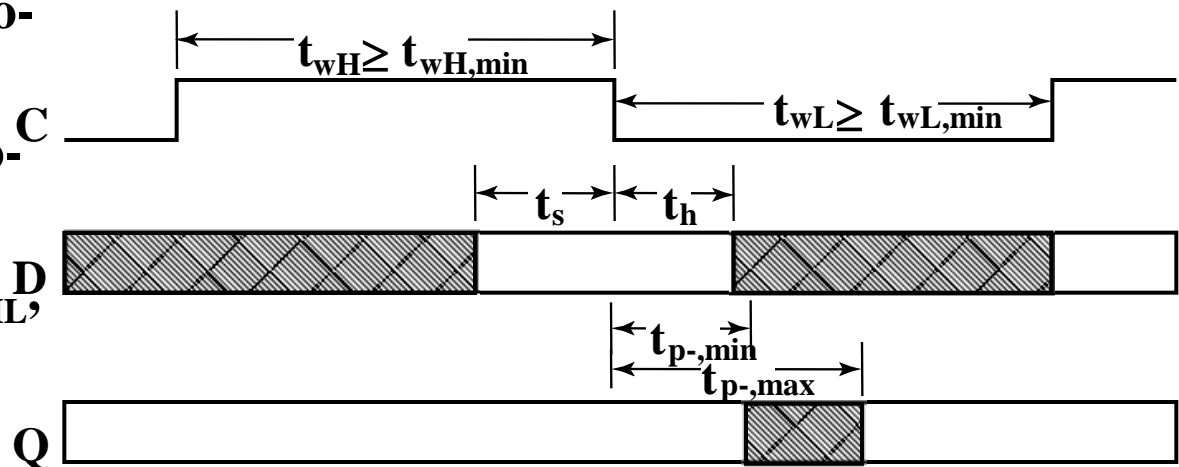(a) Pulse-triggered (positive pulse)

- $t_{PHL}$  - High-to-Low
- $t_{PLH}$  - Low-to-High
- $t_{pd} - \max(t_{PHL}, t_{PLH})$



(b) Edge-triggered (negative edge)


# Flip-Flop Timing Parameters

---

- **$t_s$  - setup time**
  - **Master-slave** - Equal to the width of the triggering pulse (**Master**)
  - **Edge-triggered** - Equal to a time interval that is generally much less than the width of the triggering pulse
- **$t_h$  - hold time** - Often equal to zero
- **$t_{px}$  - propagation delay**
  - Same parameters as for gates except
  - Measured from clock edge that triggers the output change to the output change
 
# Circuit and System Level Timing

- Consider a system comprised of ranks of flip-flops connected by logic:
- If the **clock period is too short**, some data changes will not propagate through the circuit to flip-flop inputs before the setup time interval begins



# Circuit and System Level Timing


---

## ■ New Timing Components


- **$t_p$  - clock period** - The interval between occurrences of a specific clock edge in a periodic clock
- **$t_{pd,COMB}$**  - total delay of combinational logic along the path from flip-flop output to flip-flop input
- **$t_{slack}$**  - extra time allowed in the clock period in beyond that required by the path
  - Must be greater than or equal to zero on all paths for correct operation
 
# Circuit and System Level Timing

- Timing components along a path from flip-flop to flip-flop



(a) Edge-triggered (positive edge)

 

(b) Pulse-triggered (negative pulse)

# Circuit and System Level Timing

---

- **Timing Equations**

$$t_p = t_{\text{slack}} + (t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s)$$

- For  $t_{\text{slack}}$  greater than or equal to zero,

$$t_p \geq \max (t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s)$$

for all paths from flip-flop output to flip-flop input

- **Can be calculated more precisely by using  $t_{\text{PHL}}$  and  $t_{\text{PLH}}$  values instead of  $t_{\text{pd}}$  values, but requires consideration of inversions on paths**

# Example 1: Calculation of Allowable $t_{pd,COMB}$

---

- Compare the allowable combinational delay for a specific circuit:
  - a) **Using edge-triggered flip-flops**
  - b) **Using master-slave flip-flops**
  
- **Parameters**
  - $t_{pd,FF}(\text{max}) = 1.0 \text{ ns}$
  - $t_s(\text{max}) = 0.3 \text{ ns}$  for edge-triggered flip-flops
  - $t_s = t_{wH} = 1.0 \text{ ns}$  for master-slave flip-flops
  - **Clock frequency = 250 MHz**

# Example 1: Calculation of Allowable $t_{pd,COMB}$

---

- **Calculations:**  $t_p = 1/\text{clock frequency} = 4.0 \text{ ns}$ 
  - **Edge-triggered:**  $4.0 \geq 1.0 + t_{pd,COMB} + 0.3$ ,  $t_{pd,COMB} \leq 2.7 \text{ ns}$
  - **Master-slave:**  $4.0 \geq 1.0 + t_{pd,COMB} + 1.0$ ,  $t_{pd,COMB} \leq 2.0 \text{ ns}$
- **Comparison:** Suppose that for a gate, average  $t_{pd} = 0.3 \text{ ns}$ 
  - **Edge-triggered:** Approximately 9 gates allowed on a path
  - **Master-slave:** Approximately 6 to 7 gates allowed on a path

# Example 2: Clock Period & Frequency Calculations

---

## ■ Parameters

- $t_{pd,FF}(\text{max}) = 0.2 \text{ ns}$
- $t_s(\text{max}) = 0.1 \text{ ns}$  for edge-triggered flip-flops
- $t_{pd,COMB}(\text{max}) = 1.3 \text{ ns}$
- $t_p = 1.5 \text{ ns}$

## ■ Solution

- $t_p = t_{\text{slack}} + (t_{pd,FF} + t_{pd,COMB} + t_s)$
- $\rightarrow 1.5 = t_{\text{slack}} + (0.2 + 1.3 + 0.1)$
- $\rightarrow t_{\text{slack}} = -0.1 \text{ ns}$
- $t_{\text{slack}}$  has to be greater than or equal to zero for the longest path
- $\rightarrow t_p$  is too small
- $\rightarrow t_p \geq t_{p, \text{min}} = 1.6 \text{ ns}$
- $f_{\text{max}} = 1 / 1.6 \text{ ns} = 625 \text{ MHz}$

---

# **Part 3**

# **Programmable Implementation Technologies**

# Overview

---

- **Part 1 – The Design Space**
- **Part 2 – Propagation Delay and Timing**
- **Part 3 - Programmable Implementation Technologies**
  - **Why Programmable Logic?**
  - **Programming Technologies**
  - **Read-Only Memories (ROMs)**
  - **Programmable Logic Arrays (PLAs)**
  - **Programmable Array Logic (PALs)**

# Why Programmable Logic?

---

- **Facts:**

- It is most economical to produce an IC in large volumes
- Many designs required only small volumes of ICs


- **Need an IC that can be:**

- Produced in large volumes
- Handle many designs required in small volumes

- **A programmable logic part can be:**

- made in large volumes
- programmed to implement large numbers of different low-volume designs

# Programmable Logic

 


1



Universal Programmer



2

 

# Programmable Logic - More Advantages

---

- Many programmable logic devices are ***field-programmable***, i. e., can be programmed outside of the manufacturing environment
- Most programmable logic devices are ***erasable*** and ***reprogrammable***.
  - Allows “updating” a device or correction of errors
  - Allows reuse the device for a different design - the ultimate in re-usability!
  - Ideal for course laboratories
- Programmable logic devices can be used to ***prototype design*** that will be implemented for sale in regular ICs.
  - Complete Intel Pentium designs were actually prototyped with specialized systems based on large numbers of VLSI programmable devices!

# Programming Technologies

---

## ■ Programming technologies:

### 1. Fuse:

- Fuses which are initially CLOSED are selectively "blown out" by a higher than normal voltage to establish OPEN connections.
- The pattern of OPEN and CLOSED fuses defines the logic.
- **Permanent:** The devices cannot be reprogrammed because irreversible physical changes have occurred as a result of device programming .

### 2. Antifuse:

- Antifuses contain a material that is initially OPEN.
- Antifuses are selectively CLOSED by applying a higher than normal voltage.
- The pattern of OPEN and CLOSED fuses defines the logic.
- **Permanent:** The devices cannot be reprogrammed because irreversible physical changes have occurred as a result of device programming .

# Programming Technologies


## ■ Programming technologies (continued):

### 3. Single-bit storage element

- If the stored bit value is a 1, then the transistor is turned ON, and the connection between its source and drain forms a CLOSED path.
- If the stored bit value is a 0, then the transistor is turned OFF, and the connection between its source and drain forms an OPEN path.
- **Reprogrammable:** The storage element content can be changed electronically, the device can be easily reprogrammed.
- **Volatile:** The programmed logic is lost in the absence of the power supply voltage.
 
### 4. Transistor Switching Control

- Stored charge on a floating transistor gate
  - Erasable
  - Electrically erasable
  - Flash (as in Flash Memory)
- Storage elements (as in a memory)



# Technology Characteristics

---


- **Permanent** - Cannot be erased and reprogrammed
  - Fuse
  - Antifuse
  
- **Reprogrammable:**
  - **Volatile** - Programming lost if chip power lost
    - Single-bit storage element
  
  - **Non-Volatile**
    - Erasable
    - Electrically erasable
    - Flash (as in Flash Memory)

# Programmable Configurations


---

- **Read Only Memory (ROM)** - a fixed array of AND gates and a programmable array of OR gates
- **Programmable Array Logic (PAL)<sup>®</sup>** - a programmable array of AND gates feeding a fixed array of OR gates.
- **Programmable Logic Array (PLA)** - a programmable array of AND gates feeding a programmable array of OR gates.
- **Complex Programmable Logic Device (CPLD) /Field-Programmable Gate Array (FPGA)** - complex enough to be called “architectures” - See VLSI Programmable Logic Devices reading supplement


# ROM, PAL and PLA Configurations

 

(a) Programmable read-only memory (PROM)

 

 (b) Programmable array logic (PAL) device



(c) Programmable logic array (PLA) device

# Read Only Memory

---

- Read Only Memories (**ROM**) or Programmable Read Only Memories (**PROM**) have:
  - **N input lines (Address Lines),**
  - **M output lines, and**
  - **$2^N$  decoded minterms.**
- **Fixed AND array with  $2^N$  outputs implementing all N-literal minterms.**
- **Programmable OR Array with M outputs lines to form up to M sum of minterm expressions.**

# Read Only Memory

---


- A program for a ROM or PROM is simply a multiple-output truth table
  - If a **1** entry, a **connection** is made to the corresponding minterm for the corresponding output
  - If a **0**, **no connection** is made
- Can be viewed as a ***memory with the inputs as addresses of data*** (output values), hence **ROM or PROM names!**

# Read Only Memory Example

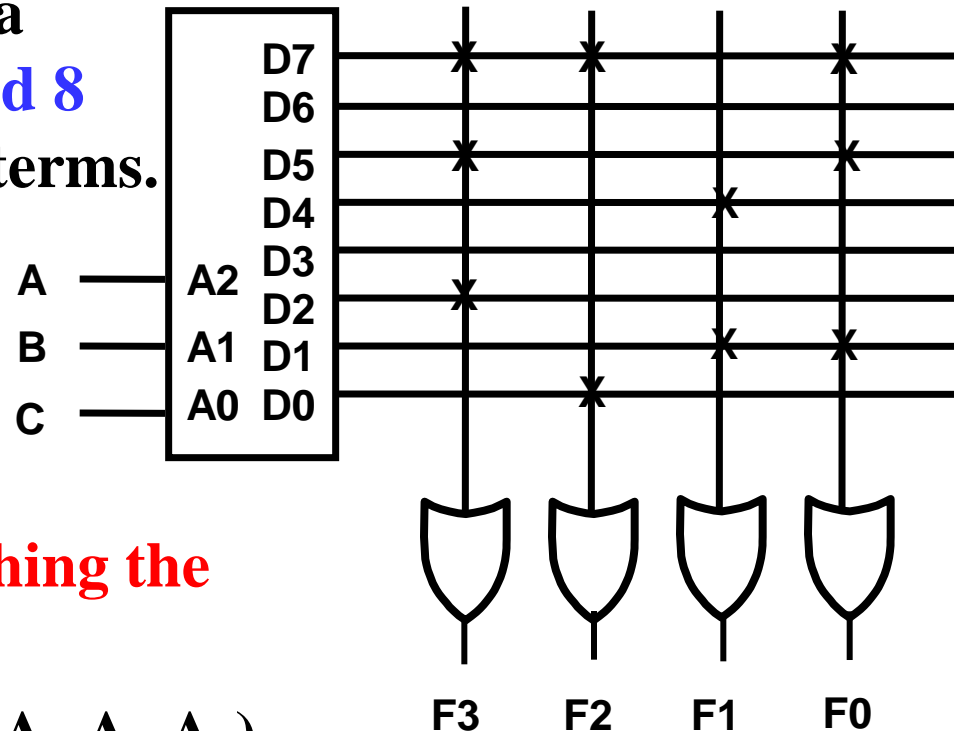- **Example: A 8 X 4 ROM (N = 3 input lines, M= 4 output lines)**

- The fixed "AND" array is a "decoder" with 3 inputs and 8 outputs implementing minterms.

- The programmable "OR" array uses a single line to represent all inputs to an OR gate. An "X" in the array corresponds to attaching the minterm to the OR




- **Read Example: For input (A<sub>2</sub>,A<sub>1</sub>,A<sub>0</sub>) = 001, output is (F<sub>3</sub>,F<sub>2</sub>,F<sub>1</sub>,F<sub>0</sub>) = 0011.**

- **What are functions F<sub>3</sub>, F<sub>2</sub>, F<sub>1</sub> and F<sub>0</sub> in terms of (A<sub>2</sub>, A<sub>1</sub>, A<sub>0</sub>)?**
 
# Programmable Array Logic (PAL)

- The PAL is the opposite of the ROM, having a programmable set of ANDs combined with fixed ORs.



Simplified programmable logic device

# Programmable Array Logic Example

- **4-input, 3-output PAL with fixed, 3-input OR terms**
- **What are the equations for F1 through F4?**

$$F1 = \bar{A} \bar{B} + \bar{C}$$

$$F2 = \bar{A} B \bar{C} + A C + A \bar{B}$$


$$F3 = AD + BD + F1$$

$$= AD + BD + \bar{A} \bar{B} + \bar{C}$$

$$F4 = AB + CD + \bar{F1}$$

$$= AB + CD + (A+B)C$$

$$= AB + CD + AC + BC$$

 

# Programmable Array Logic (PAL)

---

## ■ Advantages of PAL:


- For given internal complexity, a PAL can have **larger N and M**
- Some PALs have **outputs that can be complemented**, adding POS functions
- No multilevel circuit implementations in ROM (without external connections from output to input). **PAL has outputs from OR terms as internal inputs to all AND terms**, making implementation of multi-level circuits easier.

## ■ Disadvantage of PAL:

- ROM guaranteed to implement any M functions of N inputs. **PAL may have too few inputs to the OR gates.**

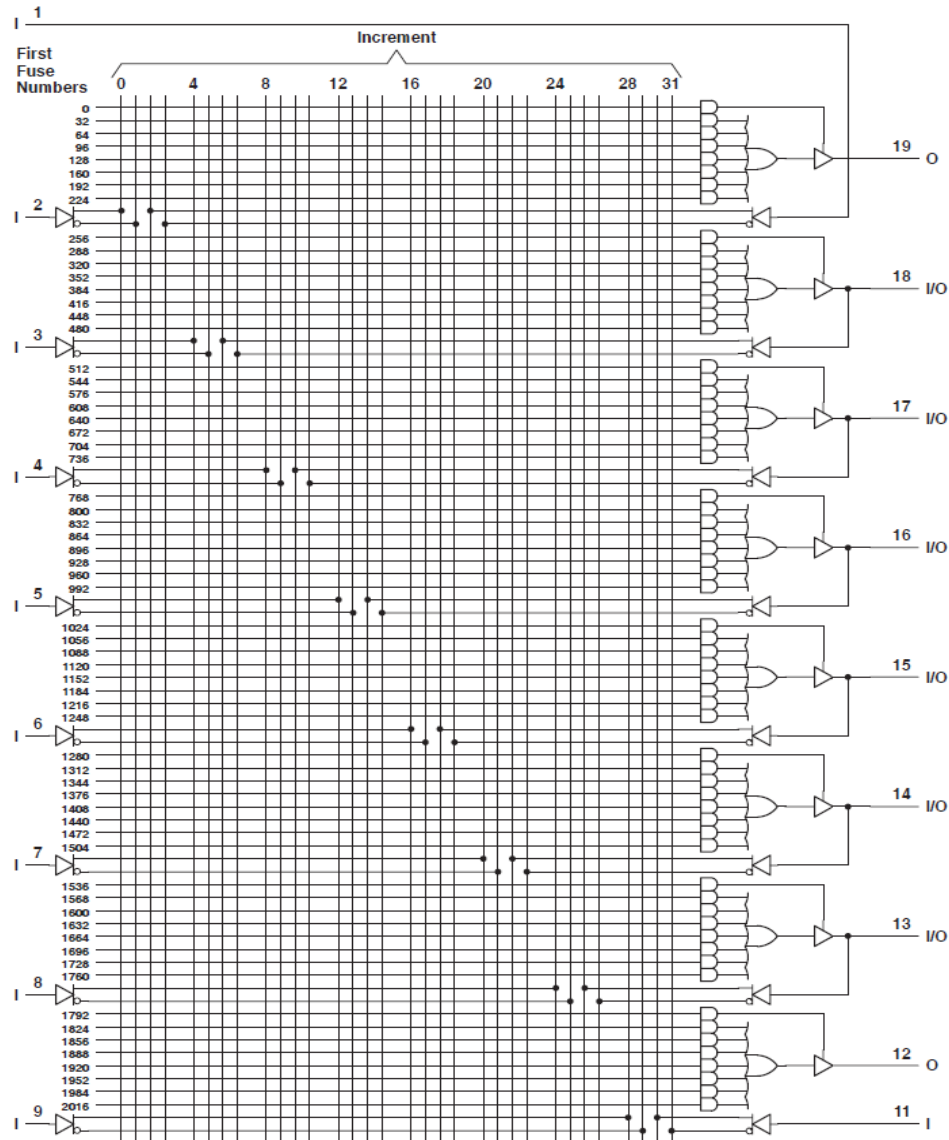
# PAL16H8

<http://www.datasheets.org.uk/pdf-datasheets/Databooks-2/Book291-186.html>



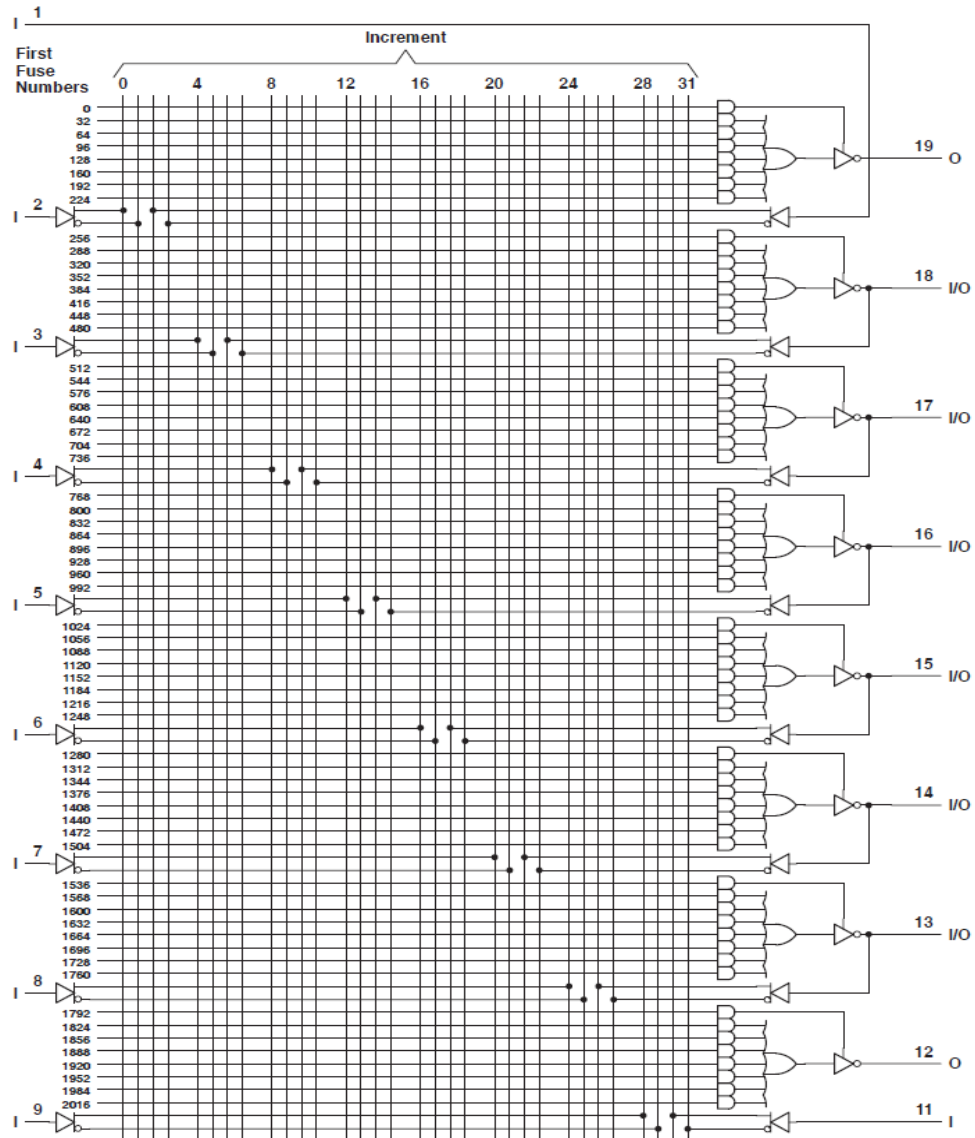
# PAL16L8

[http://www.datasheetcatalog.org/datasheets/166/34602\\_DS.pdf](http://www.datasheetcatalog.org/datasheets/166/34602_DS.pdf)



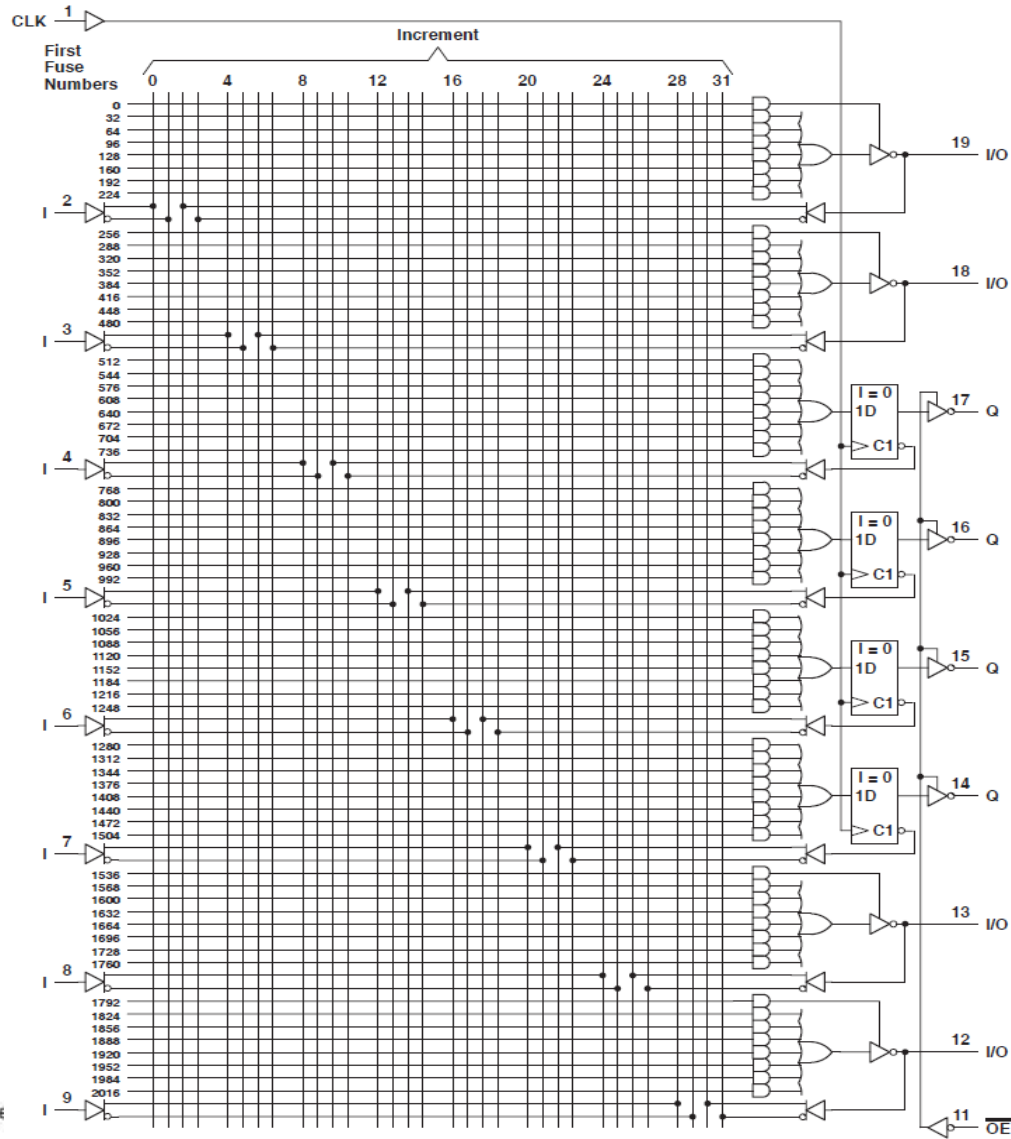
# PAL16R4

[http://www.datasheetcatalog.org/datasheets/166/34602\\_DS.pdf](http://www.datasheetcatalog.org/datasheets/166/34602_DS.pdf)



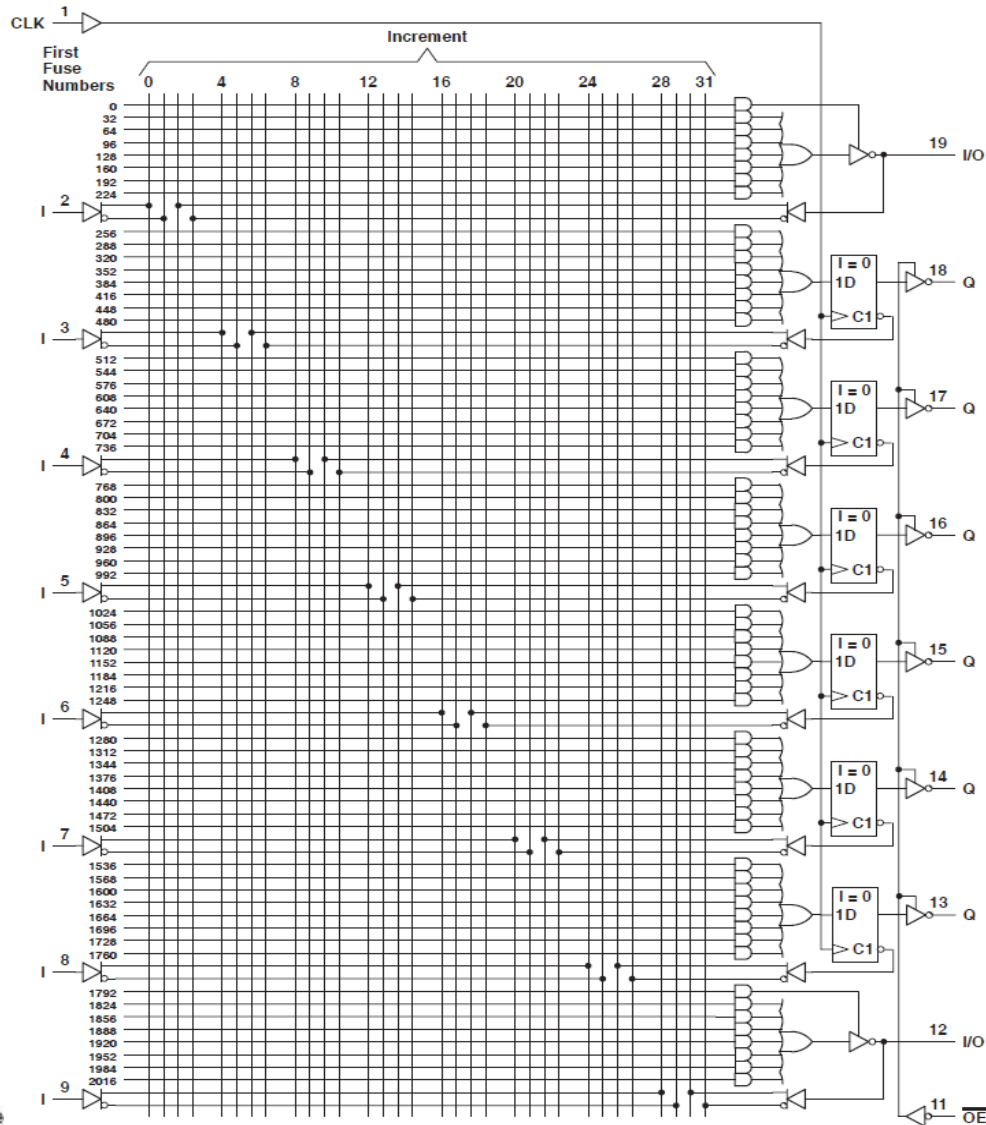
# PAL16R6

[http://www.datasheetcatalog.org/datasheets/166/34602\\_DS.pdf](http://www.datasheetcatalog.org/datasheets/166/34602_DS.pdf)


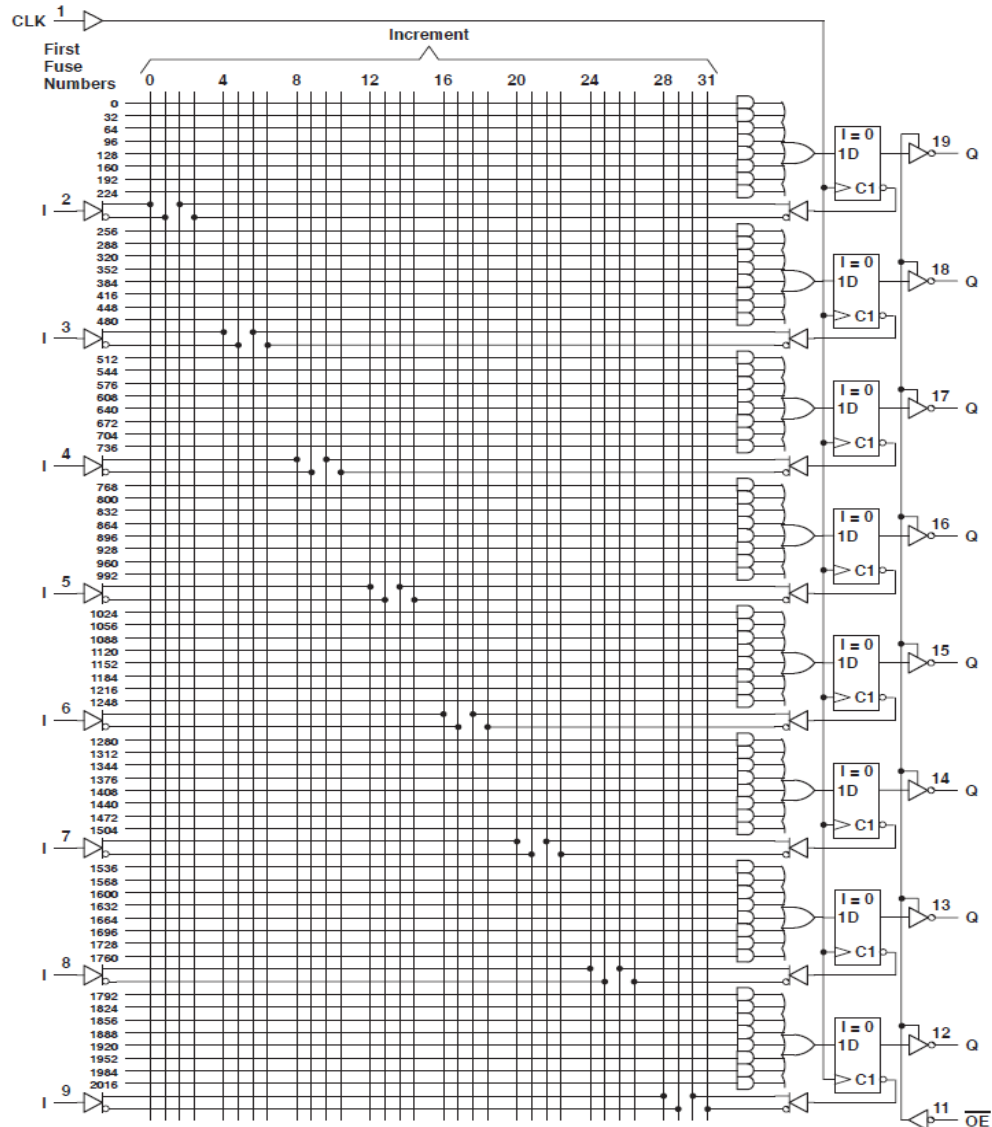
# PAL16R8

[http://www.datasheetcatalog.org/datasheets/166/34602\\_DS.pdf](http://www.datasheetcatalog.org/datasheets/166/34602_DS.pdf)



# Programmable Logic Array (PLA)

---

- Compared to a ROM and a PAL, a PLA is the most flexible having a programmable set of ANDs combined with a programmable set of ORs.
- **Advantages**
  - A PLA can have **large N and M** permitting implementation of equations that are impractical for a ROM (because of the number of inputs, N, required)
  - A PLA has **all of its product terms connectable to all outputs**, overcoming the problem of the limited inputs to the PAL ORs
  - Some PLAs have **outputs that can be complemented**, adding POS functions


# Programmable Logic Array (PLA)

---

## ■ **Disadvantages**

- **Often, the product term count limits the application of a PLA.**
- **Two-level multiple-output optimization is required to reduce the number of product terms in an implementation, helping to fit it into a PLA.**
- **Multi-level circuit capability available in PAL not available in PLA. PLA requires external connections to do multi-level circuits.**

# Programmable Logic Array Example

 

- What are the equations for  $F_1$  and  $F_2$ ?

$$\rightarrow F_1 = AB + BC + AC$$


$$\rightarrow F_2 = (AB + A'B')' = (A' + B')(A + B) = A'B + AB'$$

- Could the PLA implement the functions without the XOR gates?

**No.** If only SOP functions used, requires at least 5 AND gates.

X Fuse intact  
 + Fuse blown

 - 3-input, 2-output PLA with 4 product terms**



# Terms of Use

---

- **All (or portions) of this material © 2008 by Pearson Education, Inc.**
- **Permission is given to incorporate this material or adaptations thereof into classroom presentations and handouts to instructors in courses adopting the latest edition of Logic and Computer Design Fundamentals as the course textbook.**
- **These materials or adaptations thereof are not to be sold or otherwise offered for consideration.**
- **This Terms of Use slide or page is to be included within the original materials or any adaptations thereof.**